
High-Speed
Memory Systems

Spring 2014

CS-590.26
Lecture G

Bruce Jacob
David Wang

University
of Crete

SLIDE 1


CS-590.26, Spring 2014

High Speed Memory Systems: Architecture and Performance Analysis


Wires, Signalling, and Timing

Credit where credit is due:

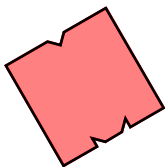Slides contain original artwork (© Jacob, Wang 2005)




“Digital” System Basics

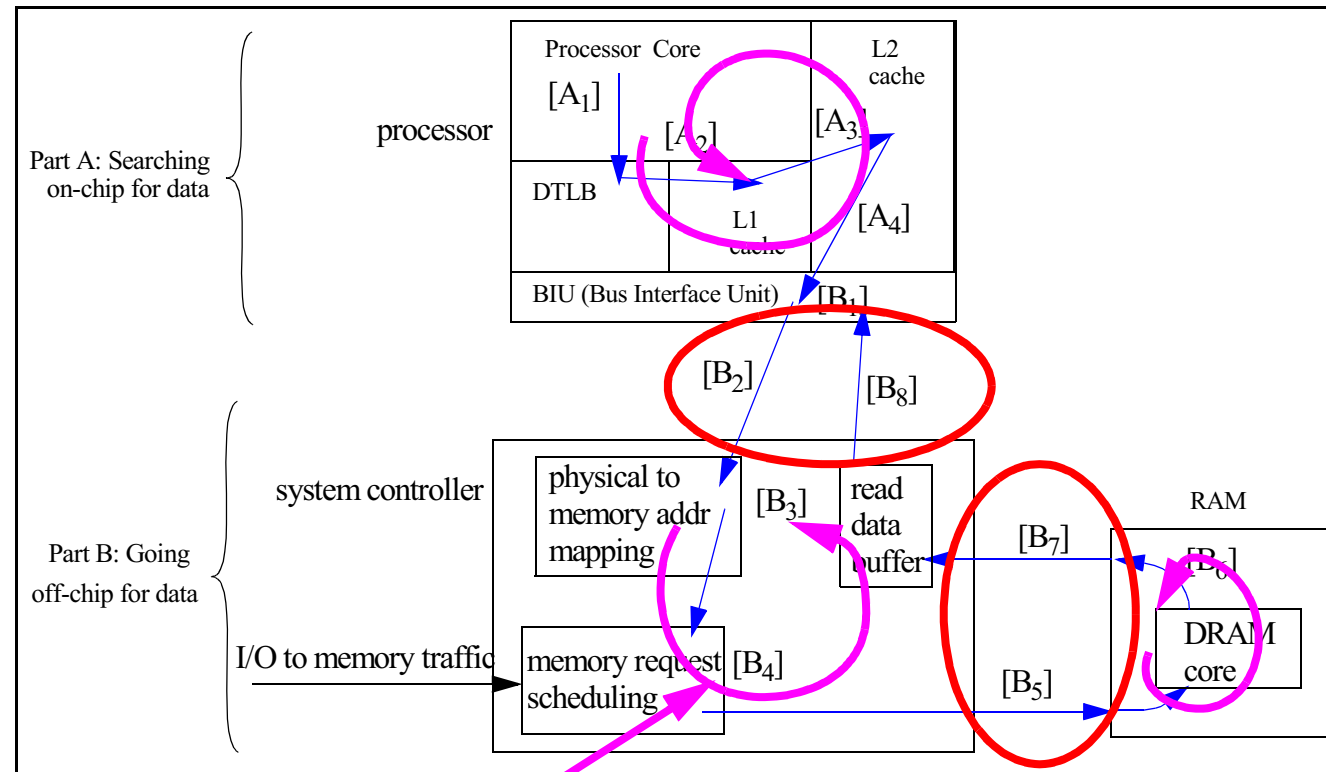


Chip performance scaling with respect to Moore's Law

 
Data transport speed on system board does not scale w.r.t. Moore's Law.




How Do We Go “Faster”?

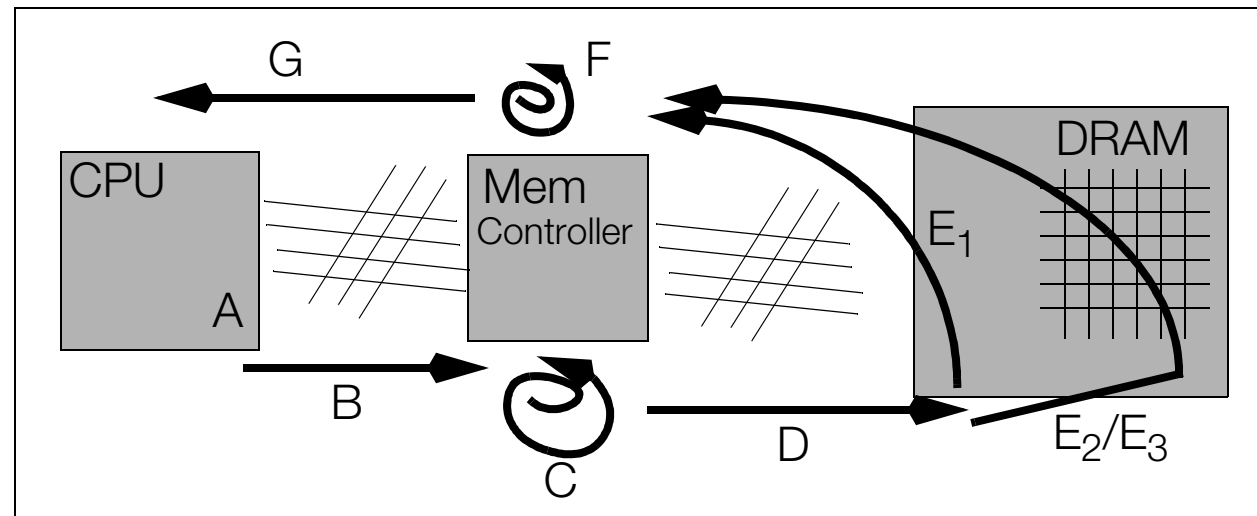

- Faster Logic** → A: Transaction request may be delayed in Queue
 - Faster Logic** → B: Transaction request sent to Memory Controller
 - Faster Logic** → C: Transaction converted to Command Sequences (may be queued)
 - Faster Wires** → D: Command/s Sent to DRAM
 - Faster Wires** → E₁: Requires only a **CAS** or
 - Faster Wires** → E₂: Requires **RAS + CAS** or
 - Faster Wires** → E₃: Requires **PRE + RAS + CAS**
 - Faster DRAM Circuits** → F: Data is staged at Controller
 - Faster DRAM Circuits** → G: Transaction sent back to CPU
- “DRAM Latency” = A + B + C + D + E + F + G

 


Protocol “Efficiency”


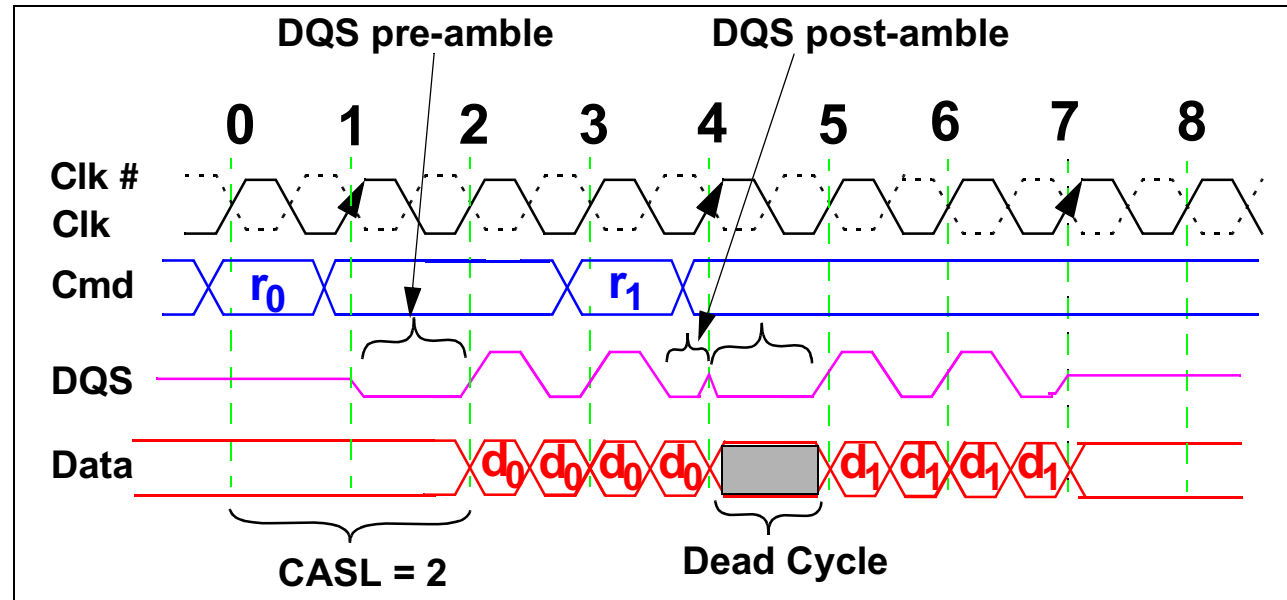


Back-to-back reads to different ranks


Can we make the cycles smaller?

 

Smaller Cycle Time Budget?

  


A Signaling System

 

- 1. Transmitter: Encodes data as current/voltage level onto the line**
- 2. Transmission Line: Deliver data from transmitter to receiver**
- 3. Receiver: Compare against reference to extract data**
- 4. Terminator: Remove signal from line, once they're received**
- 5. Clock: Tells transmitter when to send, receiver when to sample signal**

* Poulton ISSCC 1999 Signaling Tutorial

 

ENEE 359a
Lecture/s 10+11
Interconnects

Bruce Jacob

University of
Maryland
ECE Dept.

SLIDE 1

ENEE 359a


Digital Electronics

Interconnects

Prof. Bruce Jacob
blj@eng.umd.edu


Credit where credit is due:

 Slides contain original artwork (© Jacob 2004) as well as material taken liberally from Irwin & Vijay's CSE477 slides (PSU), Schmit & Strojwas's 18-322 slides (CMU), Dally's EE273 slides (Stanford), Wolf's slides for *Modern VLSI Design*, and/or Rabaey's slides (UCB).





Overview

 
- **Wires and their physical properties (MOSFETs, too ...)**
- **LC/RC/RLC transmission lines, characteristic impedance, reflections**
- **Dynamic considerations (e.g. skin effect)**
- **The Bottom Line: propagation delay, transistor sizing, inductive (Ldi/dt) noise, capacitive coupling, signal degradation, various rules of thumb for design**





Metal Layers in ICs

  



IBM's 6-layer copper interconnect

 

Some Transmission Lines

  

Cross Section of PCB Board

 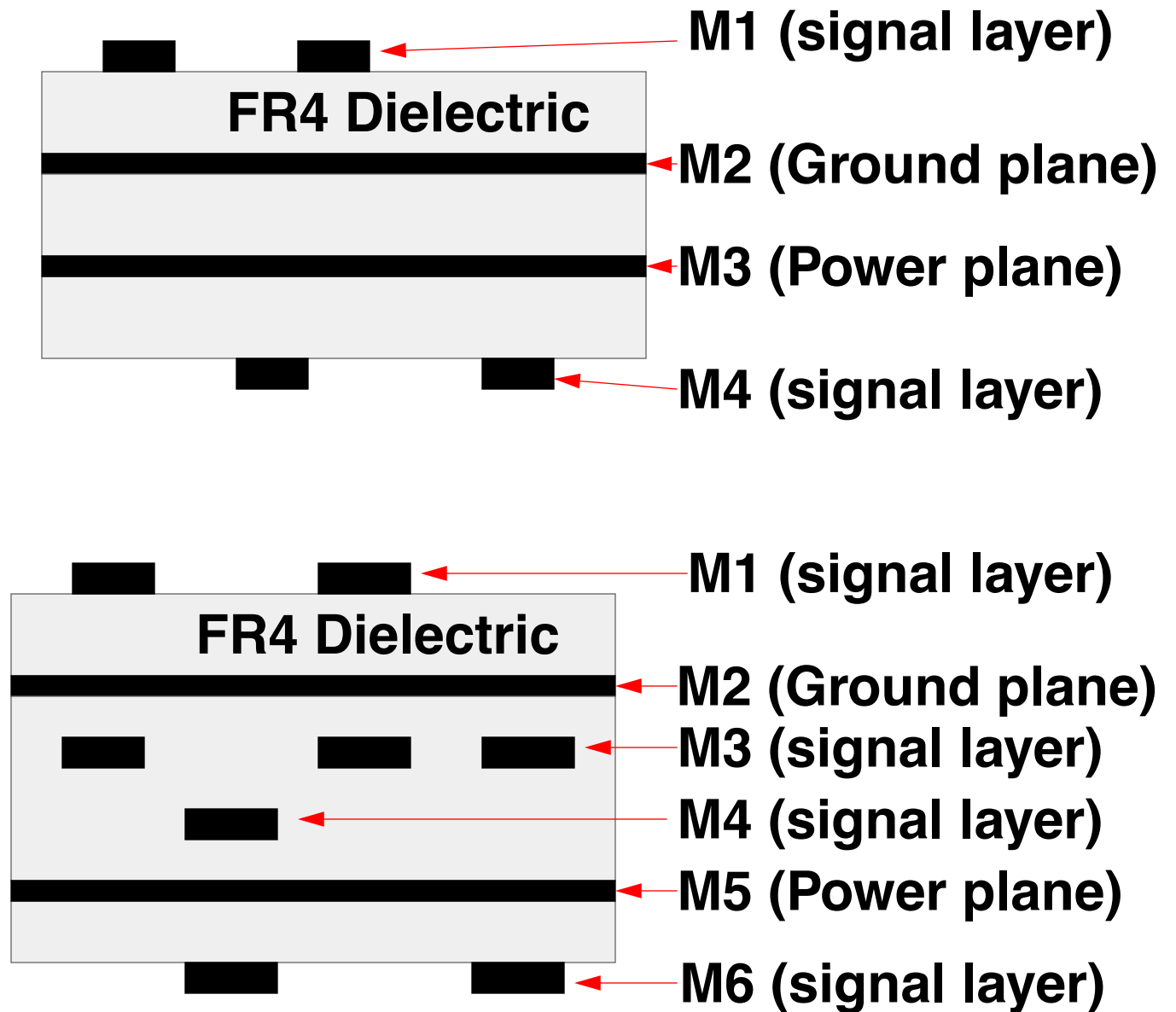

Wires in Digital Systems

Physically, wires are


- Stripguides on (and *in*) printed circuit-board cards, layed over & sandwiched between groundplanes
- Stripguides on ICs, layered atop each other
- Conductors in cables & cable assemblies
- Connectors

We tend to treat them as *IDEAL* wires


- No delay (equipotential)
- No capacitance, inductance, or resistance

They are *NOT* ideal ...

 
To build reliable systems, must understand properties & behavior




Metal Layers in ICs

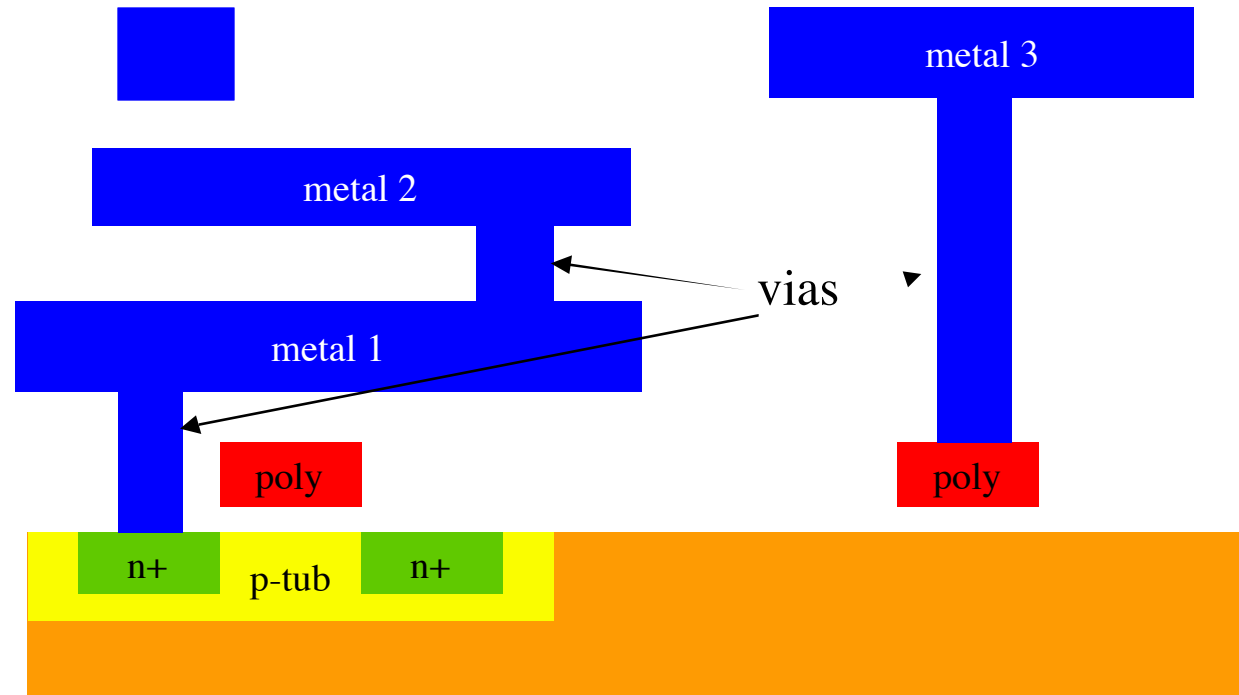


Remember the *RC Constant* τ ?

 


Metal Layers & Capacitances

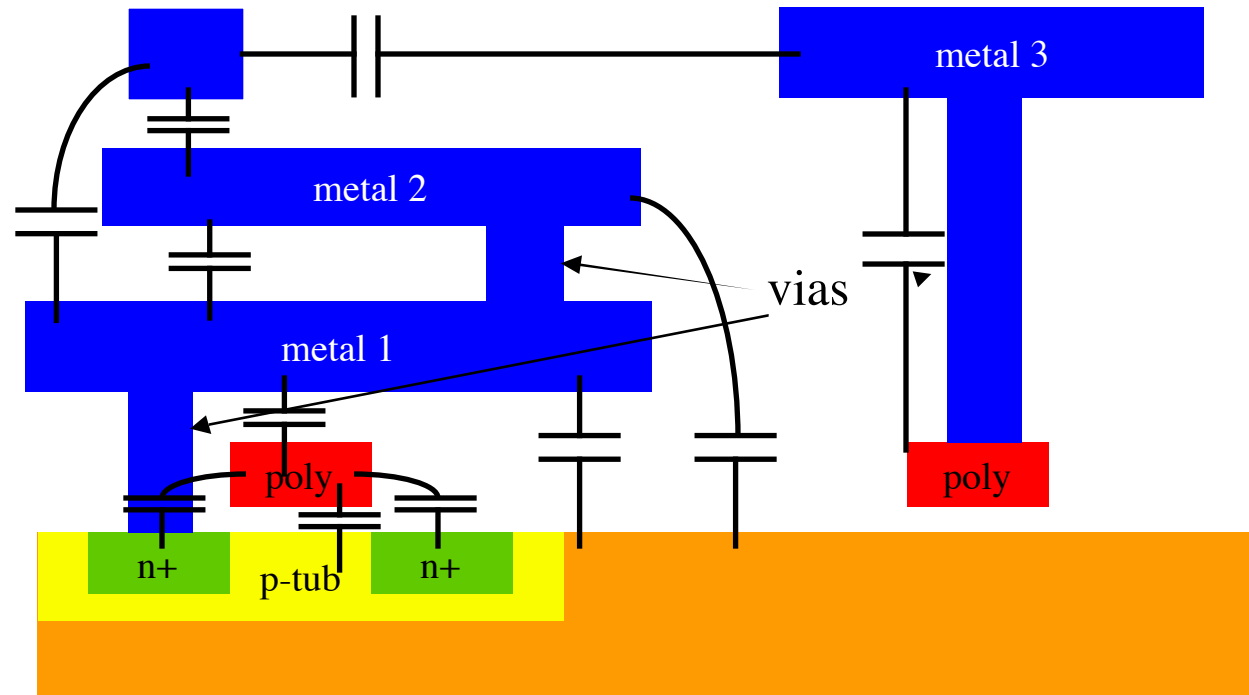

 
- On-chip wires run in multiple layers with no explicit return planes (ground is used as implicit return)
- Thus, almost all capacitance of on-chip wire is to *other wires* (same plane, different plane, etc.)
- Capacitance of MOSFET scales with V_{dd}





Metal Layers & Resistances

 

 - Resistance of conductor proportional to length/width, depends on material (resistivity), causes delay & loss
- Resistance of wire scales with square root of signaling frequency (at high speeds) (“skin effect”)
- Process scaling tends to increase resistance




Wire Resistance

  


- $R = \rho/l/A = \rho l/(wh)$ for rectangular wires (on-chip wires & vias, PCB traces)
- $R = \rho/l/A = \rho l/(\pi r^2)$ for circular wires (off-chip, off-PCB)

Material	Resistivity ρ ($\Omega\text{-m}$)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

 


Sheet Resistance

 

$R = \rho l / (wh) = l/w \cdot \rho/h$ for rectangular wires
Sheet resistance $R_{sq} = \rho/h$

Material	Sheet resistance R_{sq} (Ω/sq)
n, p well diffusion	1000 to 1500
n+, p+ diffusion	50 to 150
polysilicon	150 to 200
polysilicon with silicide	4 to 5
Aluminum	0.05 to 0.1

 

Wire Capacitance

Common wire cross-sections/permittivities:

$$C = \frac{2\pi\epsilon}{\log\left(\frac{s}{r}\right)}$$


$$C = \frac{2\pi\epsilon}{\log\left(\frac{r_o}{r_i}\right)}$$

$$C = \frac{2\pi\epsilon}{\log(2s/r)}$$

$$C = \frac{w\epsilon}{d} + \frac{2\pi\epsilon}{\log(2s/h)}$$

Material	ϵ_r
Air	1
Teflon	2
Polymide	3
SiO ₂	3.9
Glass-epoxy (PCB)	4
Alumina	10
Silicon	11.7

 - Permittivity $\epsilon = \epsilon_0\epsilon_r$
- Permittivity of free space $\epsilon_0 = 8.854 \times 10^{-12}$ F/m



Inductance

When conductors of transmission line are surrounded by uniform dielectric, capacitance & inductance are related:


$$CL = \epsilon\mu$$

Inductive effects can be ignored

- if the resistance of the wire is substantial enough (as is the case for long Al wires with small cross section)
- if rise & fall times of applied signals are slow enough

So ... inductance must be considered

 - for off-chip signals (even power/ground)
- for future even-higher-speed on-chip signalling




Wires & Models

Example Wires:

Type	W	R	C	L
On-chip	0.6 μm	150k Ω/m	200 pf/m	600 nH/m
PC Board	150 μm	5 Ω/m	100 pf/m	300 nH/m
24AWG pair	511 μm	0.08 Ω/m	40 pf/m	400 nH/m


In a situation, use a *model* of wires that captures the properties we need:

 - ideal, lumped L, R, or C
- LC, RC, RLC transmission line
- General LRCG transmission line



Appropriate choice of model
depends on signaling frequency


$$f_0 = \frac{R}{2\pi L}$$

 

General LRCG Model

Model an *infinitesimal* length of wire, dx , with lumped components

 L , R , C , and G
(inductance, resistance, capacitance, and conductance)



Drop across R and L

$$\frac{\partial V}{\partial x} = RI + L \frac{\partial I}{\partial t}$$


Current into C and G

$$\frac{\partial I}{\partial x} = GV + C \frac{\partial V}{\partial t}$$


$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG) \frac{\partial V}{\partial t} + LC \frac{\partial^2 V}{\partial t^2}$$

For $G=0$:
 
$$\frac{\partial^2 V}{\partial x^2} = RC \frac{\partial V}{\partial t} + LC \frac{\partial^2 V}{\partial t^2}$$



Impedance

 


$$Z_0 = \left(\frac{R + Ls}{G + Cs} \right)^{\frac{1}{2}} \quad s = 2\pi jf = j\omega \quad Z_0 = \left(\frac{L}{C} \right)^{\frac{1}{2}}$$


(typical assumption: $G = 0$)

At high frequency (LC lines)

 
- An infinite length of LRCG transmission line has *impedance* Z_0
- Driving a line *terminated* into Z_0 is same as driving Z_0
- In general, Z_0 is complex and frequency-dependent
- For LC lines (operating at “high” frequencies), Z_0 is real-valued and independent of frequency



Cut-off Frequency f_0

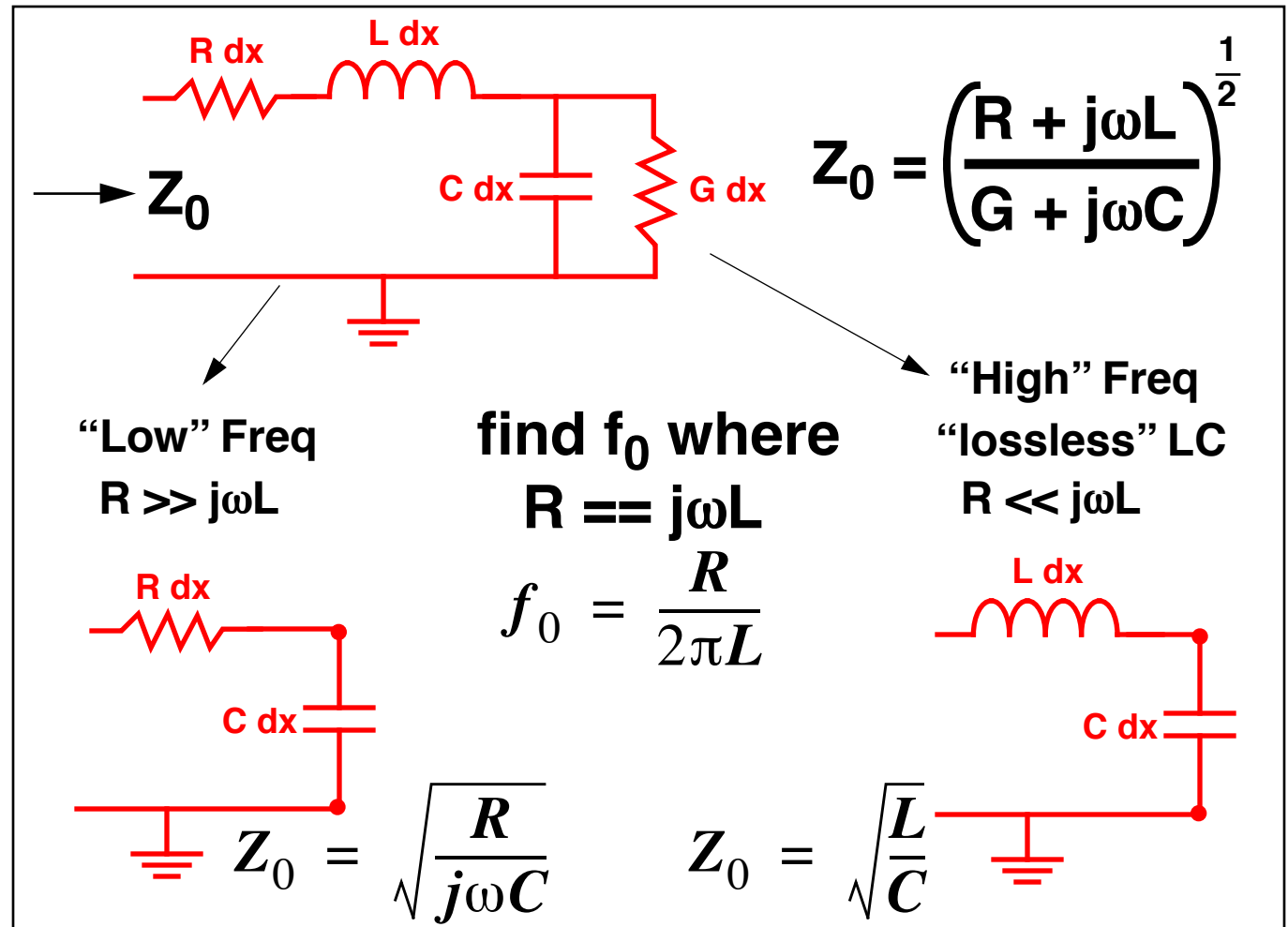

 - Transmission lines have characteristic frequency f_0
- Below $f_0 \approx RC$ model, Above $f_0 \approx LC$ model





Cut-off Frequency f_0

 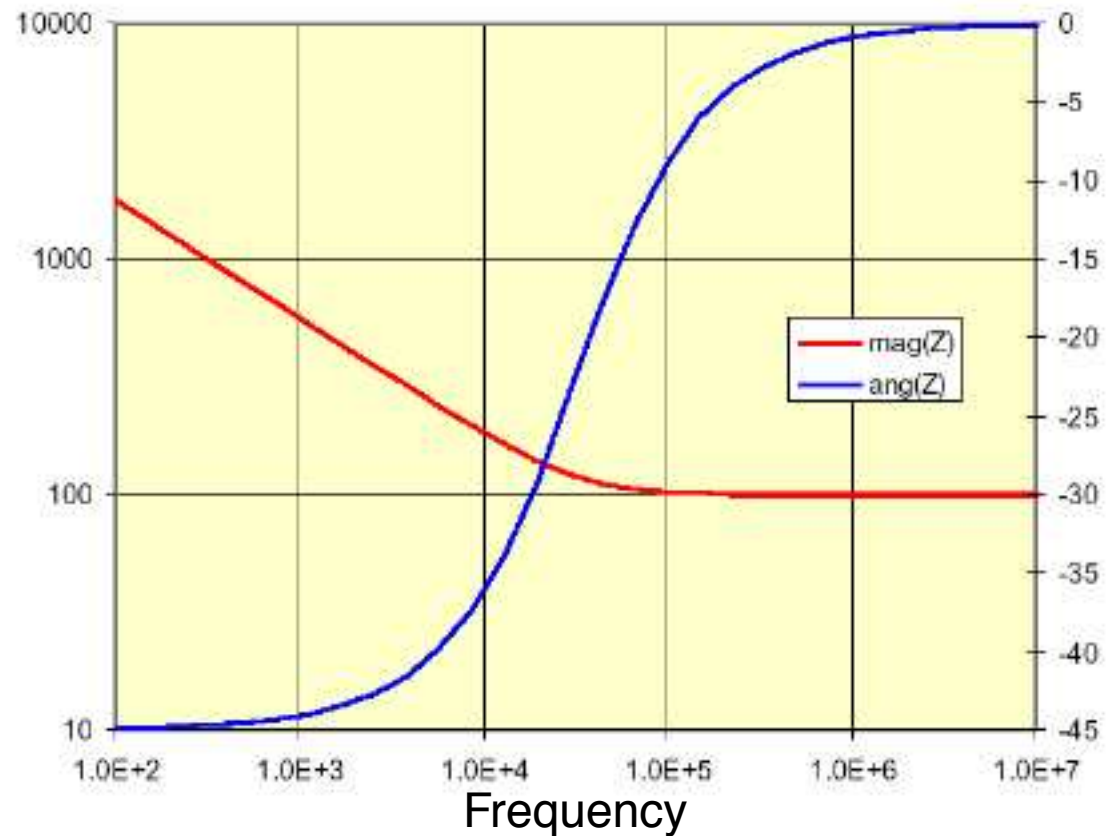
Example, 24AWG Pair

- $f_0 = 33\text{kHz}$
- Below f_0 , line is RC
- Above f_0 , line is LC

$$Z_0 = \left(\frac{.08 + 400 \times 10^{-9} \times 2\pi f j}{40 \times 10^{-9} \times 2\pi f j} \right)^{\frac{1}{2}}$$




Cut-off Frequency f_0 II

 

$$\begin{aligned}L &= 0.6 \text{ nH/mm} \\C &= 73 \text{ nF/mm} \\R_{\text{dc}} &= 120 \Omega / \text{mm} \\f_0 &= 32 \text{ GHz}\end{aligned}$$

~RC Model for on chip
interconnects

 


$$\begin{aligned}L &= 0.5 \text{ nH/mm} \\C &= 104 \text{ fF/mm} \\R_{\text{dc}} &= 0.008 \Omega / \text{mm} \\f_0 &= 2.5 \text{ MHz}\end{aligned}$$

~LC Model for PC Board
traces

$$Z_0 = \left(\frac{L}{C} \right)^{\frac{1}{2}} = \left(\frac{0.5 \text{ nH}}{0.1 \text{ pF}} \right)^{\frac{1}{2}} \approx 70 \Omega$$

1 mil = 0.001 inch

Example from Poulton 1999 ISSCC Tutorial

 

RC Lines (low frequency)

$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG)\frac{\partial V}{\partial t} + LC\frac{\partial^2 V}{\partial t^2}$$

$R \gg j\omega L$, governed by diffusion equation:

$$\frac{\partial^2 V}{\partial x^2} = RC\frac{\partial V}{\partial t}$$

Signal diffuses down line, disperses:

**R increases w/ length d
C increases with d**



**Delay & rise time both
increase with RC,
thus with d^2**

For a typical wire:

$$R = 150\text{K}\Omega/\text{m}$$

$$C = 200\text{pF}/\text{m}$$
  
$$\tau = RC = 30\ \mu\text{s}/\text{m}^2 \\ = 30\ \text{ps}/\text{mm}^2$$




LC Lines (high frequency)

$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG)\frac{\partial V}{\partial t} + LC\frac{\partial^2 V}{\partial t^2}$$


$R \ll j\omega L$, governed by wave equation:

$$\frac{\partial^2 V}{\partial x^2} = LC\frac{\partial^2 V}{\partial t^2} \quad V_i(x, t) = \left(\frac{Z_0}{Z_0 + R_S}\right) V_S\left(t - \frac{x}{v}\right)$$

 Waveform on line is superposition of forward- and reverse-traveling waves:



 - Waves travel with velocity $v = (LC)^{-1/2}$
- What happens when the wave gets to the end of line?




RLC/G Lines (general case)

$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG)\frac{\partial V}{\partial t} + LC\frac{\partial^2 V}{\partial t^2}$$


Ignoring G, wave propagation equation:

$$\frac{\partial^2 V}{\partial x^2} = RC\frac{\partial V}{\partial t} + LC\frac{\partial^2 V}{\partial t^2}$$

 Lossy transmission line, dispersive waves:




 Substrate-doping-dependent dispersion of a picosecond-scale pulse in propagation of an on-chip transmission line




RC vs. RLC

 Output response of inverter with step input:




 In reality, we have a non-zero inductance in series with the RC circuit. (Inductors and capacitors both “have memory”)




RC vs. RLC

 Output response of inverter with step input:




Result: slower response time, ringing

 

Impedance and Reflections

Terminating a Transmission Line:

 


Telegrapher's Equations:

$$k_r = \frac{I_r}{I_i} = \frac{V_r}{V_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$$


Reflection coefficient k_r may be complex for complex impedances Z_T – i.e., the reflected wave may be phase-shifted from the incident wave.

 For real-valued Z_T the reflection coefficient is real, and the phase shift is either 0 (k_r positive) or π (k_r negative).





Impedance and Reflections


 
$$k_r = \frac{I_r}{I_i} = \frac{V_r}{V_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$$





Matched Termination, $k_r = 0$

  



Open-Circuit Termination, $k_r = 1$

  


Short-Circuit Termination, $k_r = -1$

  

Impedance and Reflections

  

Impedance and Reflections

 


$$V_i = \left(\frac{Z_0}{Z_0 + R_S} \right) V_S = \left(\frac{50}{50 + 400} \right) 1V = 0.111V$$


$$k_{rR} = \frac{Z_T - Z_0}{Z_T + Z_0} = \frac{1000 - 50}{1000 + 50} = 0.905$$

$$k_{rS} = \frac{Z_T - Z_0}{Z_T + Z_0} = \frac{400 - 50}{400 + 50} = 0.778$$

 
**Values are typical for 8-mA CMOS driver
with 1kΩ pullup**






Impedance and Reflections

 


	Vwave	Vline	time t
Vi1	0.111	0.111	0
Vr1	0.101	0.212	5
Vi2	0.078	0.290	10
Vr2	0.071	0.361	15
Vi3	0.055	0.416	20
Vr3	0.050	0.465	25
Vi4	0.039	0.504	30
Vr4	0.035	0.539	35
Vi5	0.027	0.566	40

 

Impedance and Reflections

 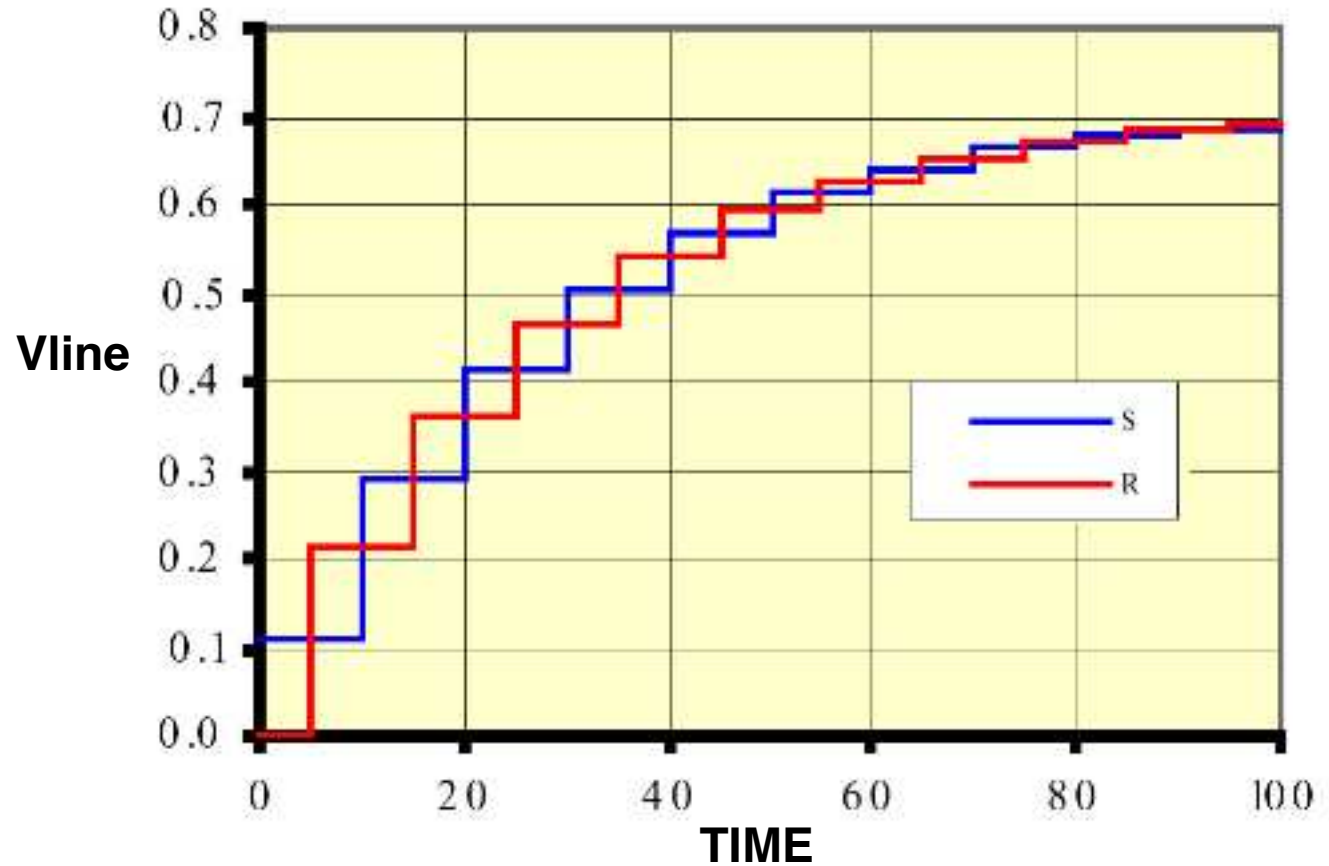 

Reflections, $Z_S < Z_0$

 

$$Z_S = 25 \Omega$$

$$Z_0 = 50 \Omega$$


$$Z_L = \text{inf } \Omega$$

$$V_I = 0\text{v} \rightarrow 2\text{v}$$

$$V_S = V_I \frac{Z_S}{Z_S + Z_0} = 2 * \frac{50}{25 + 50} = 1.3333 \text{ V}$$

$$k_r (\text{load}) = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\text{inf} - 50}{\text{inf} + 50} = 1$$



 
$$k_r (\text{source}) = \frac{Z_S - Z_0}{Z_S + Z_0} = \frac{25 - 50}{25 + 50} = -0.3333$$



Reflections, $Z_S < Z_0$



$$k_r(\text{load}) = 1$$

$$k_r(\text{source}) = -0.3333$$

   


Reflections, $Z_S < Z_0$

Volts

 
 


Add In Capacitance ...

 


What if we throw in a capacitor (i.e., reality?)

  
Simple case: matched impedance at source end





Impedance and Reflections

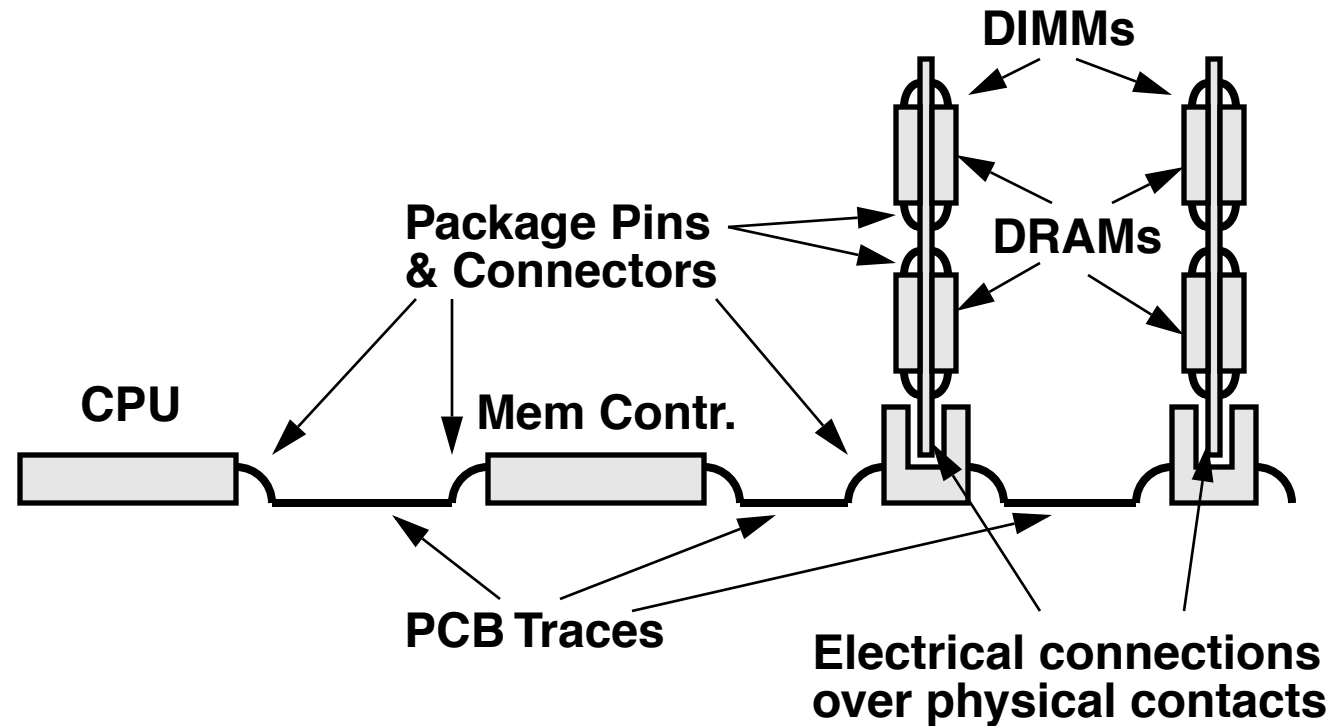

 
**Modern systems have MANY, MANY, MANY
potential sources of impedance-mismatch
and/or reflections**





Multidrop Bus I

  

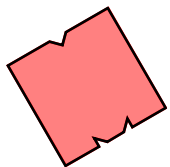
Each impedance discontinuity is a reflective interface




Multidrop Bus II

 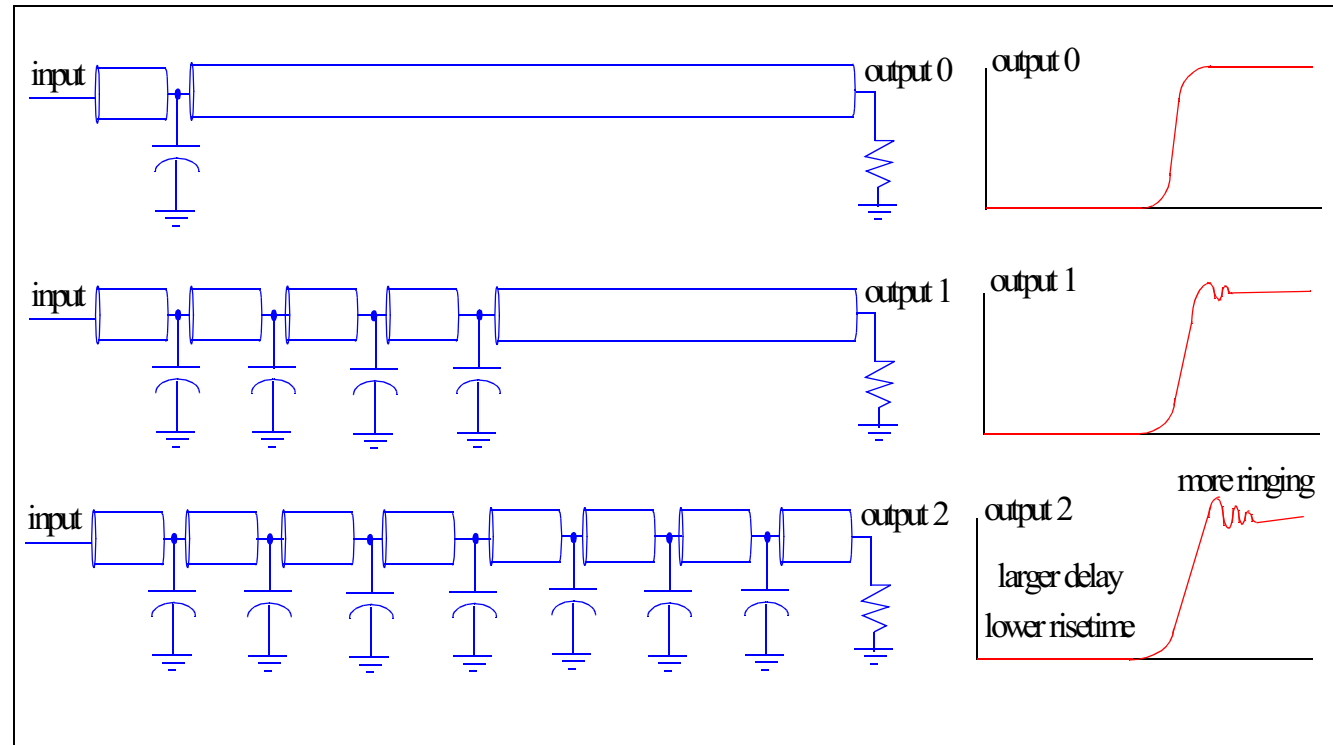


Capacitive Termination I

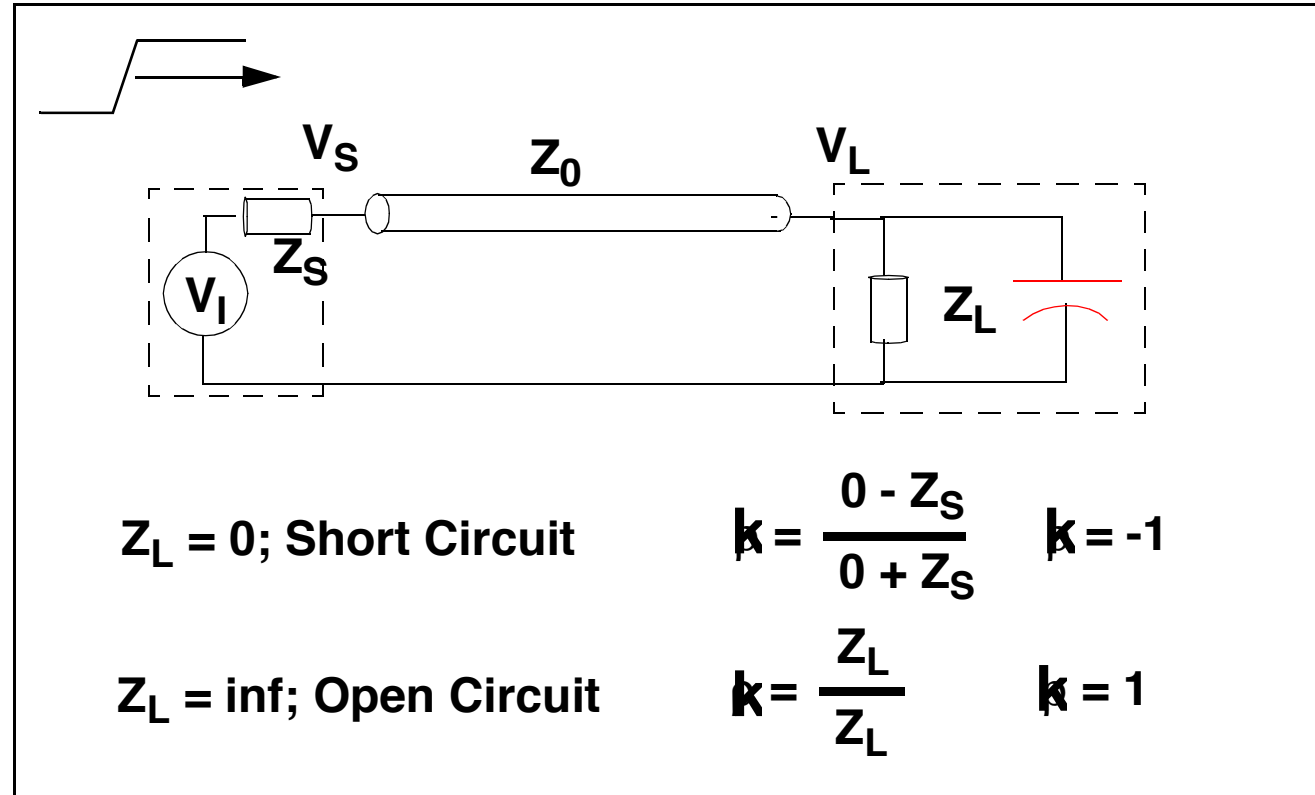

 
- Capacitors behave like short circuit when not charged. Once charged, behaves like open circuit.




Capacitive Termination II

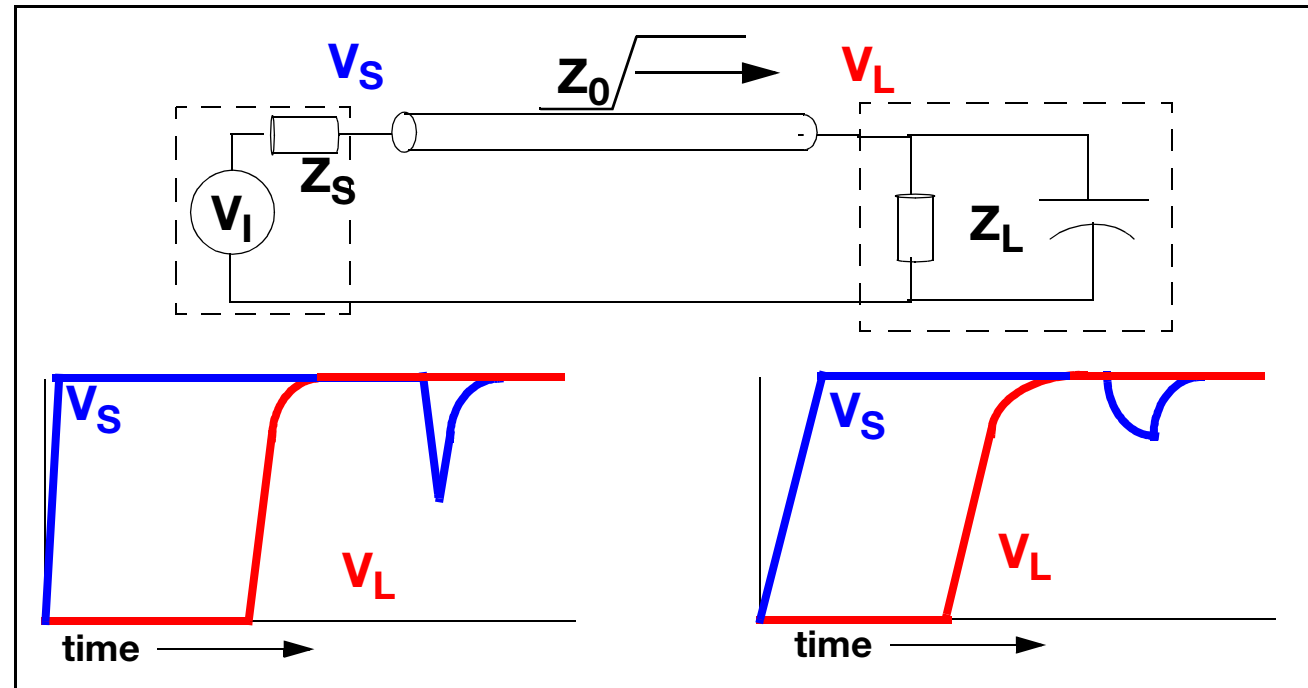

 
- When “shorted”, V_S is reflected with the same magnitude back toward source.
- The “magnitude” here is the “magnitude” of rise time.
- To minimize glitch, limit slew rate.




What is a Stub?

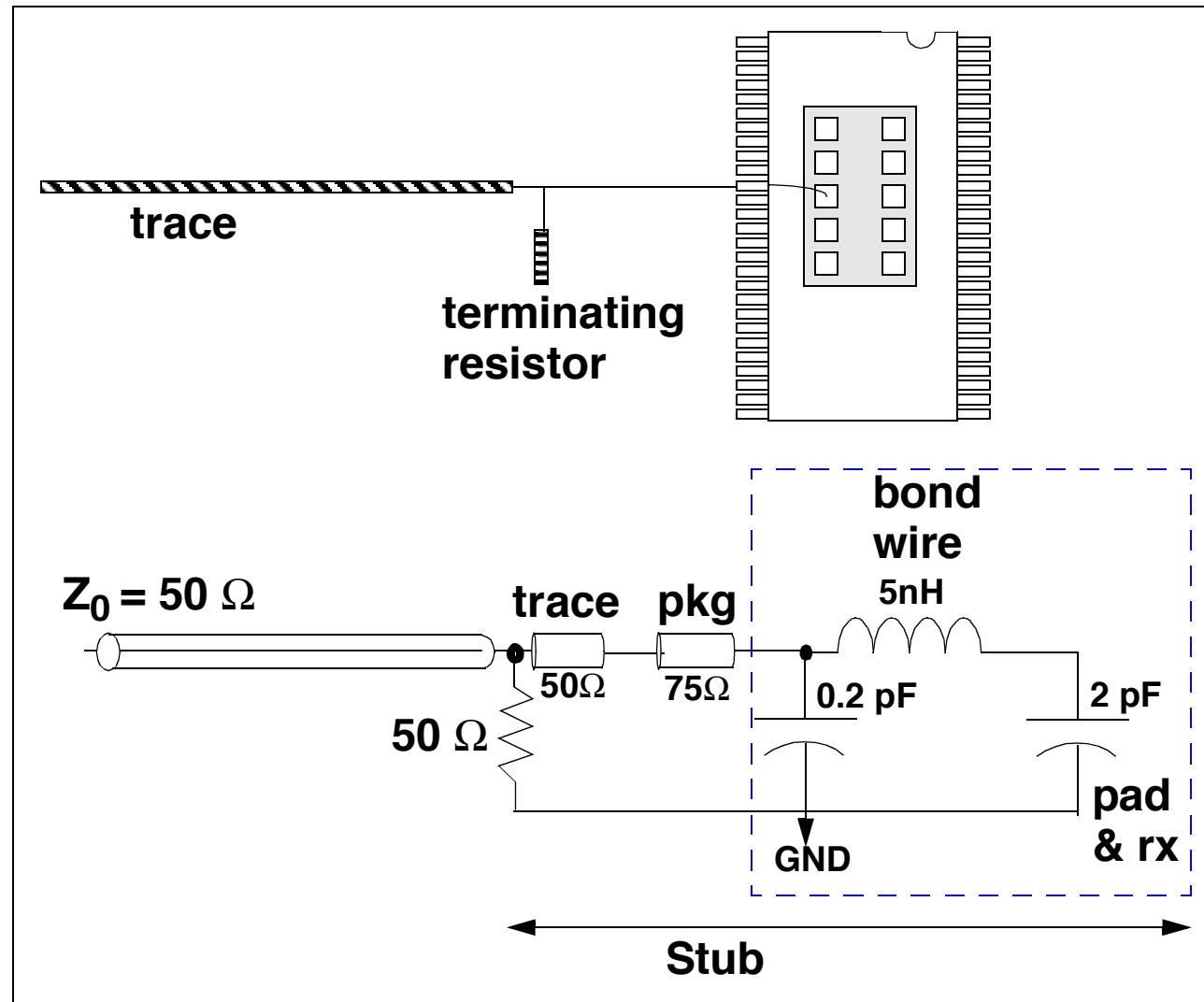

 
- Signal path inside of package also significant




Series Stub Terminated Logic

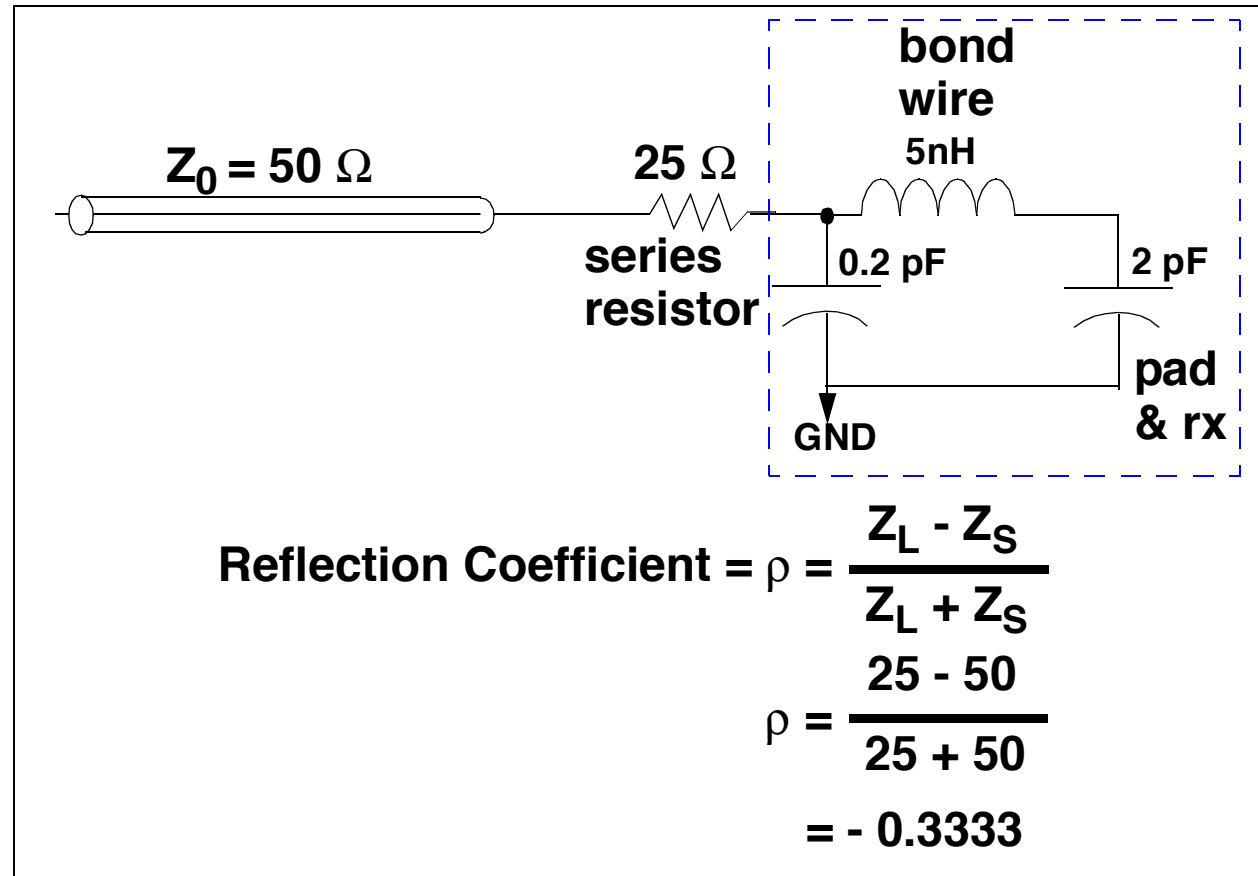

 
- Series resistor isolates stub from line
- reduces ringing
- reduces power




Rambus Signalling

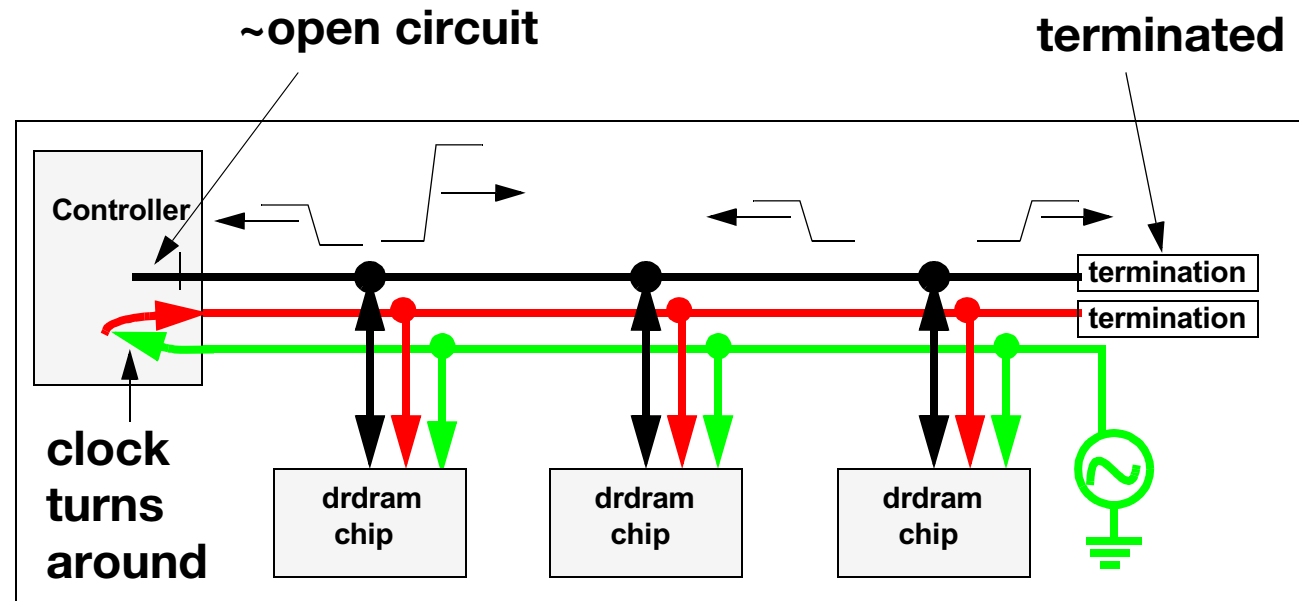

 
- **Current mode**
- **Controller sends full height signal swings**
- **DRAM chips send half height signal swings**
- **Reflection off of controller driver creates full height signal swing**
- **Current control and voltage slewrate control**




Rambus Channel - 16 bit

 

 
- RIMM #3 dropped from spec to solve signalling problems
- Need Continuity RIMM




Rambus Channel - 32/64 bit

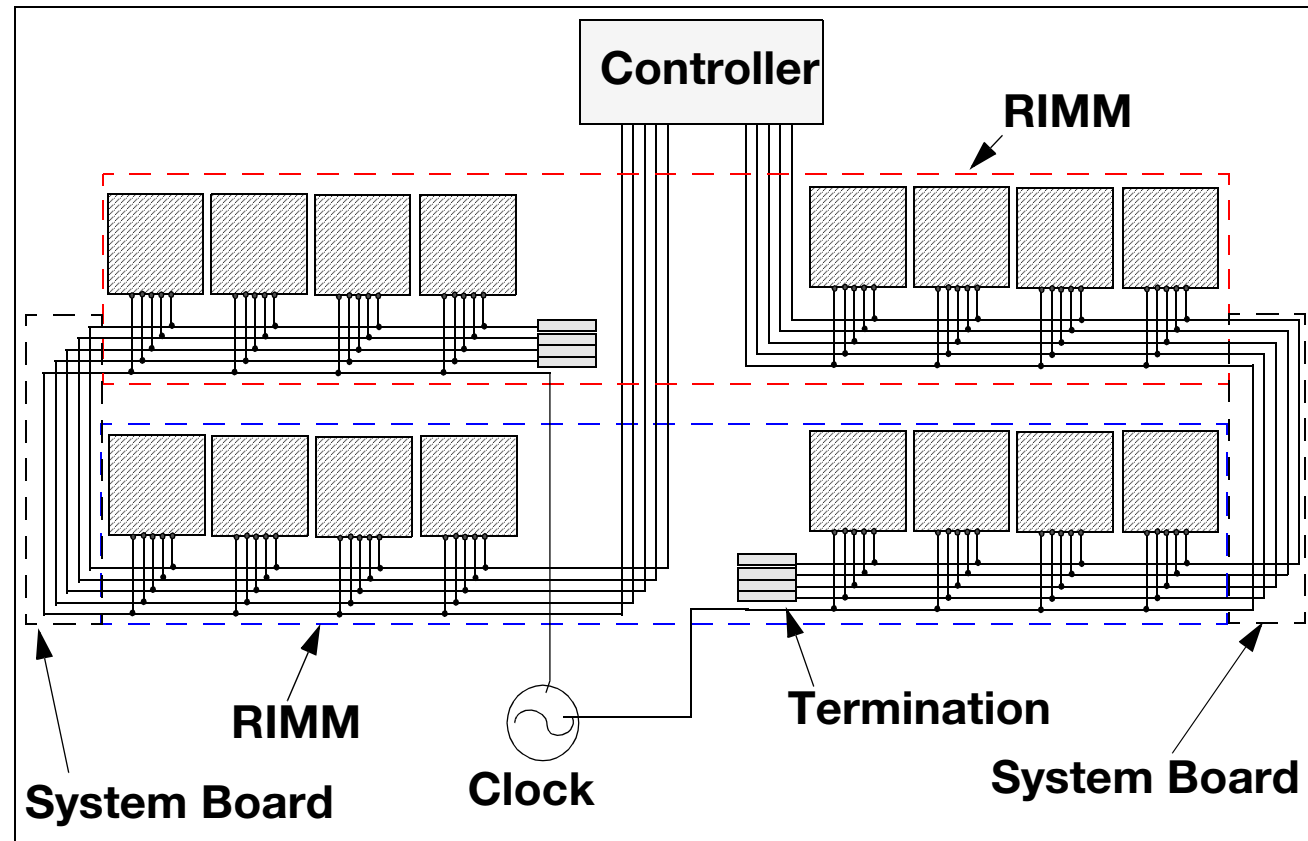

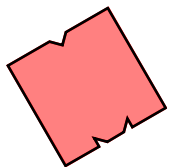
- Termination brought onto RIMM
- Connector interface count reduced from 4 to 3
- No need for special terminated RIMM and non-terminated RIMM





ODT: On Die Termination

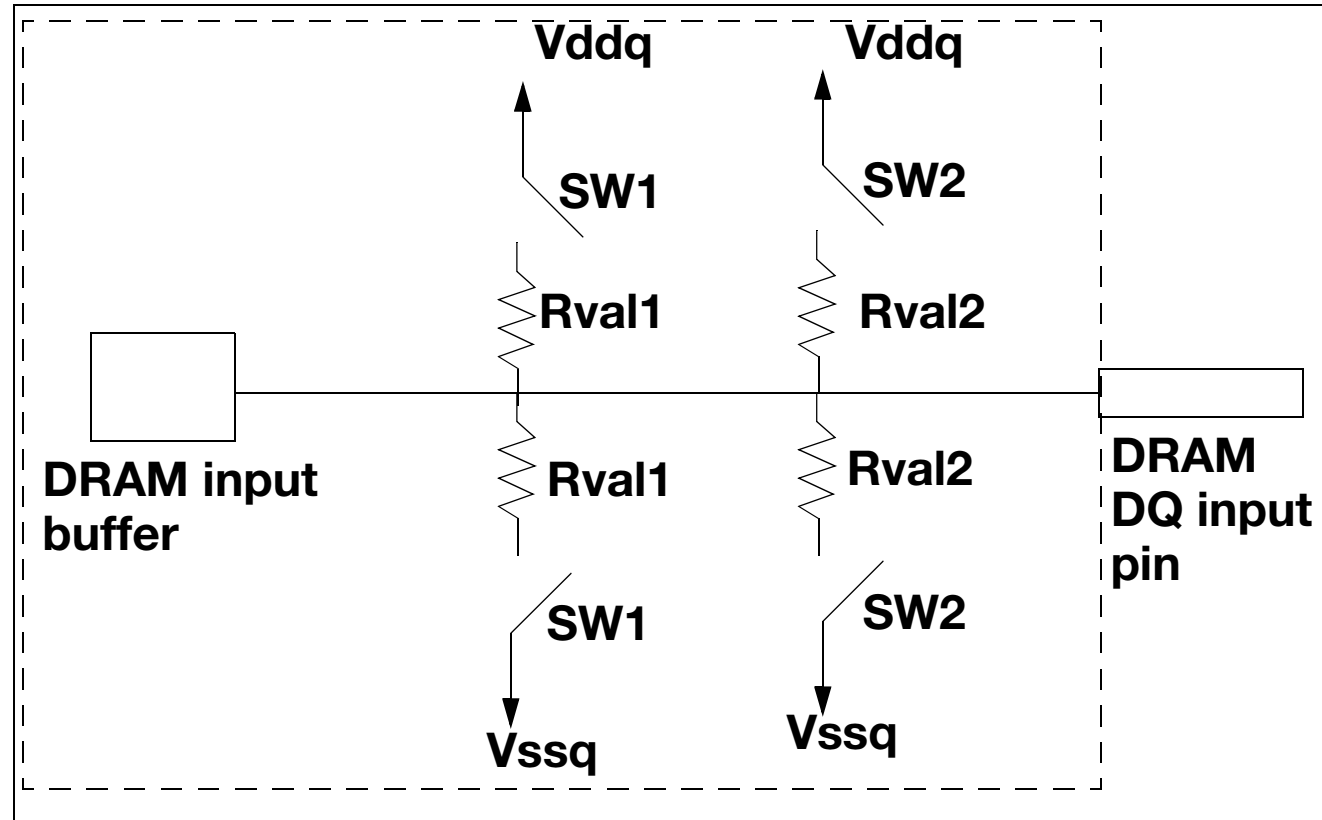



 
- Active, dynamic termination, depending on R/W, and number of loads on electrical bus
- Can be turned on/off in 2 cycles, off in 2.5 cycles
- Designed into DDR II




Input Buffering - References I

  


Simple Inverter

   


Input Buffering - References II

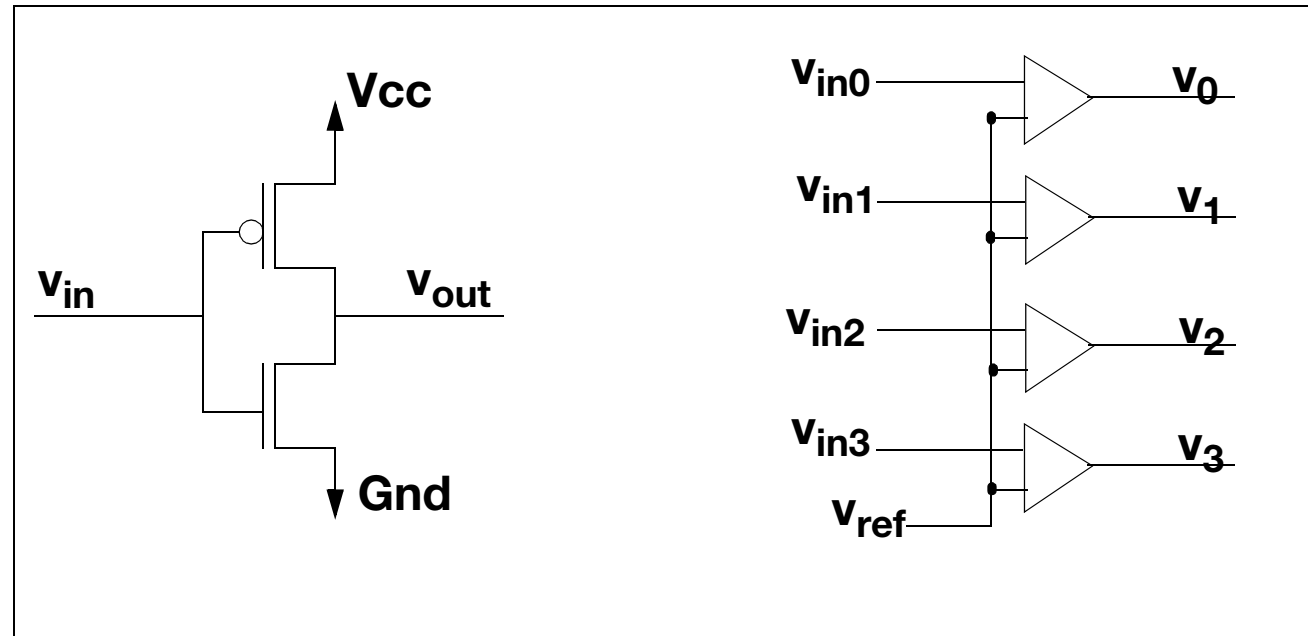

 
- Inverters aren't very good for high frequency signalling
- Local or remote reference?



Differential Signalling


 


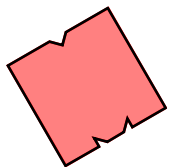- **Send the signal and its complement**
- **The complement signal path is the current return path**
- **Signal pairs must be routed closely together**
- **Signalling scheme can reject common mode noise quite well**





Inductive Noise

$L \, di/dt$ noise (ground bounce):

 
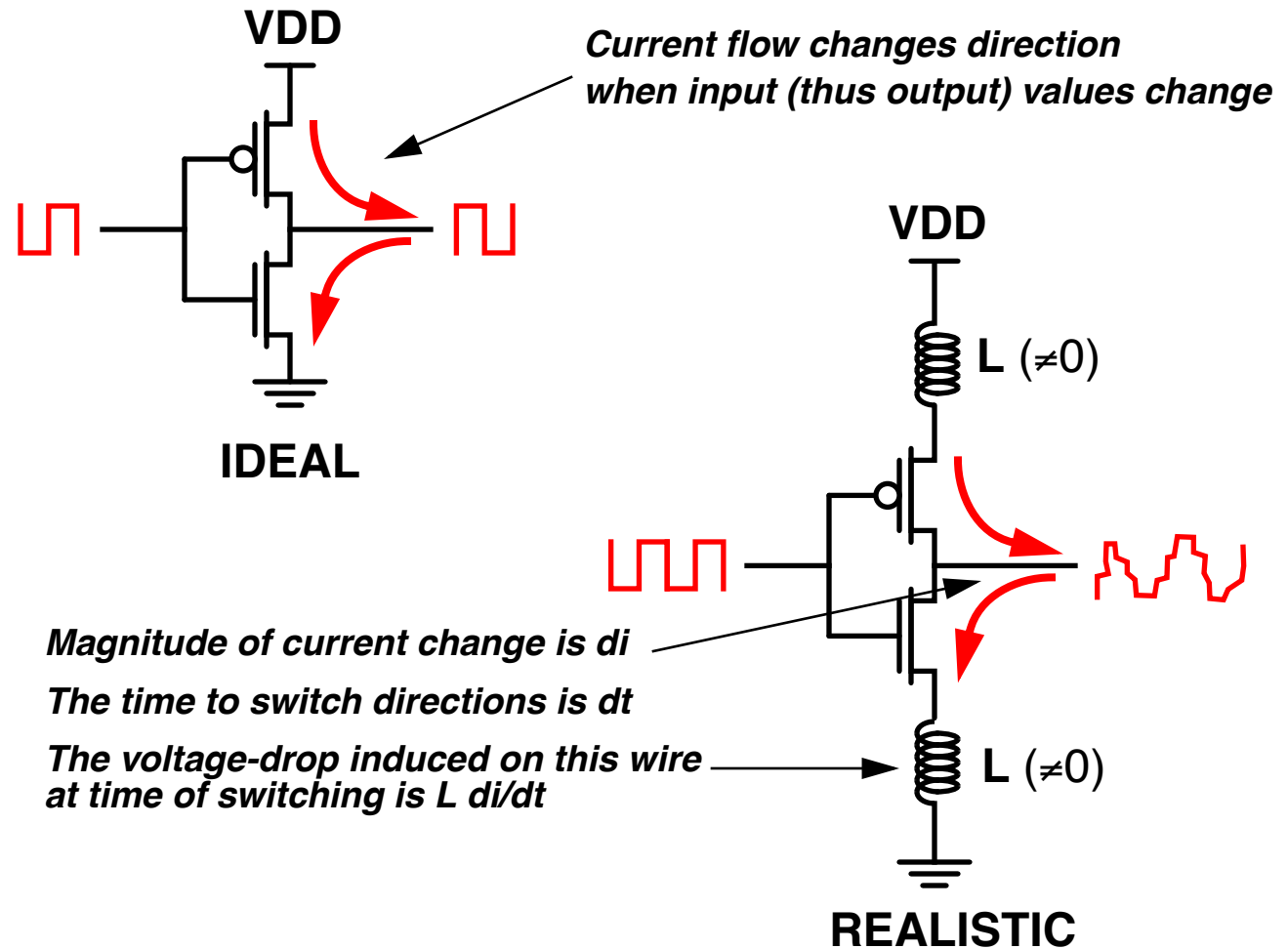


Inductive Noise


$L \, di/dt$ noise (ground bounce):

 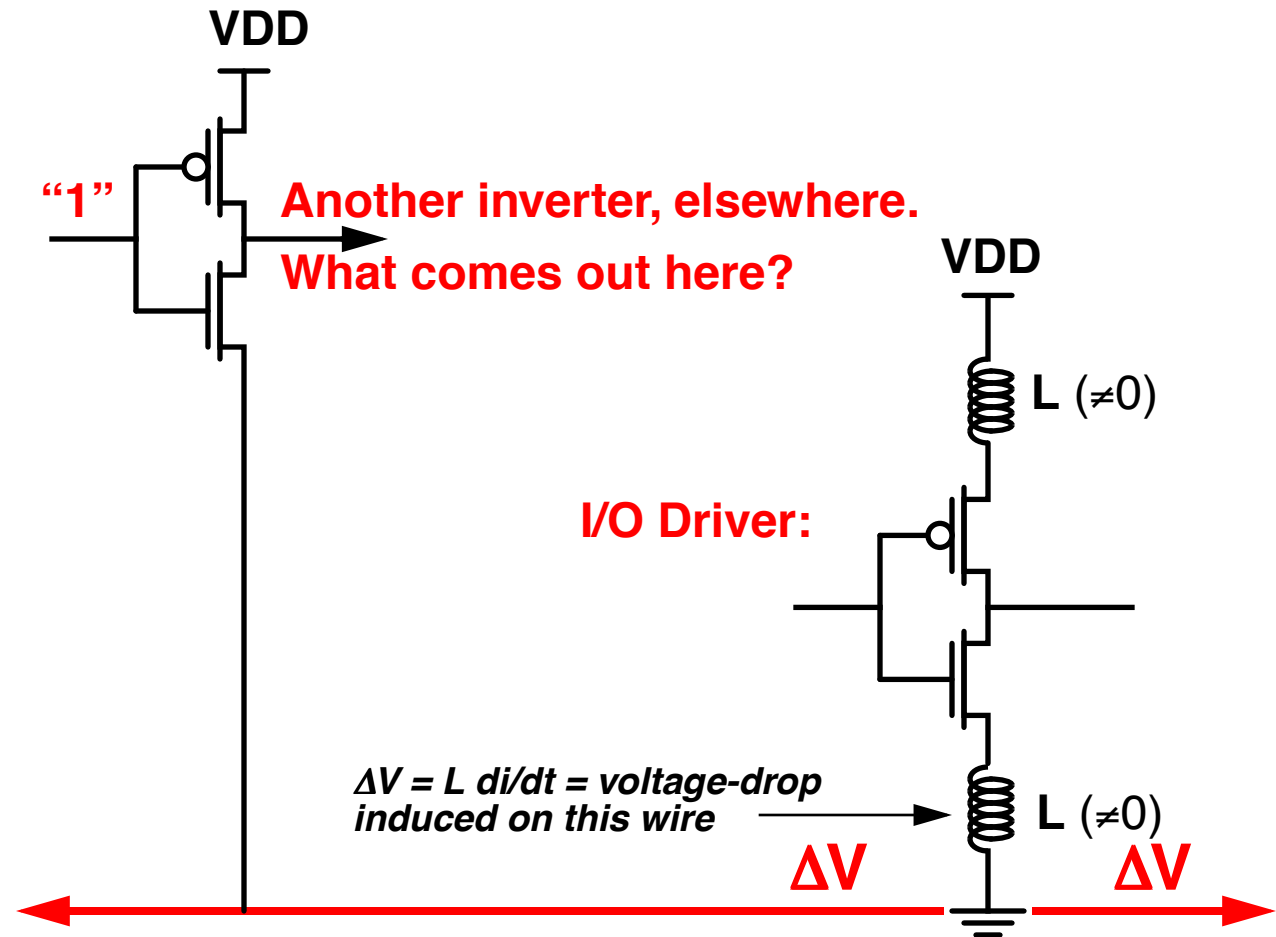


Real vs Ideal World

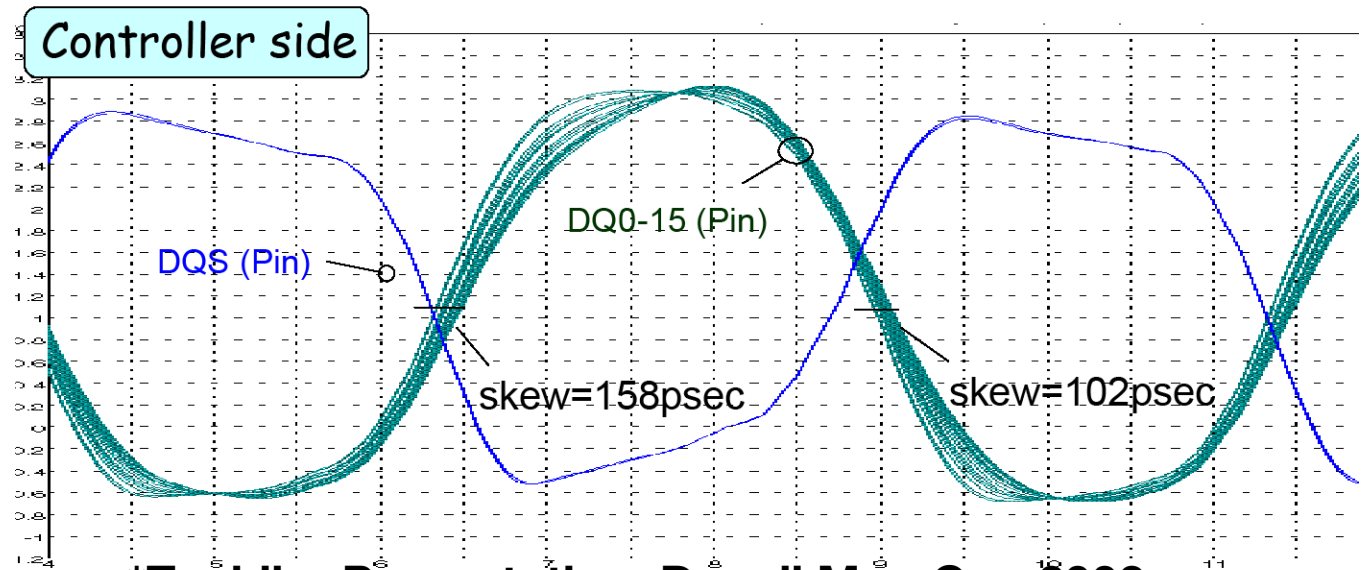 

 ***Toshiba Presentation, Denali MemCon 2002**




A Signaling System



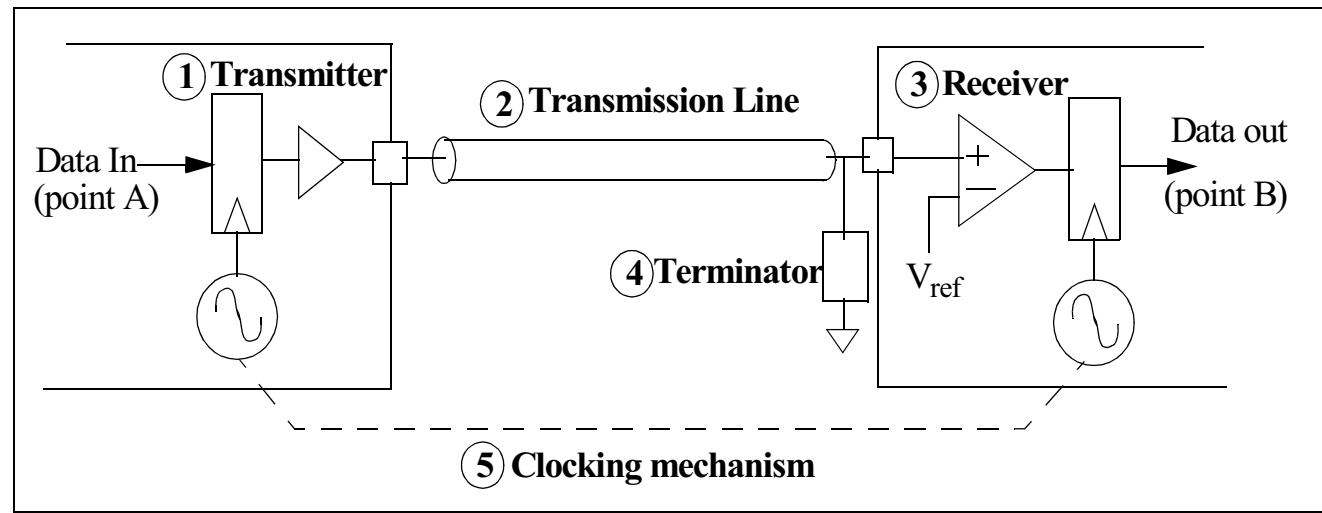


- 1. Transmitter: Encodes data as current/voltage level onto the line**
- 2. Transmission Line: Deliver data from transmitter to receiver**
- 3. Receiver: Compare against reference to extract data**
- 4. Terminator: Remove signal from line, once they're received**
- 5. Clock: Tells transmitter when to send, receiver when to sample signal**


* Poulton ISSCC 1999 Signaling Tutorial

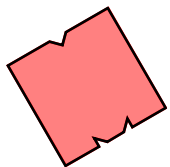


Timing Budget Visualized

  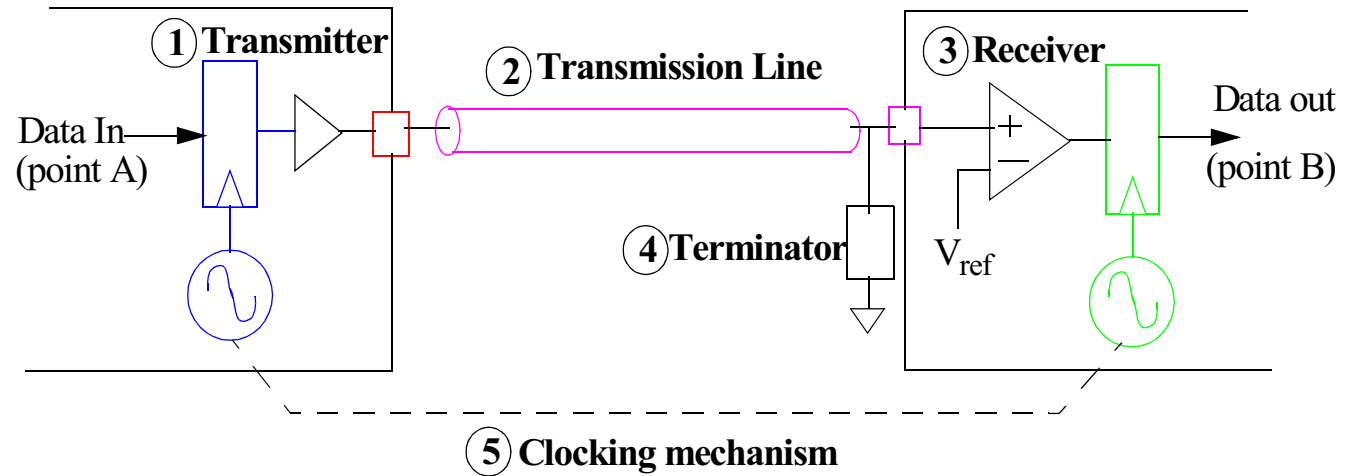



Definitions: *Skew*

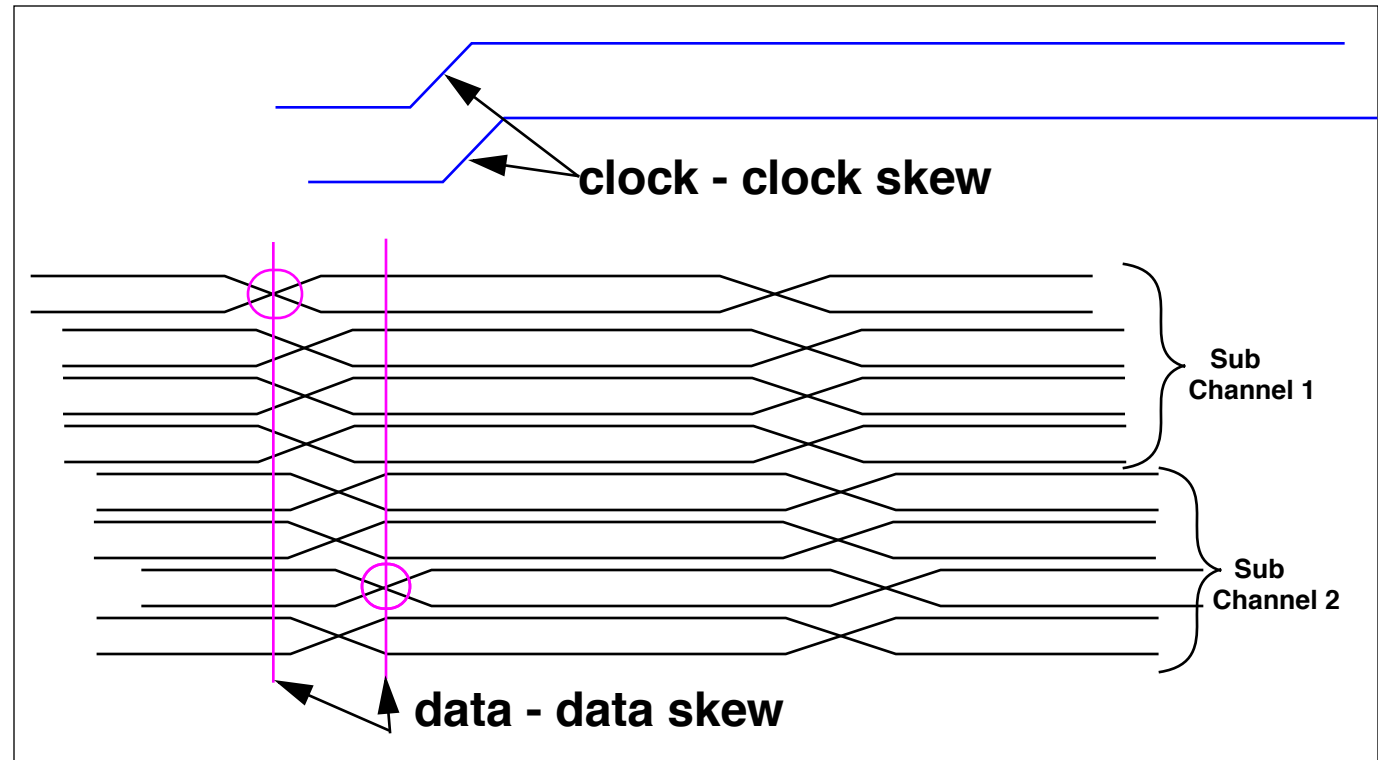

 
- **Static timing displacement from ideal design**
- **Caused by differences in signal path characteristics**
- **Total timing budget must take data-data skew, data-clock skew as well as clock-clock skew into cycle budget consideration**




Path Length Differential

 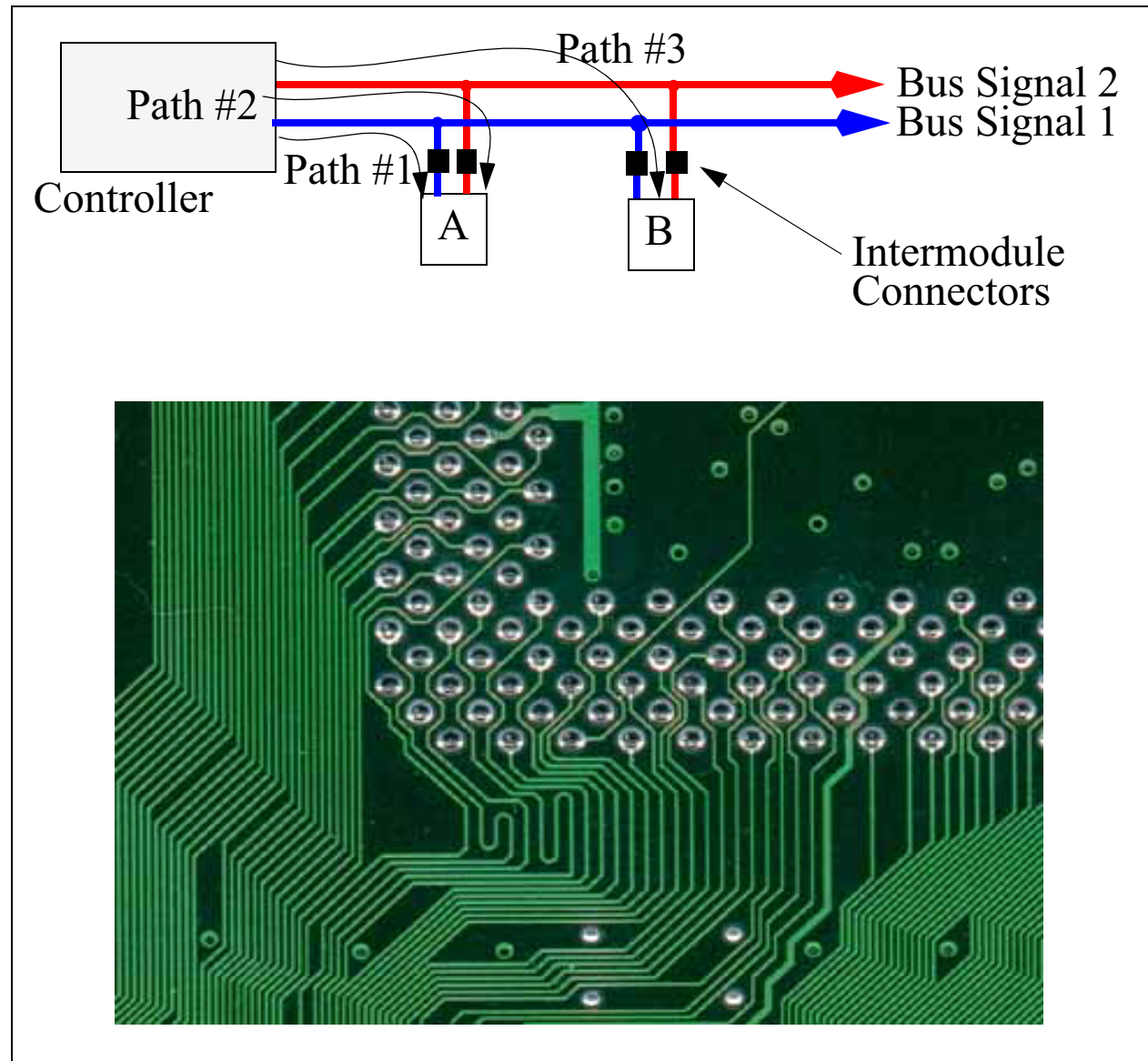


Definitions: *Jitter*

 

 
- **Dynamic timing displacement from nominal timing characteristics**
- **Magnitude and offset of timing displacement could depend on: previous signal state(s), current signal state(s), supply voltage level(s), crosstalk, variations in thermal characteristics. Perhaps even phases of the moon (not proven).**




Uncertainty == Bad

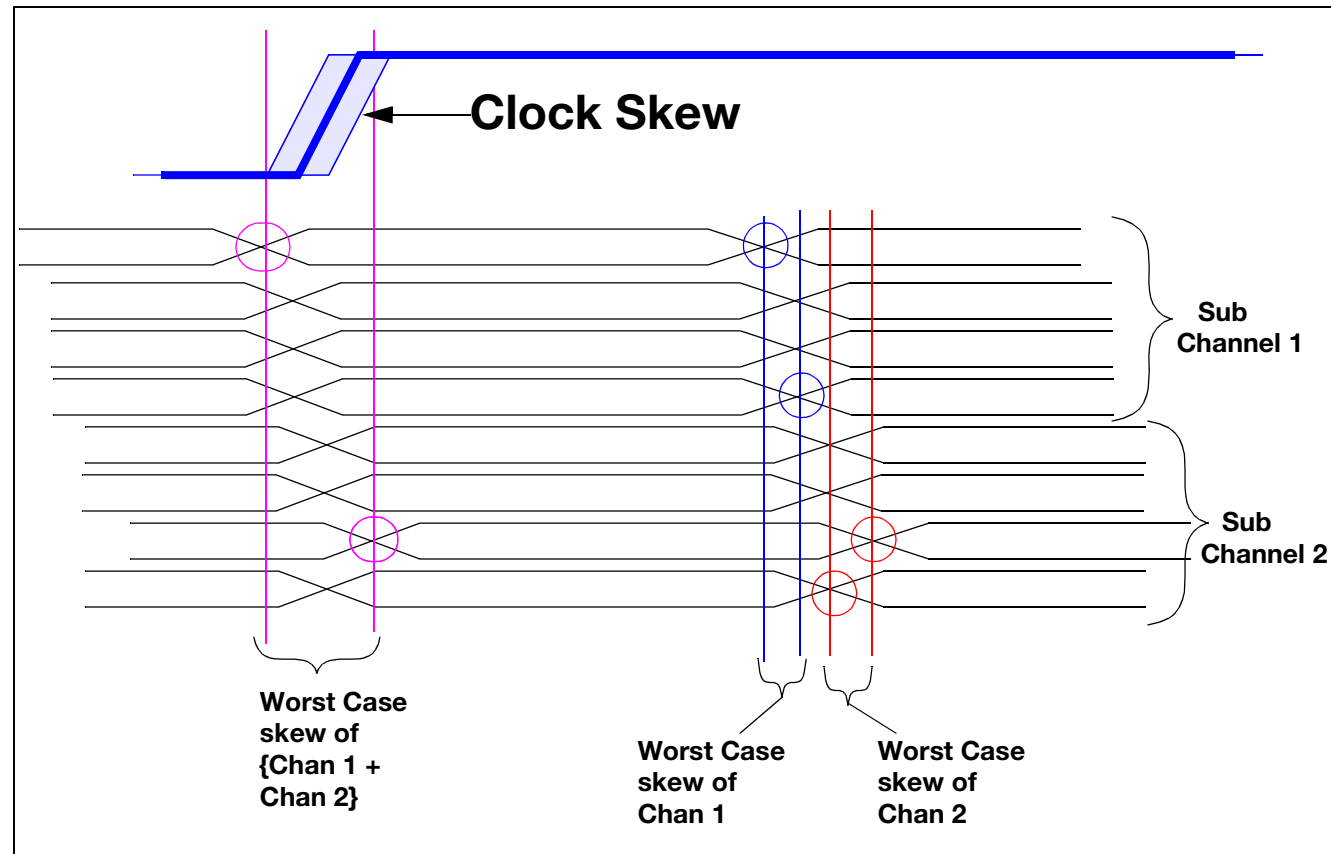

 
Worst case skew must be considered in system timing




Global Clock I

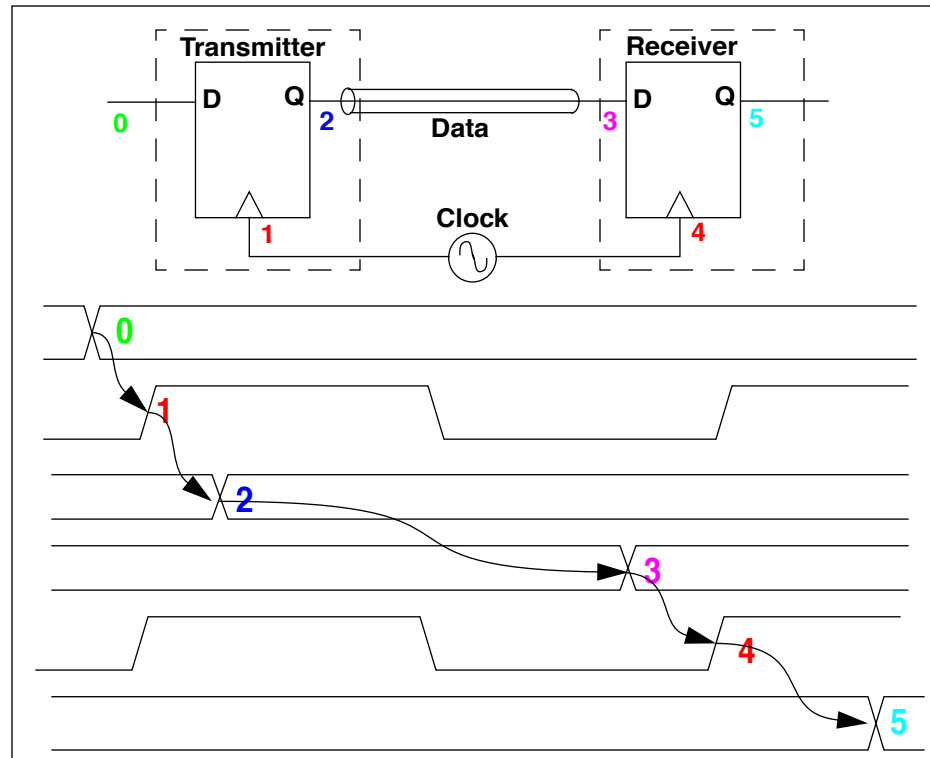

 
- 0:** Assume data is stable for setup time before clock edge
- 1:** Rising edge of transmitter clock
- 2:** Transmitter begins to drive data (perhaps through logic)
- 3:** Signal reaches input of receiver.
- 4:** Rising edge of receiver clock
- 5:** Receiver latches data and drives internal signal lines




Global Clock II: Parallel Data

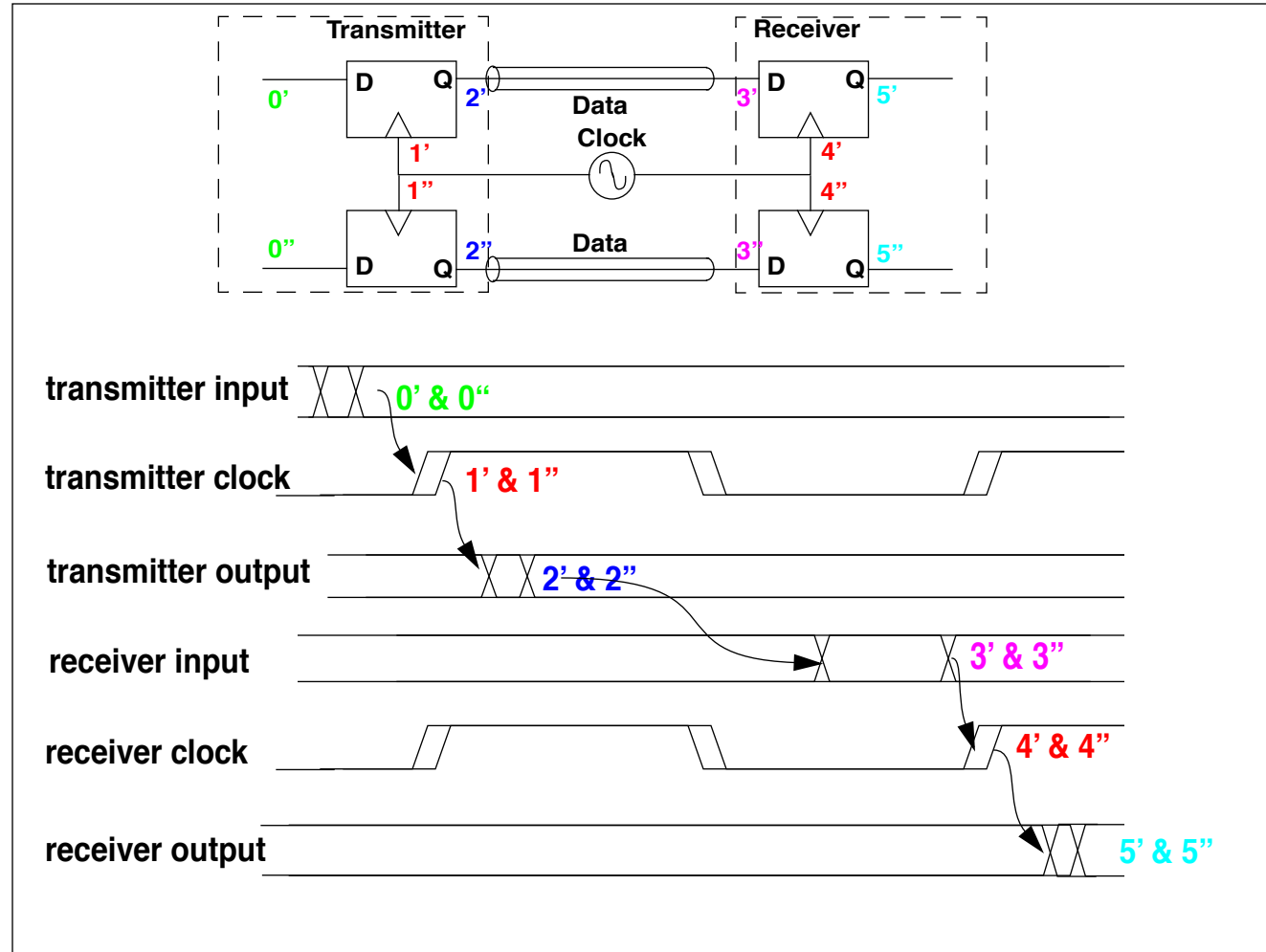

 
- Skew and jitter eats into timing budget
- Luckily, uncertainty does not accumulate beyond latches



What Needs To Be Done?


 


By the way: “global” clock scheme

 



Background: Elmore Delays

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

 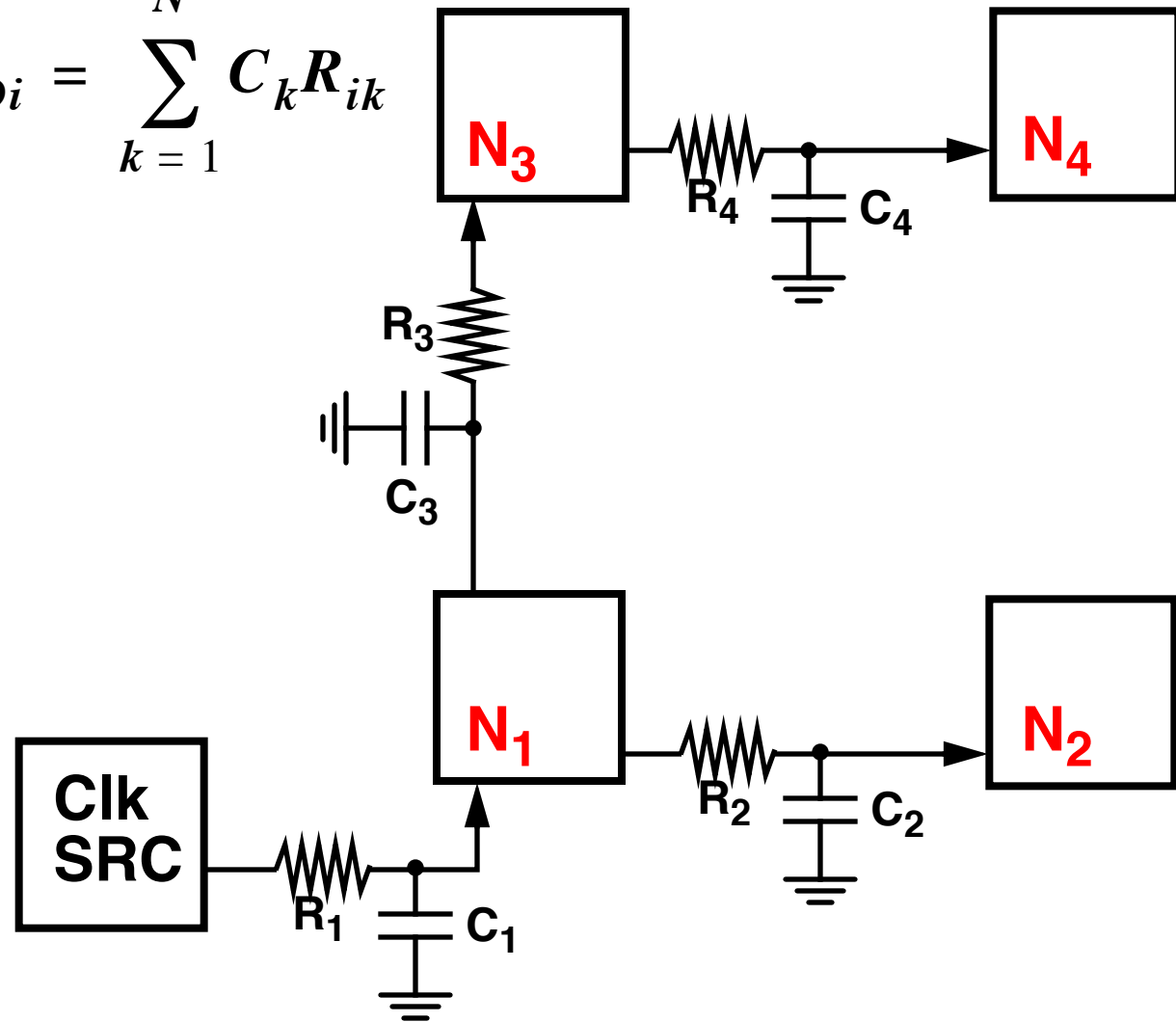


Background: Elmore Delays


$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

 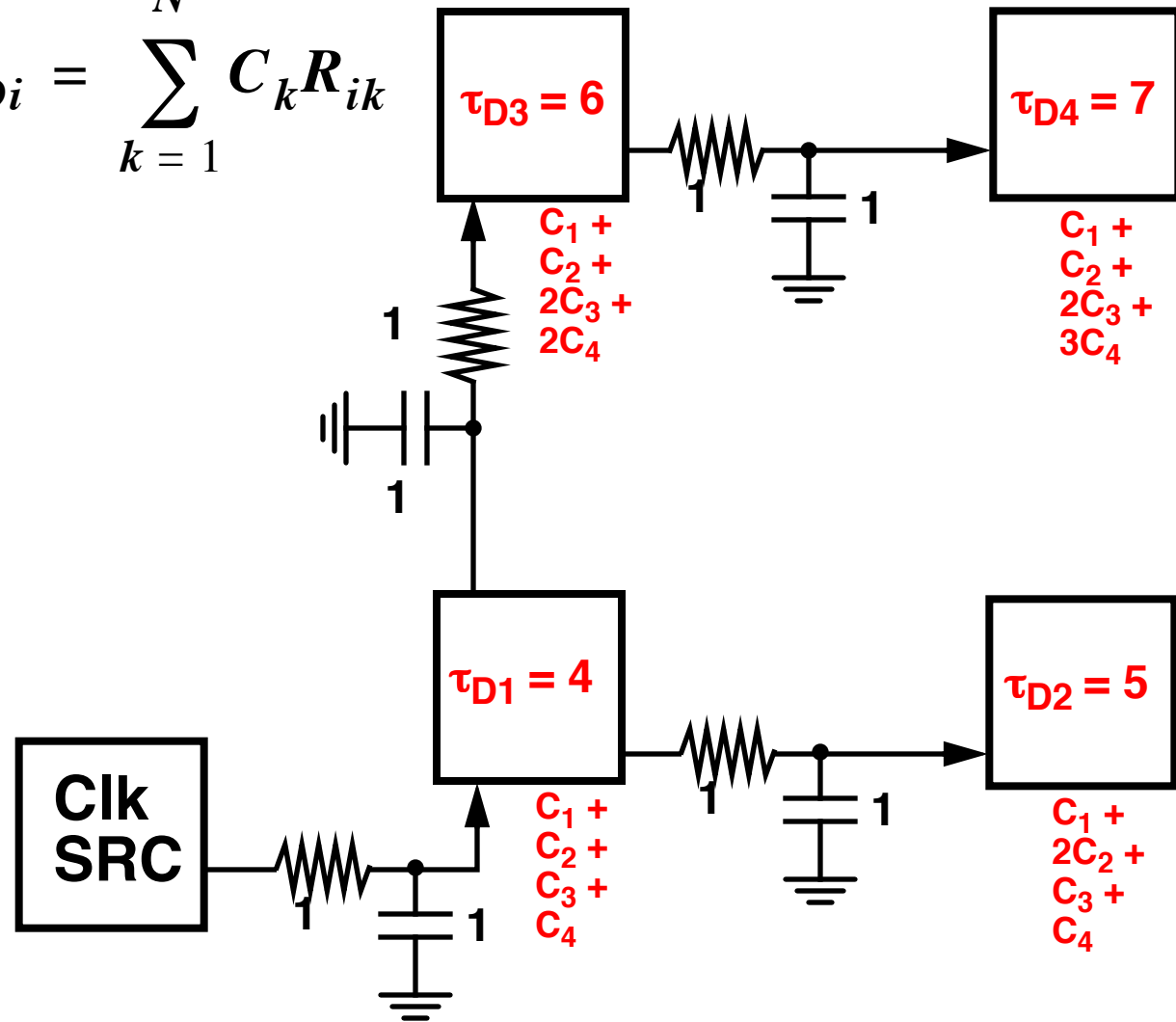


End Result: *Clock Skew*

 

 In general, even nearby clocks **not** in synch




Clock Tree I

 


**Clock distribution
is a *major*
design problem!**

 
- **Every branch sees same wire length and capacitance**
- **The clock skew is theoretically zero**
- **The sub-blocks should be small enough s.t. the skew within the block is tolerable**
- **Essential to consider clock distribution *early* in the design process**




Clock Tree I

 


An on-chip clock tree

 


Clock Tree II (I with buffers)

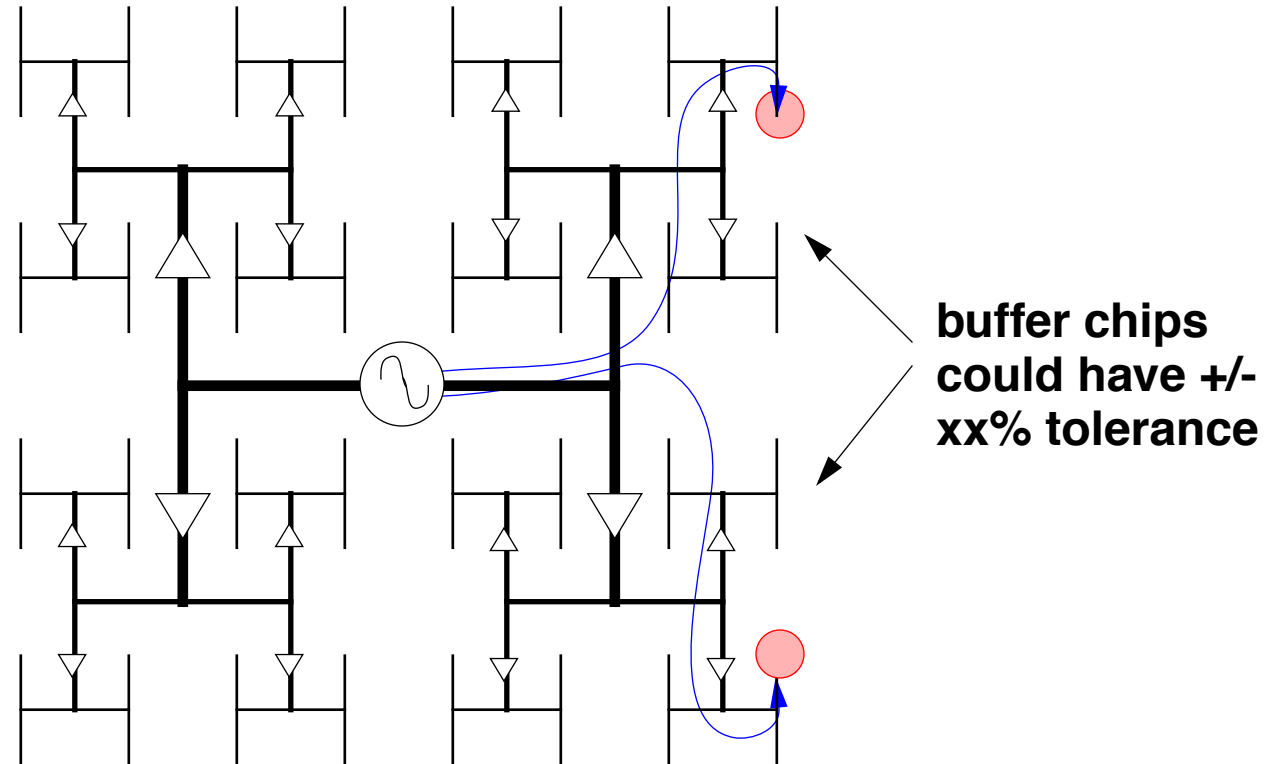

 - Large synchronous systems require all components (chips or registers) to be driven by clock signal.
- Clock signal paths and buffers could introduce both skew and jitter at each stage
- Jitter and skew are additive with larger systems. More buffering, more skew and jitter.



DEC Alpha 21164

 

9.3 M Transistors, 4 metal layers, 0.55 μ m


Clock Freq: 300 MHz

Clock Load: 3.75 nF



Power in Clock = 20W (out of 50W)

Two Level Clock Distribution:

 
- **Single 6-stage driver at center**
 - **Secondary buffers drive left and right side**
- Max clock skew less than 100psec**
- **Routing the clock in the opposite direction**
 - **Proper timing**




Clock Skew in Alpha

  


Phase Locked Loop

 

 - Given a data signal, recover the frequency and phase of the data signal, generate local reference clock ϕ_{out}
- Local reference clock may be frequency multiple of input clock
- PLL depends on data input to provide “enough” signal transitions to lock onto, else PLL could lose coherency.
- Modern processors utilize PLL’s for frequency multiplication




Voltage Controlled Oscillator

 


Ring Oscillator

 - **VCO may be designed from ring oscillator where voltage controls the number of (odd) stages of inverters in the feedback ring**




LC Oscillator (conceptual illustration)

 
- **VCO may be designed from resonant oscillator where voltage controls capacitance in LC circuit.**






Delay Locked Loop

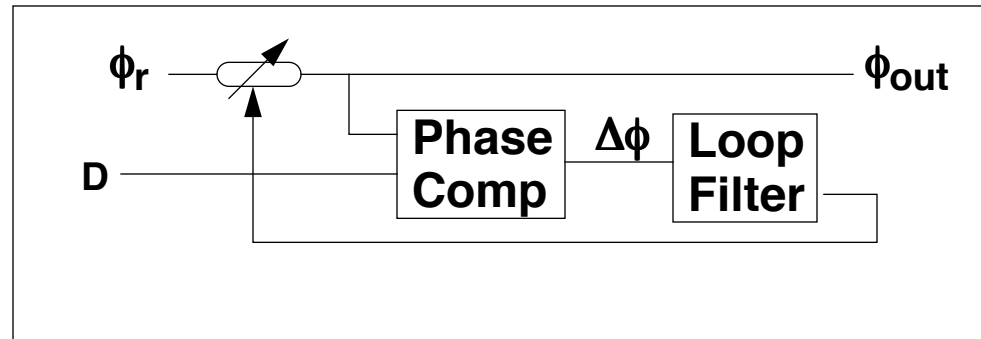



 
- Given a data signal and reference clock, compare and adjust phase of local clock signal by $\Delta\phi$
- Unlike PLL, requires reference clock
- Hence, no need to “recover” clock signal with VCO
- Modern DRAM with dual edged clocking utilizes DLL's for phase compensation. (gets you 90 degrees)





Zero-Skew Clock Distribution

  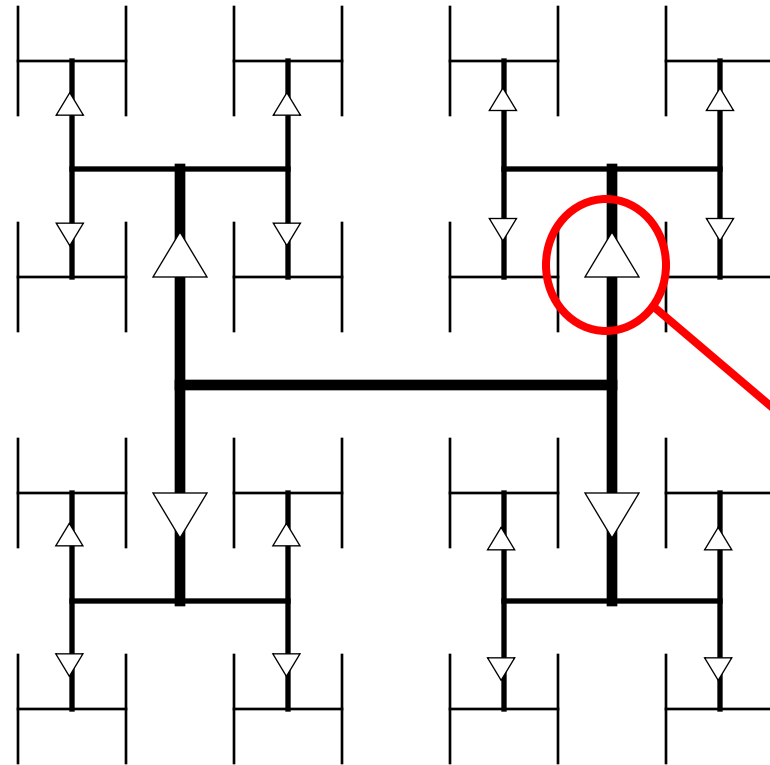


DLL in DDR SDRAM

 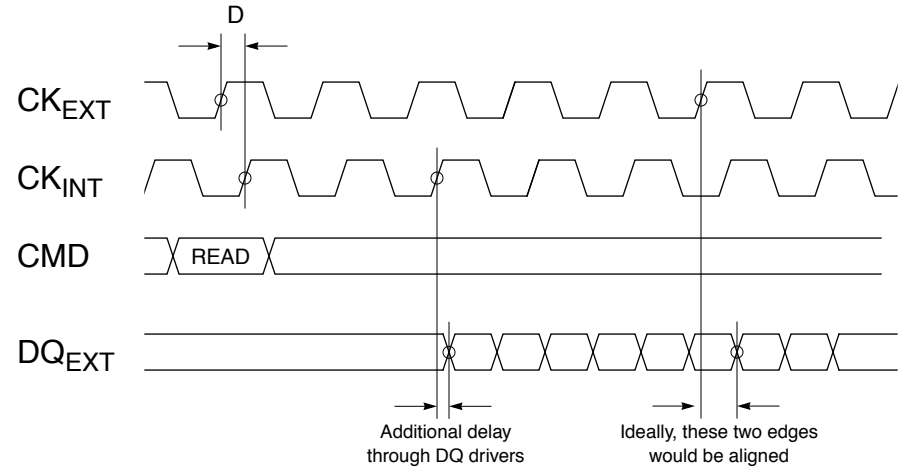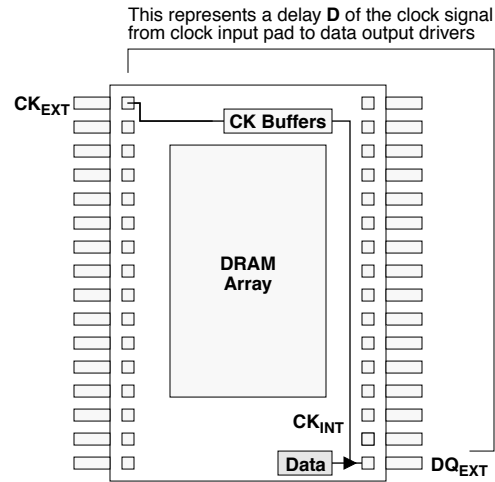

 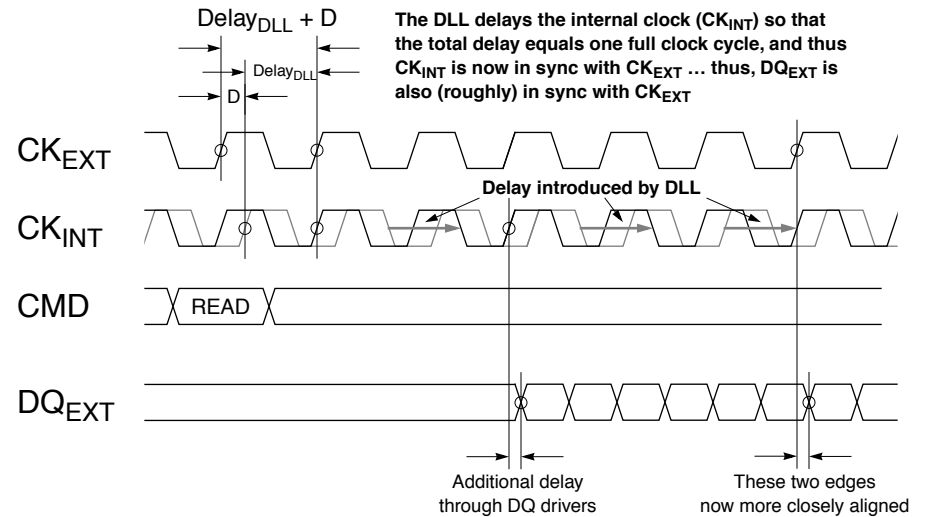The Phase Comparison, Loop Filter, and Variable Delay components constitute a DLL




A Signaling System





 


- 1. Transmitter: Encodes data as current/voltage level onto the line**
- 2. Transmission Line: Deliver data from transmitter to receiver**
- 3. Receiver: Compare against reference to extract data**
- 4. Terminator: Remove signal from line, once they're received**
- 5. Clock: Tells transmitter when to send, receiver when to sample signal**


* Poulton ISSCC 1999 Signaling Tutorial

 


Idea: Detect “0” vs. “1”

     


Basic Problem: Voltage Noise

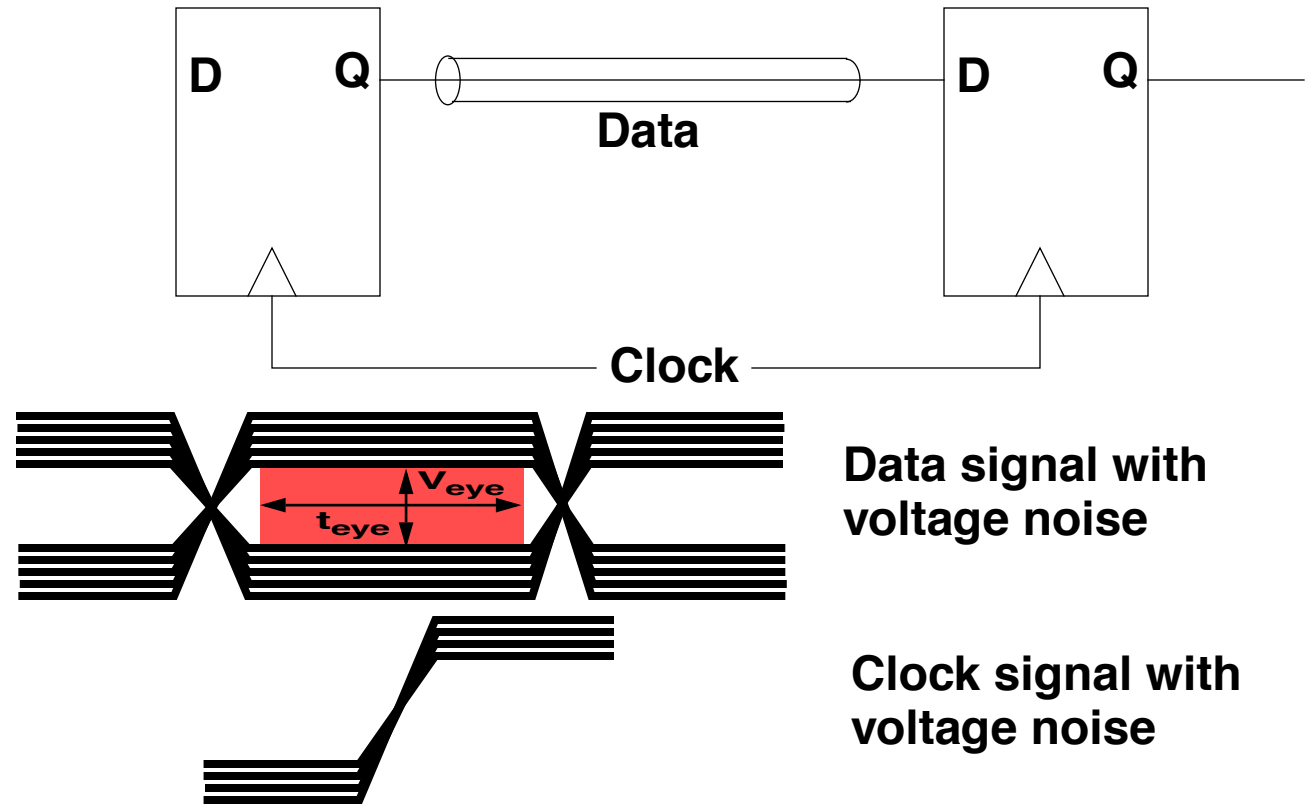


Voltage noise reduces operating margins

 


Basic Problem: **Timing Noise**

 


Timing noise reduces operating frequency

 


Basic Problem: **Both**

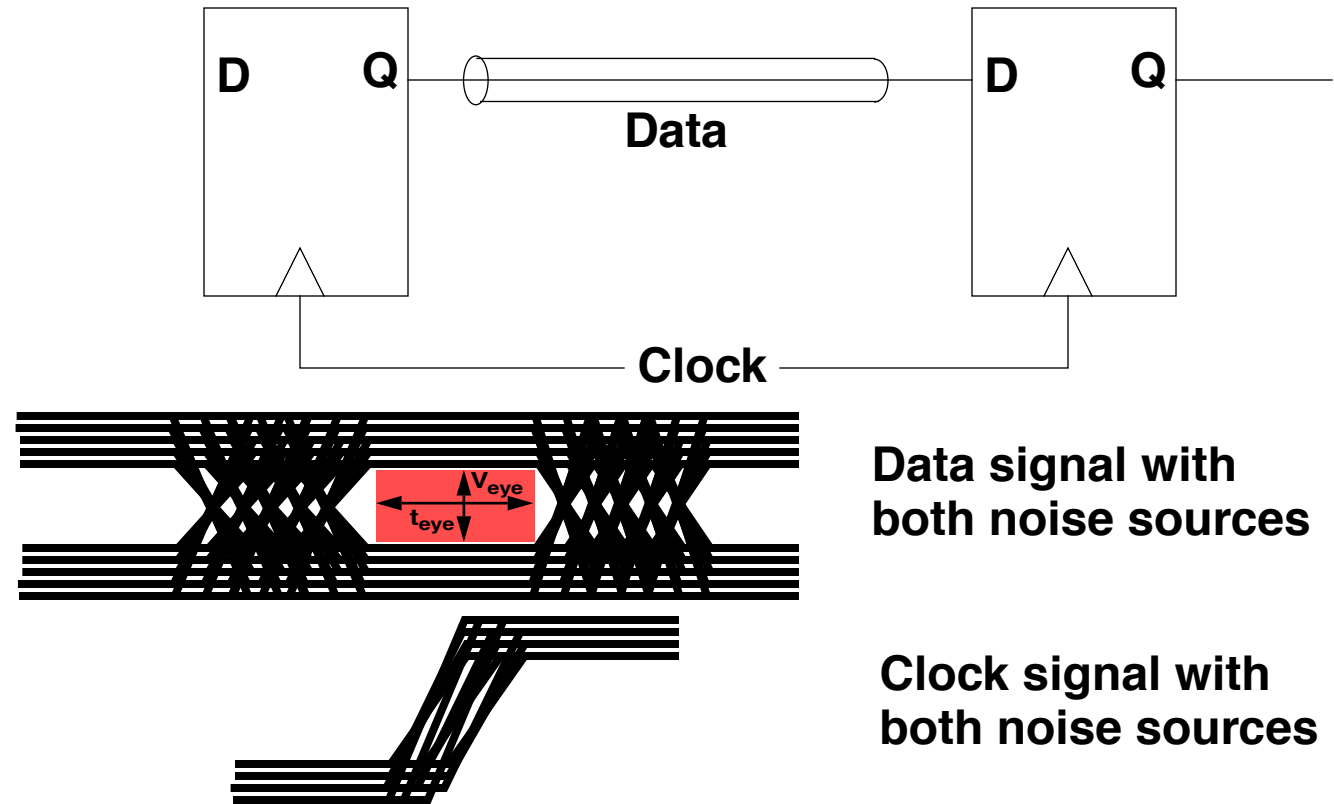

 Note: Clock signal is just another signal subject to same constraints of voltage noise, skew and jitter as data signals




Eye Diagram

 


**Yes, there really is that much voltage noise;
Yes, there really is that much timing noise ...**


Life sucks; deal with it.

 


Dual Edge Clocking

 

 
- Only one edge of clock latches data
- Duty cycle of clock signal is not relevant
- Clock signal operating at 2X switching rate of data
- Always a clock edge where you need one



 - Both edges of clock used to latch in data
- Duty cycle & rise/fall times of clock must be even
- Clock signal must be phase shifted by 90 degrees relative to phase of data signal
- How do you get 90 degrees ??




Cycle Budget

 

$$t_{\text{skew}} = \max(\text{skew}) + \max(\text{jitter})$$

$$t_{\text{tran}} = \text{Edge transition time} = \max(\text{rise_time}, \text{fall_time})$$

 
$$t_{\text{eye}} \leq t_{\text{cycle}} - t_{\text{tran}} - t_{\text{skew}}$$



One “Typical” Timing Budget

Timing Parameters	pS
Clock Skew on Transmit Side	100
Silicon on Transmit side	1,000
Wiring - drive to chip pad, drive module, card (40cm), receiver module, chip pad to receiver.	3,000
Silicon on Receive Side	1,000
Clock Skew on Receive Side	100
Coupling, Jitter, Reflections	700
PLL - Long term jitter	250
Total	6,150

 *Power4 Synchronous Wave Pipelined Interface Presentation, Hotchips '99



Timing: Clock \cap Data

Define *when* a value is present on a line ...

How many 1's? How many 0's?




Need **convention** to distinguish where one '1' ends and next '1' begins ... conventions typically mark boundaries w/ *TRANSITIONS*


- of the signal itself
- of an associated *clock* signal

(original definition of "synchronous")

 
Uncertainty in timing limits operating speed



Timing Conventions


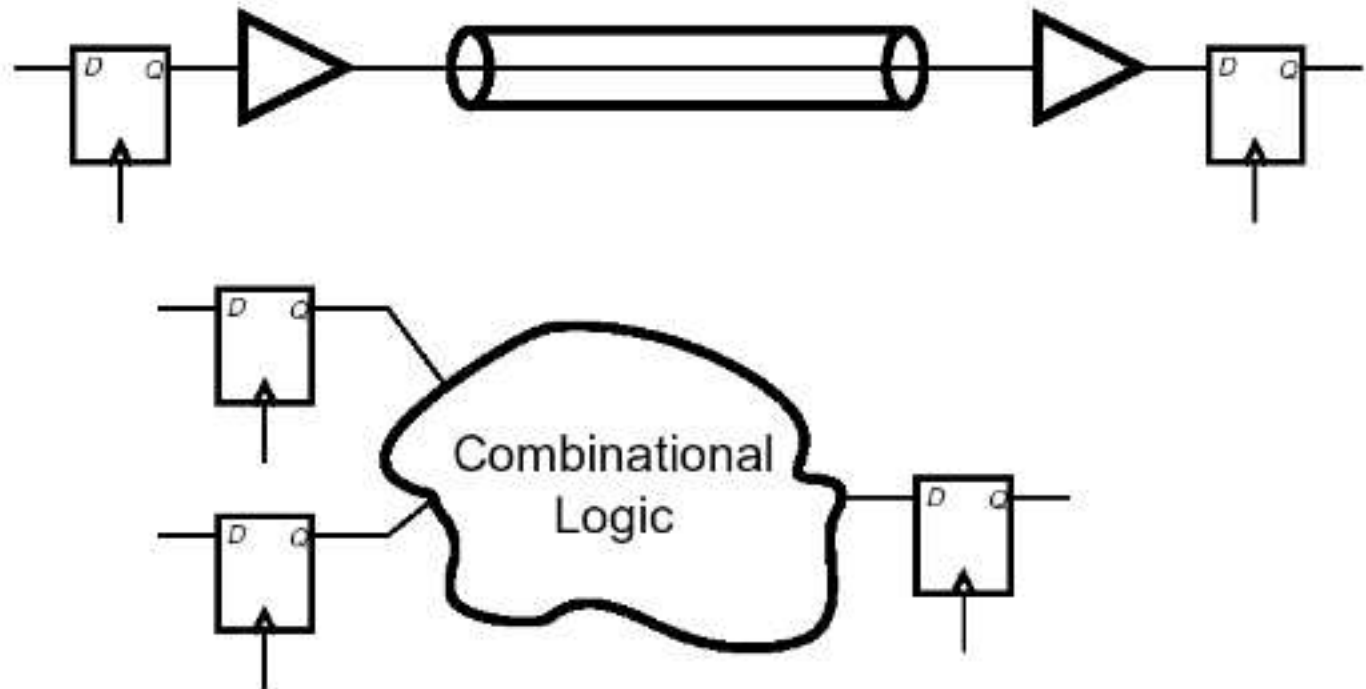


 Apply to both inter- *and* intra-chip signaling




Setup Time

 
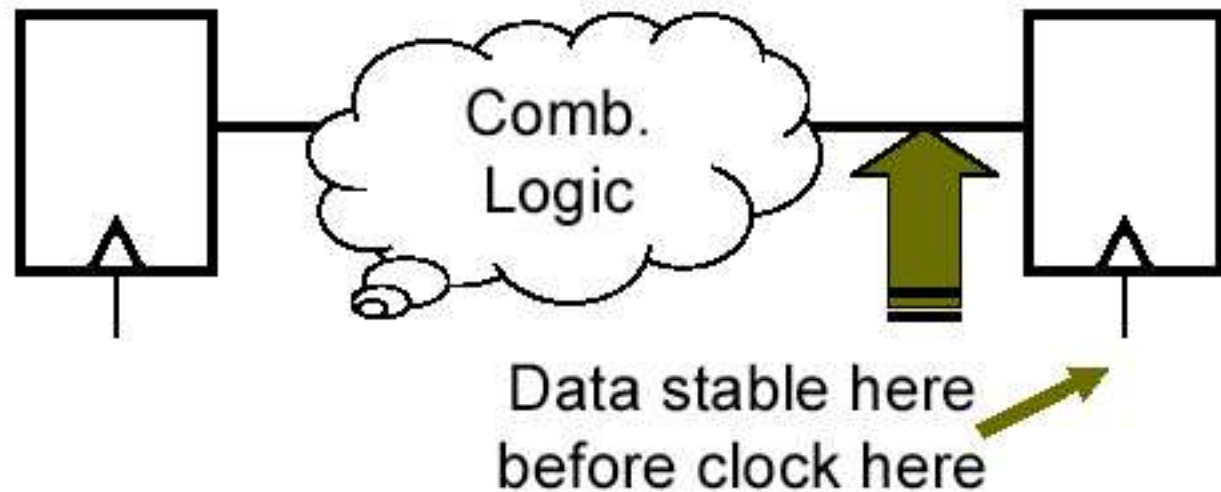
**Required time for input to be stable
BEFORE CLOCK EDGE**





Setup Time Fix

 

  This violation can be fixed by stretching the clock cycle





Setup Time Fix II

  

Hold Time


Required time for input to be stable

AFTER CLOCK EDGE

  

Hold Time Violations



Prop Delay: 1 ns Hold Time: 2 ns

 

Hold time violations are caused by “short paths”

Cannot be fixed by slowing down the clock!!!

Fixed by slowing down fast paths

  


A Tale of Two (or more) Timing Conventions

Synchronous: global clock

Synchronous: source-synchronous I
(“open-loop” meaning no control loop)

Synchronous: source-synchronous II
(“closed loop” meaning feedback control)


~~**Asynchronous: self-timed**~~

 

System Building Blocks



DELAY ELEMENTS

 - Nominal delay
- Timing uncertainty, skew, jitter




COMBINATIONAL LOGIC

  - Contamination delay
- Propagation delay



CLOCKED STORAGE ELEMENTS

 - Align signal to a clock
- Signal waits to be sampled by clock
- Output held steady until next clock





Edge-Triggered Register

Samples data on
rising edge of CLK

- **Data must remain valid during an aperture of time during sampling**

Output held steady
until next CLK edge

 
 
- **Output is held until a *contamination delay* following CLK edge**
- **Output has a correct value after a *propagation delay* following CLK edge**



Other Storage Elements


LEVEL-SENSITIVE LATCH

  - **Passes data through** when enable (clock) is **high**
- **Holds data stable** when enable (clock) is **low**



DUAL-EDGE-TRIGGERED FLIP-FLOP/REGISTER

 - **Samples data at both edges** of the clock
- Internally two interleaved flip-flops (1 posedge FF + 1 negedge FF)
- Allows **CLK** to run at **same speed as data**




Eye Diagram, Redux


MAXIMUM OPERATING RATE

(i.e., signaling speed)

LIMITED BY THREE FACTORS:

 


 - T_r – Transition time (rise/fall time)
- T_u – Timing uncertainty, skew, jitter
- T_a – Aperture time
- $T_{bit} \geq T_r + T_u + T_a$ (*but not that simple ...*)




Synchronous Timing I

GLOBAL CLOCK (Conventional) EXAMPLE

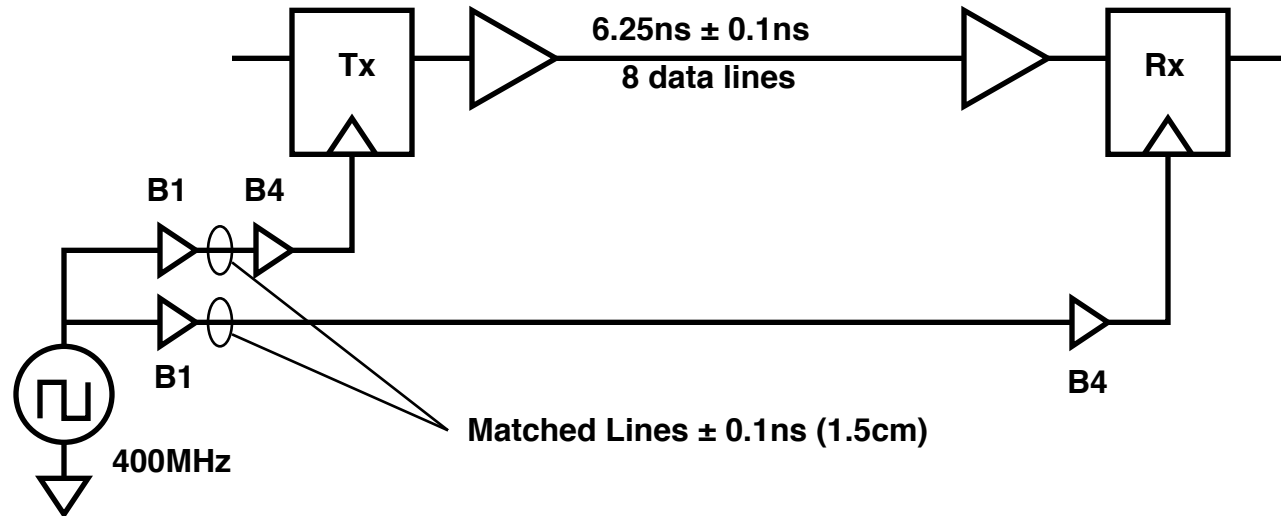


Parameter	Symbol	Nominal	Skew	Jitter
Bit Cell (data period)	Tbit	2.5 ns		
Transmitter Rise Time	Tr	1.0 ns		
Cable Delay	Twire	6.25 ns	100 ps	
Receiver Aperture	Ta	300 ps	100 ps	50 ps
Transmitter Delay		500 ps	150 ps	50 ps
Buffer Stage Delay	B#	250 ps	100 ps	50 ps

 


Synchronous Timing I

Sources of uncertainty:

 - **Skew** (across multiple lines) of line delay
- **Jitter** of Tx, Rx, and line delay
- **Skew** and **jitter** of global clock (usually large due to high fan-out)




 For best performance,
center sampling edge
on data eye





Gross timing margin
 
$$= \frac{1}{2} [T_{\text{bit}} - T_r - T_a] = \pm 600\text{ps} = \underline{\underline{1/2 T_u?}}$$



An Aside ...

 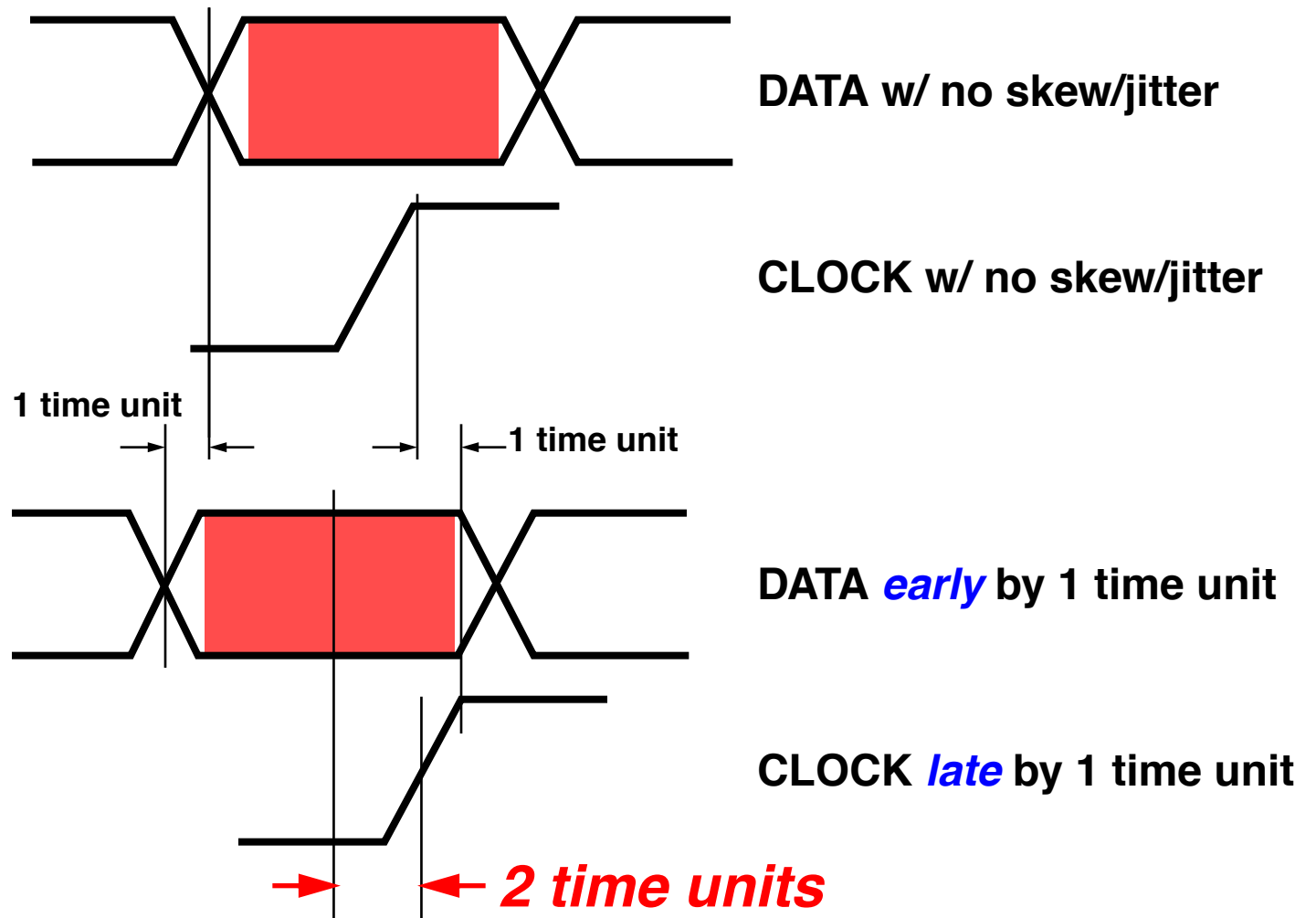***Why do we simply add up the uncertainties?
And why does each effectively count twice?***



Synchronous Timing I

TIMING ANALYSIS

Clock Skew: 100ps
lines + 100ps B1 +
400ps B4

Clock Jitter: 50ps B1 + 200ps B4



[CLKs **times 2**: one for xmit, one for recv]

Transmitter: 150ps skew, 50ps jitter

Receiver: 100ps skew, 50ps jitter

Data Cable: 100ps skew

  TOTAL: 1550ps skew, 600ps jitter (**BAD**)





Synchronous Timing I


LIMITS TO LINE DELAY & DATA FREQUENCY

Conventional Wisdom:
Line Delay Must Be

ODD NUMBER of HALF-BITS ... WHY?

  


 For fixed line length and tight margins,
this limits the bus speeds that can be used



Synchronous Timing I


SUMMARY

 

GLOBALLY


SYNCHRONOUS DESIGN:

 - For long wires and high speeds, only a handful of frequencies work
- Impractical to control uncertainties
- Cannot switch frequencies



Synchronous Timing II


PIPELINED TIMING: BASIC IDEA

 

**Delay the clock by the same amount as data
... PLUS half a bit-cell**


**System will work from DC to maximum
theoretical frequency $1/(T_r + T_u + T_a)$**

 Defines new clock domain at receiving end



Synchronous Timing II

SOURCES OF UNCERTAINTY

 


SKEW:

- **Between CLK & Data line**
- **Fixed differences in FF, Tx, Rx delays**
- **Different CLK delays to different FFs**
- **Aperture offset in Rx FF**
- **Extra offset in the delayed CLK line**



JITTER:

 - **In Tx clock**
- **In FF, Tx, Rx delays**



Synchronous Timing II

OPEN-LOOP PIPELINED EXAMPLE

 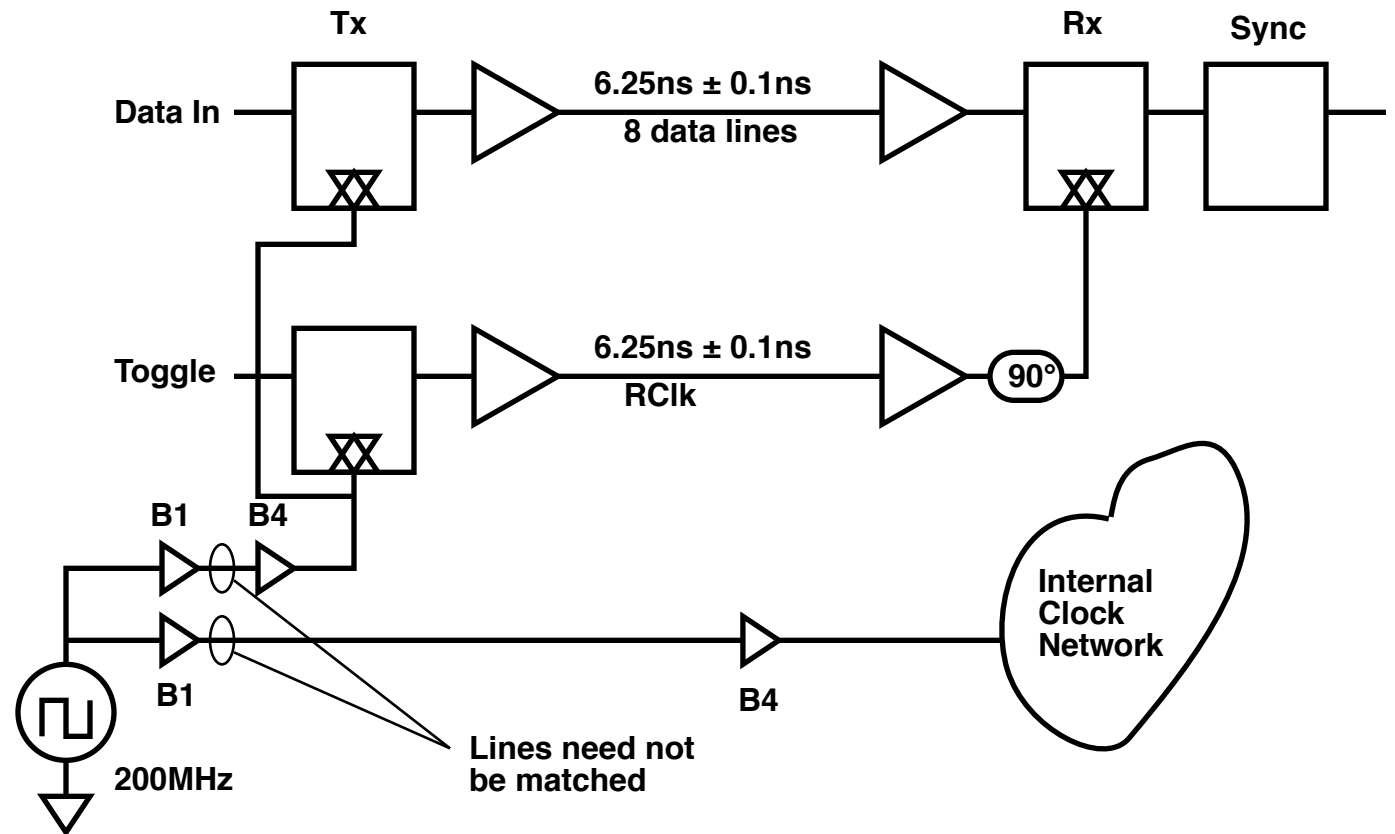

Synchronous Timing II

TIMING ANALYSIS

Xmit data: 150ps
skew, 50ps jitter



Xmit toggle: 150ps
skew, 50ps jitter

Receiver: 100ps skew, 50ps jitter

Data cable: 100ps skew


Toggle clock cable: 100ps skew

TOTAL: 600ps skew, 150ps jitter (BETTER)

 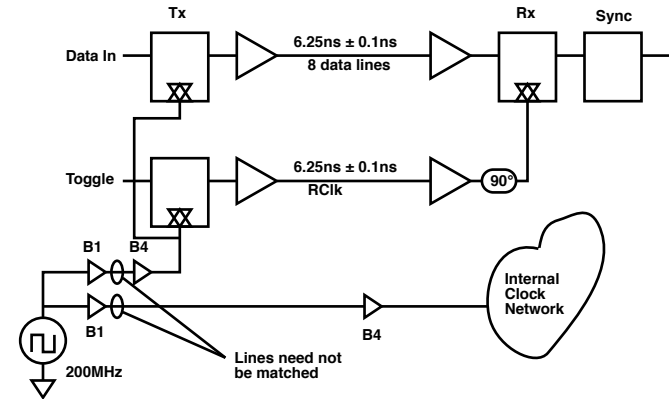


Synchronous Timing III

CLOSED-LOOP PIPELINED EXAMPLE


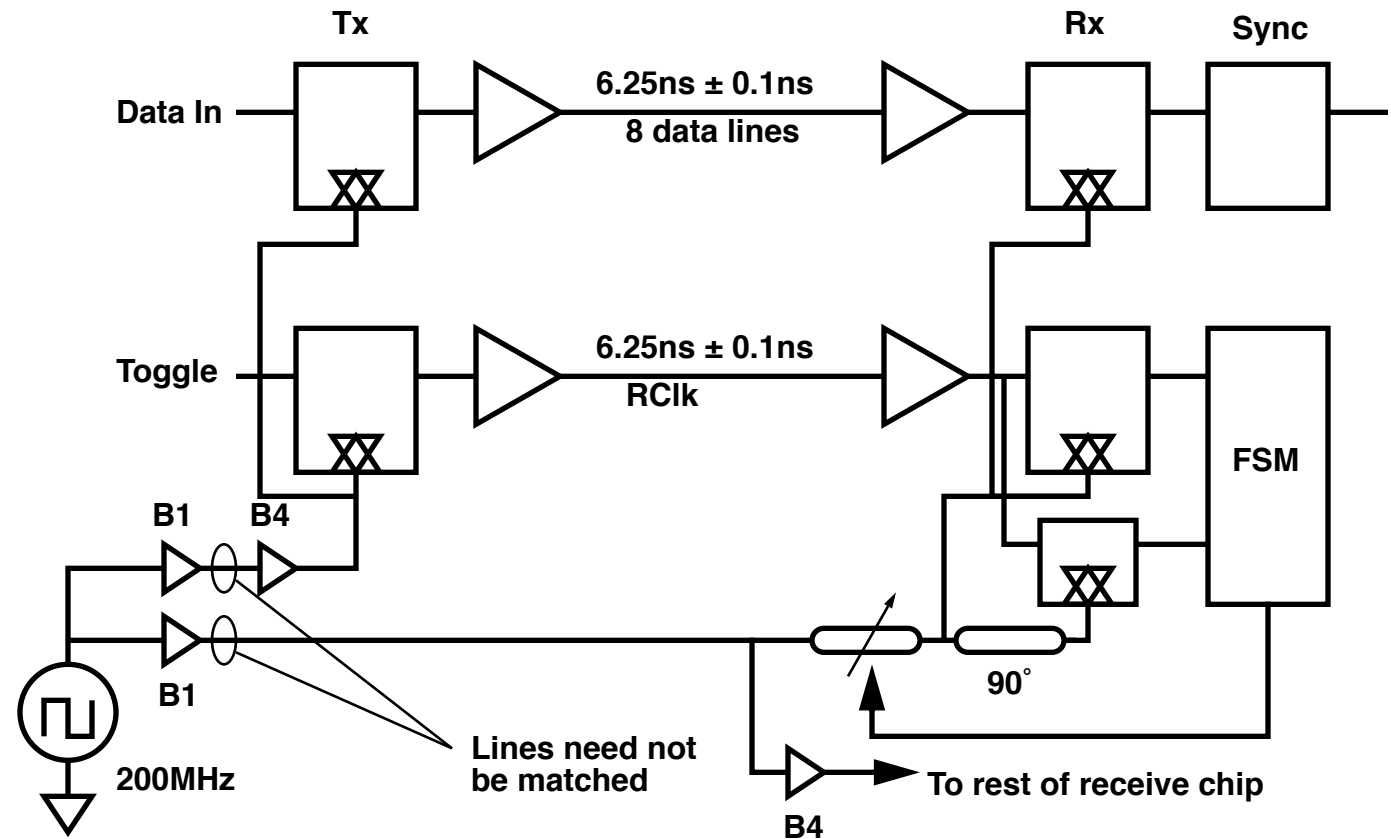


 (almost)
Variable delay line can cancel ALL SKEW



Synchronous Timing III

COMPONENTS of CONTROL LOOP (DLL)

 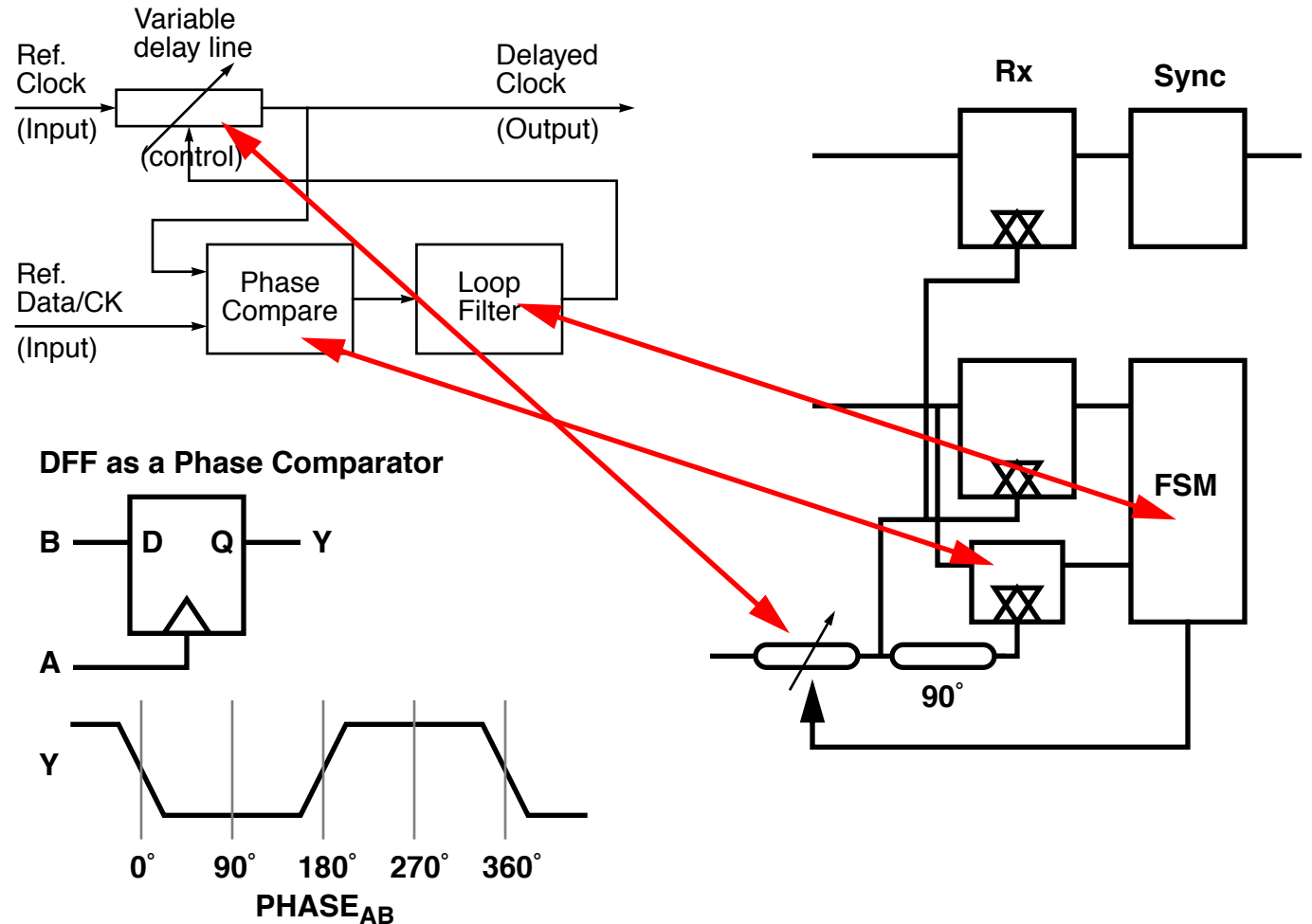

Synchronous Timing III

TIMING ANALYSIS

Xmit data: 50ps jitter

Recv data: 50ps jitter

Xmit toggle: 30ps



skew data/toggle (0?), 50ps jitter

Recv toggle: 20ps skew (0?), 50ps jitter

Data cable: 100ps skew

Toggle clock cable: 100ps skew

TOTAL: 250ps skew, 200ps jitter (GOOD!)


 
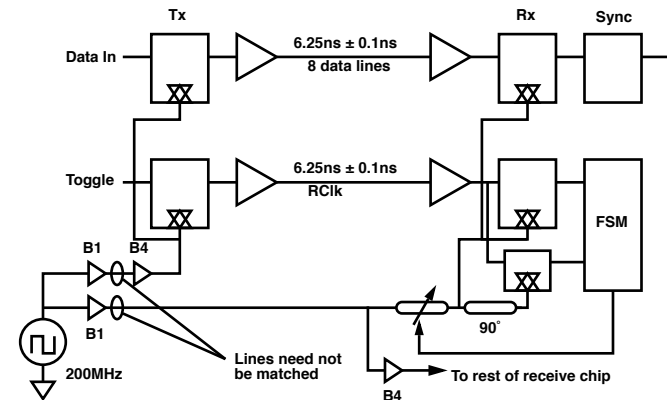


Synchronous Timing II & III

LIMITS TO LINE DELAY & DATA FREQUENCY

None.

 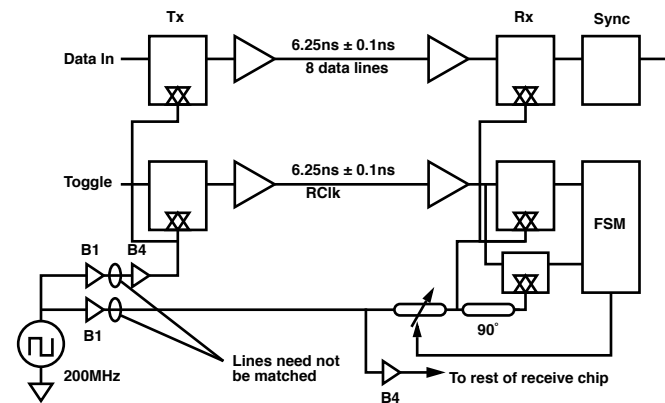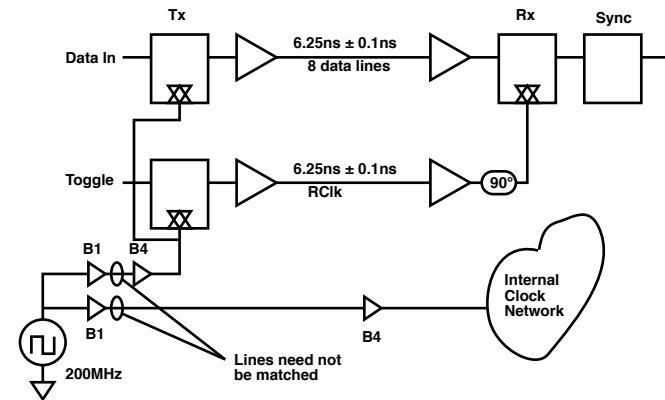Only limiter to bus
frequency is the rate
at which you can
successfully transmit
& receive data
(e.g. Taperture +
Tuncertainty + Ttransmit)



Example from the other day (re: question – why does DDR need a turnaround time but Rambus does not?)

