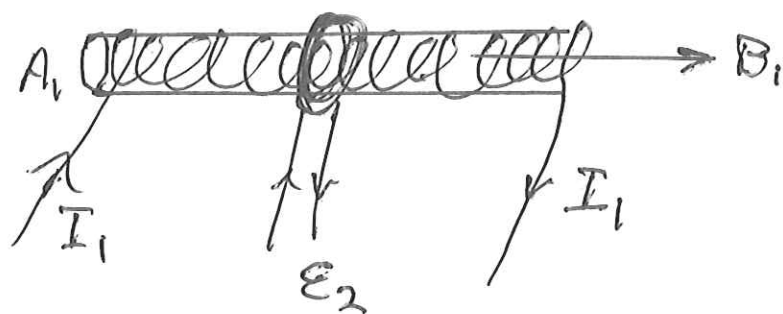


Inductance

We previously discussed how the changing current and magnetic field in a solenoid ~~induces~~ induces an electric field throughout space and in the presence of secondary coil can induce an emf in that coil.



$$B_1 = \mu_0 \frac{N_1}{l_1} I_1$$

N_1 = total # of loops in the solenoid

l_1 = the solenoid length

$$\Phi_1 = B_1 A_1 = \mu_0 \frac{A_1 N_1}{l_1} I_1$$

The induced emf in the secondary coil with N_2 wraps is given by

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_1}{dt}$$

$$= -N_2 \frac{\mu_0 A_1 N_1}{l_1} \frac{dI_1}{dt} = -M \frac{dI_1}{dt}$$

$\Rightarrow$ the changing current I_1 and flux Φ_1 induces an emf in the N_2 coil. The constant

$$M \equiv \frac{N_1 N_2 \mu_0 A_1}{l_1}$$

is the mutual inductance of the two coils. It depends only on the geometry of the two coils.

More generally,

$$M \equiv \frac{N_2 \Phi_1}{I_1}$$

with Φ_1 the flux produced by the current I_1 that links N_2 . A perhaps surprise is that

$$M = \frac{N_1 \Phi_2}{I_2}$$

$\Rightarrow$ with Φ_2 the flux produced by I_2 that links N_1 .

units: the measure of inductance is the Henry

$$1 \text{ H} \equiv \frac{1 \text{ V s}}{\text{A}}$$

$\Rightarrow$ typically in the range of μH


example: $\ell = 0.5 \text{ m}$, $A = 10 \text{ cm}^2$, $N_1 = 10^3$, $N_2 = 10$

$$\begin{aligned} M &= \frac{4\pi \times 10^{-7} \text{ T m}}{\text{A}} \cdot \frac{10^{-3} \text{ m}^2 \cdot 10^3 (10)}{0.5 \text{ m}} \\ &= \frac{4\pi}{0.5} \mu\text{H} = 25 \mu\text{H} \end{aligned}$$

Self-inductance

A single solenoid whose current is changing in time also induces an emf in itself due to its changing magnetic flux. This is called self-inductance, and plays an important role in the time behavior of circuits.

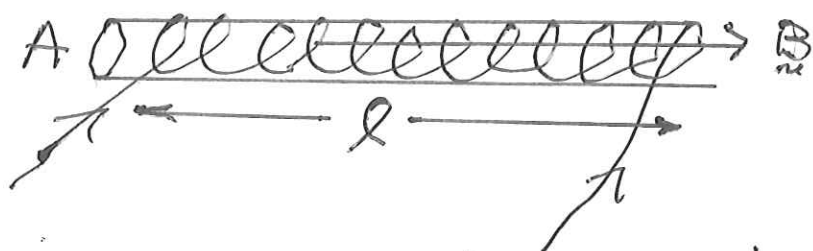Consider a long solenoid of area A and length ℓ wound with N turns of wire. Current I .



The magnetic field is

$$B = \mu_0 \frac{NI}{\ell}$$

The flux through the solenoid is

$$\Phi = BA = \frac{\mu_0 NI}{\ell} A$$

The induced emf across the solenoid is given by

$$\begin{aligned} \mathcal{E} &= -N \frac{d\Phi}{dt} = -N \frac{\mu_0 NA}{\ell} \frac{dI}{dt} \\ &= -\frac{\mu_0 N^2 A}{\ell} \frac{dI}{dt} \end{aligned}$$

Define

$$L = \frac{\mu_0 N^2 A}{l} = \text{self-inductance}$$

$$\text{or } L = \frac{N \Phi}{I}$$

$$\Rightarrow \mathcal{E} = -L \frac{dI}{dt}$$

The direction of the emf is so as to resist the change in current

$$\text{units: } L = 1 \text{ Henry} = 1 \frac{\text{volt-sec}}{\text{amp}}$$

Energy stored in an inductor

As you increase the current in an inductor, you must overcome the emf in the inductor which opposes the change in I . You are injecting energy into the inductor. As you move charge ΔQ along the inductor you change its energy by $\Delta Q \mathcal{E}$. The rate of injection of power into the inductor is therefore

$$P = -\mathcal{E} \frac{\Delta Q}{\Delta t} = -\mathcal{E} I$$

$$\text{or } P = -(-L \frac{dI}{dt}) I = L I \frac{dI}{dt}$$

$$= \frac{d}{dt} \left(\frac{1}{2} L I^2 \right)$$

$$W = \frac{1}{2} L I^2 = \text{energy stored in the inductor}$$

The energy stored is magnetic energy

$\Rightarrow$ an inductor is a magnetic energy storage device

$\Rightarrow$ just like a capacitor is an electric field energy storage device

magnetic energy.

For a solenoid

$$L = \frac{\mu_0 N^2}{\ell} A, \quad B = \frac{\mu_0 N I}{\ell}$$

so

$$W = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{\ell} I^2$$

$$= \frac{1}{2} \left(\frac{\mu_0^2 N^2 I^2}{\ell^2} \right) \frac{\ell A}{\mu_0}$$

$$= \left(\frac{B^2}{2\mu_0} \right) A \ell = \frac{B^2}{2\mu_0} \text{Vol}$$

$\Rightarrow V = A \ell = \text{volume of solenoid}$

$$u = \frac{B^2}{2\mu_0} = \frac{\text{energy}}{\text{vol}} \Rightarrow \text{energy density of magnetic field}$$


$\Rightarrow$ compare this to $u = \frac{1}{2} \epsilon_0 E^2$

for the electric field energy density

$\Rightarrow$ with magnetic materials

$$u = \frac{B^2}{2\mu}$$

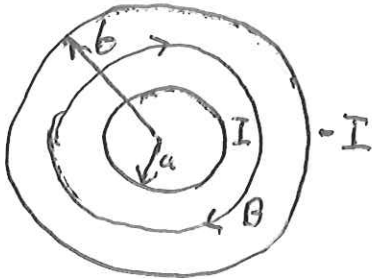example: Energy storage and inductance of a co-axial cable $\Rightarrow$ length l and radii a, b with $a < b$.



A co-axial cable has a current I flowing into the page (assume current on surface) ~~and~~ on the inner conductor and a current $-I$ flowing out of the page on the outer conductor.

Use Ampere's Law to solve for B :

$B=0$ for $r < a$, $r > b$ since zero current ($r < a, I=0$; $r > b, I-I=0$)

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 (\text{current through loop})$$


For $a < r < b$

$$\oint \vec{B} \cdot d\vec{l} = B 2\pi r = \mu_0 I$$

$$B = \frac{\mu_0 I}{2\pi r}$$

Calculating inductance
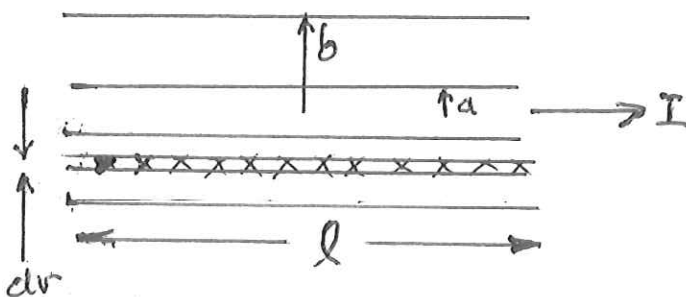
$$L = \frac{N\Phi}{I} = \frac{\Phi}{I} \Rightarrow N=1 \text{ single loop} \Rightarrow \text{down and back}$$



magnetic flux $d\Phi$ in area $dr \cdot l$

$$d\Phi = \frac{\mu_0 I}{2\pi r} l dr$$

Integrate the magnetic flux from "a" to "b".

$$\Phi = \int_a^b d\Phi = \frac{\mu_0 I}{2\pi} \ell \int_a^b \frac{dr}{r} = \frac{\mu_0 I \ell}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$L = \frac{\Phi}{I} = \frac{\mu_0 \ell}{2\pi} \ln\left(\frac{b}{a}\right)$$


Stored magnetic energy

$$\begin{aligned}
 U &= \int dV \frac{B^2}{2\mu_0} \quad) \quad dV = 2\pi r dr \ell \\
 &= \int_a^b 2\pi r dr \ell \left(\frac{\mu_0^2 I^2}{4\pi^2 r^2} \right) \frac{1}{2\mu_0} \quad \Rightarrow \text{cylindrical shell} \\
 &= \frac{\mu_0 I^2 \ell}{4\pi} \int_a^b dr \frac{1}{r}
 \end{aligned}$$


The diagram shows a cylindrical shell of length ℓ . A cross-section is shown with radius r and thickness dr . The shell is oriented horizontally.

$$= \frac{\mu_0 \ell}{4\pi} \ln\left(\frac{b}{a}\right) I^2 = \frac{1}{2} L I^2$$

Circuits with inductors: R-L circuits

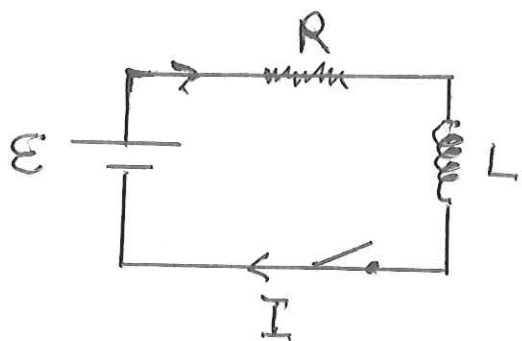

Consider an inductor L and resistor R in a circuit.

⇒ close switch at $t=0$

How does the current evolve in time? Without the inductor

$$\mathcal{E}_L = -L \frac{dI}{dt}$$

$$I_0 = \frac{\mathcal{E}}{R}$$

However the current can't instantaneously increase to this value since the emf needs to supply magnetic energy to the inductor for the current to build up

⇒ requires some time

⇒ after a long time?

~~After a long time~~

Once the magnetic energy in the inductor has built up, the inductor no longer produces an emf so it doesn't affect the final current

$$I = \frac{\mathcal{E}}{R}$$

Use Kirchhoff's loop rule

$$\mathcal{E} - IR - L \frac{dI}{dt} = 0$$

⇒ divide by L

$$\frac{dI}{dt} + \frac{R}{L} I = \frac{\mathcal{E}}{L} = \frac{\mathcal{E}}{R} \frac{R}{L} = I_0 \frac{R}{L}$$

$\Rightarrow$ Find time constant using units of the equation

$$\Rightarrow \frac{\text{current}}{\text{time}}$$

$$\Rightarrow \frac{1}{\gamma} = \frac{R}{L} \Rightarrow \gamma = \frac{L}{R}$$

$\gamma = \frac{L}{R} = \text{time constant of a L-R circuit}$

$$\text{units: } \gamma = \frac{\text{Henry}}{\text{Ohms}} = \left(\frac{\text{Vs}}{\text{A}} \right) \left(\frac{\text{amp}}{\text{V}} \right) = \text{sec}$$

The time constant tells you how long it takes the magnetic energy in the inductor to build up, allowing the current to reach its full value.

Solution for time dependence:

$$\frac{dI}{dt} + \frac{1}{\gamma} I = \frac{1}{\gamma} I_0$$

$$\frac{dI}{dt} = \frac{1}{\gamma} (I_0 - I)$$

$$\int_0^I \frac{dI}{I_0 - I} = \int_0^t \frac{dt}{\gamma} = \frac{t}{\gamma}$$

$$-\ln(I_0 - I) \Big|_0^I = \frac{t}{\tau}$$


$$\ln\left(\frac{I_0 - I}{I_0}\right) = -\frac{t}{\tau}$$

Take the exponential of both sides

$$\frac{I_0 - I}{I_0} = e^{-\frac{t}{\tau}} \Rightarrow I = I_0(1 - e^{-\frac{t}{\tau}})$$

As $t \rightarrow \infty$, $e^{-\frac{t}{\tau}} \rightarrow 0 \Rightarrow I = I_0$

At $t = 0$, $I = 0$.

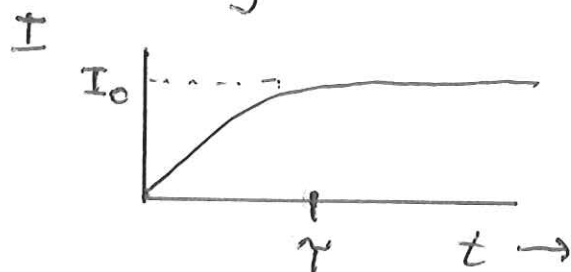


The current reaches a steady value in a time $\tau = \frac{L}{R}$

Note that for $t \ll \tau$, most of the potential drop is across the inductor since $\epsilon - IR \ll L \frac{dI}{dt}$ and for $t \gg \tau$ most of the potential drop is across the resistor.

L-C circuit (no resistance)

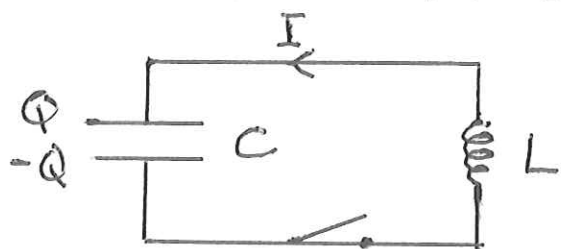Consider a capacitor in series with an inductor. We initially have the capacitor charged with Q_0 . Close the switch and follow the behavior in time



Choose current direction
so $I = \frac{dQ}{dt}$

$\Rightarrow$ positive I means charge flowing into C .

Use Kirchhoff's loop rule in direction of I .

$$-L \frac{dI}{dt} - \frac{Q}{C} = 0$$

$$-L \frac{d^2Q}{dt^2} - \frac{Q}{C} = 0$$

$$\frac{d^2Q}{dt^2} + \frac{1}{LC} Q = 0 \quad \Rightarrow \quad \omega^2 \equiv \frac{1}{LC}$$


$$\frac{d^2Q}{dt^2} + \omega^2 Q = 0 \quad \sim \frac{1}{\text{sec}^2}$$

$\Rightarrow$ same as eqn for pendulum or spring/mass system


$$Q = Q_0 \cos \omega t$$

$$I = \frac{dQ}{dt} = -\omega Q_0 \sin(\omega t)$$

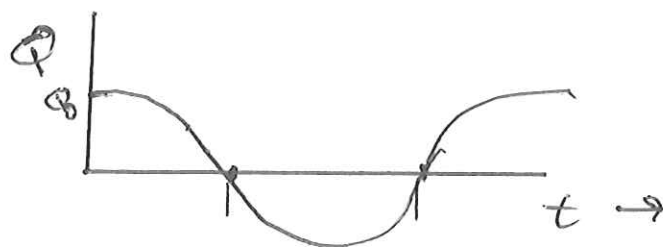$\Rightarrow$ both Q and I are oscillatory



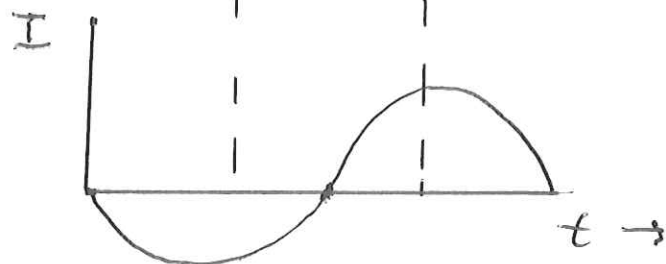$\Rightarrow Q$ decreases in time initially



$\Rightarrow I < 0$ at early time as current flows out of C.

It is useful to look at how energy is exchanged between C (electric field energy) and L (magnetic field energy).

$$L \frac{dI}{dt} + \frac{Q}{C} = 0$$

Multiply by I ,

$$L I \frac{dI}{dt} + I \frac{Q}{C} = 0$$

$$\frac{d}{dt} \left(\frac{1}{2} L I^2 \right) + \frac{1}{C} Q \frac{dQ}{dt} = 0$$

$$\frac{d}{dt} \left(\frac{1}{2} L I^2 \right) + \frac{d}{dt} \left(\frac{Q^2}{2C} \right) = 0 \quad V = \frac{Q}{C}$$


$$\frac{d}{dt} \left(\underbrace{\frac{1}{2} L I^2}_{\text{magnetic energy in inductor}} + \underbrace{\frac{1}{2} C V^2}_{\text{electric field energy in capacitor}} \right) = 0$$

magnetic energy in inductor

electric field energy in capacitor

$\Rightarrow$ energy exchanged between capacitor and inductor

L-R Circuit

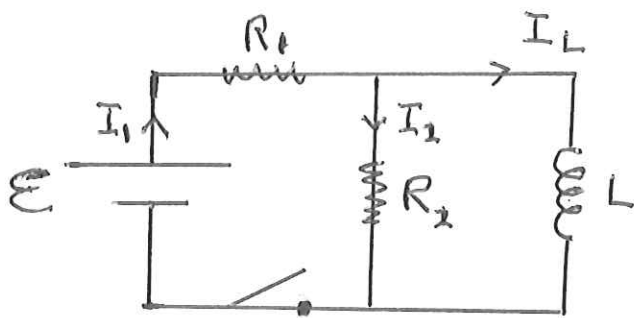

At ~~t~~ $t=0$ close switch

Find I_1 , I_L and I_2 just after the switch is closed.

$\Rightarrow I_L = 0 \Rightarrow$ no time to build magnetic energy in L

Loop rule (left loop)

$$\mathcal{E} - I_1 R_1 - I_2 R_2 = 0$$

point rule

$$I_1 = I_2 + I_L$$

$$\Rightarrow I_1 = I_2$$

$$I_1 = I_2 = \frac{\mathcal{E}}{R_1 + R_2}$$

Late time $\Rightarrow$ steady state $dI_L/dt = 0$

$\Rightarrow$ emf across inductor is zero

Loop rule right loop

$$-L \frac{dI_L}{dt} + I_2 R_2 = 0 \Rightarrow I_2 = 0$$

$\Rightarrow$ all current flows through inductor

Large loop

$$\mathcal{E} - I_1 R_1 = 0 \quad I_1 = \frac{\mathcal{E}}{R_1} = I_L$$

Time constant for circuit

Loop rule for large loop

$$\mathcal{E} - I_1 R_1 - L \frac{dI_L}{dt} = 0$$

$$I_1 = \frac{\mathcal{E} - L \frac{dI_L}{dt}}{R_1}$$

Right loop

$$-I_2 R_2 + L \frac{dI_L}{dt} = 0$$

$$I_2 = \frac{L}{R_2} \frac{dI_L}{dt}$$

Point rule

$$I_1 = I_2 + I_L$$

eliminate I_1, I_2


$$\frac{\mathcal{E} - L \frac{dI_L}{dt}}{R_1} = \frac{L}{R_2} \frac{dI_L}{dt} + I_L$$

$$L \left(\frac{1}{R_2} + \frac{1}{R_1} \right) \frac{dI_L}{dt} + I_L = \frac{\mathcal{E}}{R_1}$$

$$\gamma = L \left(\frac{1}{R_2} + \frac{1}{R_1} \right)$$

$$\gamma = \frac{L(R_1 + R_2)}{R_1 R_2}$$

LRC Circuit

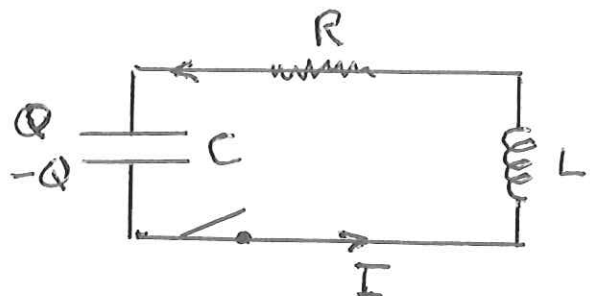

Loop rule


$$-L \frac{dI}{dt} - IR - \frac{Q}{C} = 0$$

Look at energy

$\Rightarrow$ multiply by I

$$\frac{d}{dt} \left(\frac{1}{2} LI^2 + \frac{1}{2} CV^2 \right) = -I^2 R$$

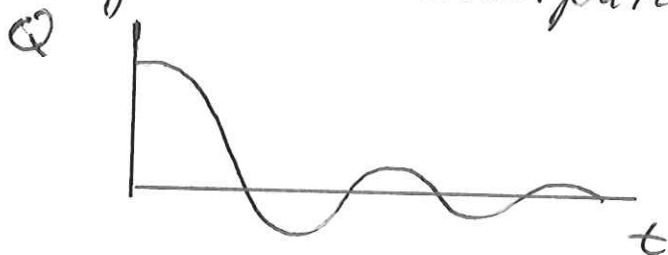The energy stored in the inductor and capacitor is dissipated in the resistor



Since $I = \frac{dQ}{dt}$

$$\frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$$

Solution

$$Q = Q_0 e^{-t/\gamma} \cos \omega t$$

$$\gamma = \frac{2L}{R} \quad \omega = \left(\frac{1}{LC} - \frac{R^2}{4L^2} \right)^{1/2}$$

valid for

$$\frac{R^2}{4L^2} < \frac{1}{LC} \Rightarrow \text{small resistance}$$

Oscillation with damping as shown above

$\Rightarrow$ called an under-damped oscillator

For $\frac{R^2}{4L^2} > \frac{1}{LC} \Rightarrow$ large resistance

$$Q = Q_0 e^{-t/\tau} \left(e^{t/\tau_1} + e^{-t/\tau_1} \right)^{1/2}$$

$$\frac{1}{\tau_1} = \left(\frac{R^2}{4L^2} - \frac{1}{LC} \right)^{1/2}$$

$\Rightarrow$ overdamped oscillator

$\Rightarrow$ no oscillations

