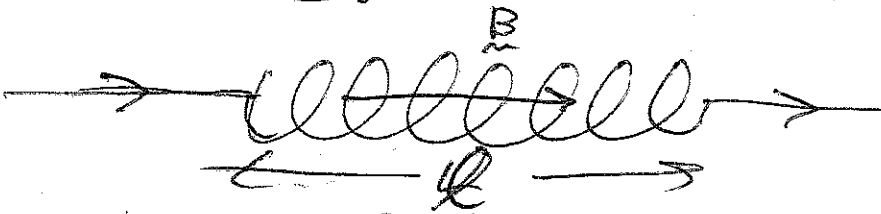


Self-Inductance

Consider a ~~wire~~^{long} solenoid of area A and length l wound with N turns of wire with current I .



magnetic field is $B = \frac{\mu_0 N I}{l}$

magnetic flux going through the solenoid is

$$\Phi = BA = \frac{\mu_0 N I}{l} A$$

What is the EMF induced ~~in the solenoid~~ across the solenoid as the current changes

$$\mathcal{E} = -N \frac{d\Phi}{dt} = -N \frac{\mu_0 N A}{l} \frac{dI}{dt}$$

$$= - \frac{\mu_0 N^2 A}{l} \frac{dI}{dt}$$

$$\mathcal{E} = -N \frac{d\Phi}{dt}$$

$$L = \frac{N\Phi}{I}$$

$$L = \frac{\mu_0 N^2 A}{l} = \text{self-inductance}$$


$$\mathcal{E} = -L \frac{dI}{dt}$$

direction of EMF is so as to ~~maintain~~ resist the change in current.

units $L = 1 \text{ Henry} = \frac{1 \text{ volt-sec}}{\text{Amp}}$

Energy Stored in an Inductor

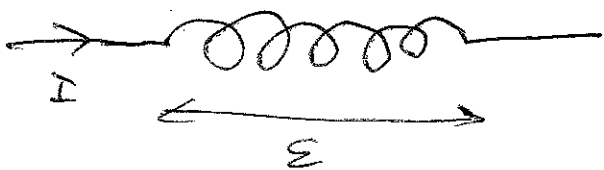As you increase the current in an inductor, you must ~~push~~ overcome the EMF in the inductor which opposes the change. Basically you are ~~pushing~~ injecting energy into the inductor.



$$\epsilon = -L \frac{dI}{dt}$$

power into the inductor

$$\frac{dW}{dt} = P = -\epsilon I = \mathcal{E} I \left(L \frac{dI}{dt} \right)$$

$$\frac{dW}{dt} = \frac{d}{dt} \left(\frac{1}{2} L I^2 \right)$$

$W = \frac{1}{2} L I^2 =$ total energy stored in the inductor.

⇒ as the current builds up, the magnetic field of the inductor increases

⇒ energy ~~stored~~ is stored as magnetic energy.

an inductor is a mag. energy storage device

example Solenoid

$$L = \frac{\mu_0 N^2}{l} A$$

$$B = \frac{\mu_0 NI}{l}$$

$$W = \frac{1}{2} LI^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{l} I^2 \Rightarrow$$

$$= \frac{1}{2} \frac{1}{\mu_0} \left(\frac{\mu_0^2 N^2 I^2}{l^2} \right) l A$$

$$= \left(\frac{1}{2} \frac{B^2}{\mu_0} \right) l A$$

$$V = \text{Vol} = l A$$

$$= \frac{1}{2} \frac{B^2}{\mu_0} V$$

$$u = \frac{B^2}{2\mu_0} = \frac{\text{energy}}{\text{unit Vol.}}$$


Energy in the magnetic field.

with magnetic material
 $u = \frac{B^2}{2\mu}$

\Rightarrow compare this to $u = \frac{1}{2} \epsilon_0 E^2$ associated with E field.


R-L Circuit

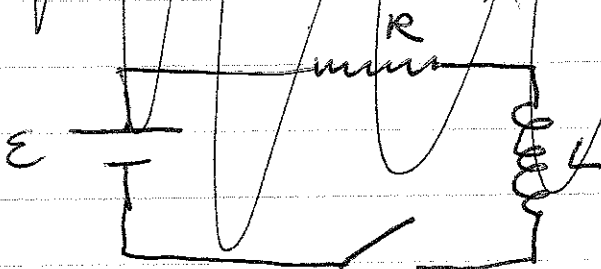We now want to include an inductor in a circuit. Consider the following circuit



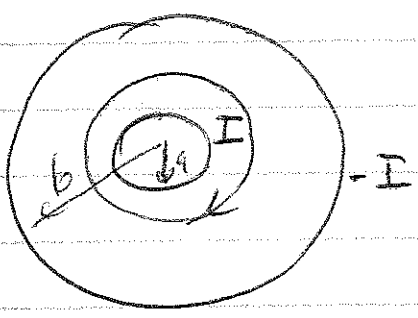Example

Energy storage and inductance of a co-axial cable. (Length l)




$$\oint \underline{B} \cdot d\underline{l} = \mu_0 I$$

$$B 2\pi r = \mu_0 I$$

$$B = \frac{\mu_0 I}{2\pi r}$$

$$L = \frac{N\Phi}{I} = \frac{\Phi}{I}$$
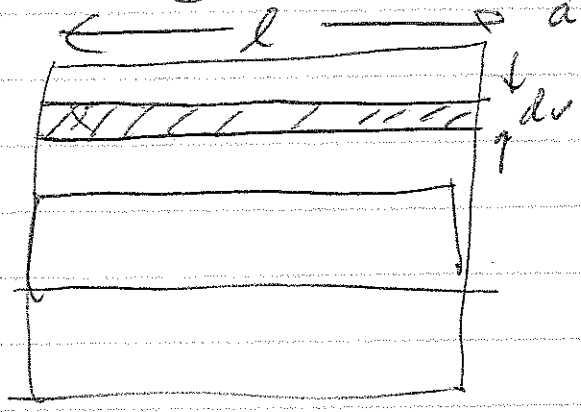
$$\Phi = \oint \underline{B} \cdot d\underline{A} = l \int_a^b \frac{\mu_0 I}{2\pi r} dr = \frac{l \mu_0 I}{2\pi} \ln\left(\frac{b}{a}\right)$$



$$L = \frac{l \mu_0}{2\pi} \ln\left(\frac{b}{a}\right)$$

Energy


$$U = \int dv \frac{B^2}{2\mu_0} = \frac{1}{2} \int_a^b \frac{\mu_0^2 I^2}{4\pi^2 r^2} \frac{2\pi r dr l}{2\mu_0}$$

$$= \frac{\mu_0^2 I^2 l}{4\pi} \ln\left(\frac{b}{a}\right) = \frac{1}{2} L I^2$$

Can calculate L by calculating Φ

R-L Circuit . Include inductor in a circuit. Consider

117

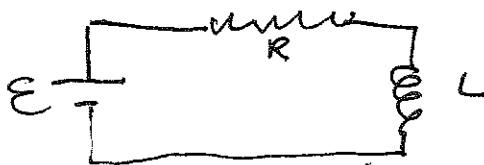

At ~~t=0~~ $t=0$, we close the switch. How does the current evolve in time?

Without the inductor $I_0 = \frac{\mathcal{E}}{R}$.

Can the current instantly increase to this value?

\Rightarrow must ~~be~~ supply energy to the inductor until the magnetic field is built up.


\Rightarrow requires some time.

What is the current after the switch has been closed for a long time?

$$I = \frac{\mathcal{E}}{R}$$

Once the magnetic energy in the inductor has been built up, the inductor no longer produces an EMF so ~~it~~ does not affect ^{final} current.

Use Kirchhoff's loop rule.

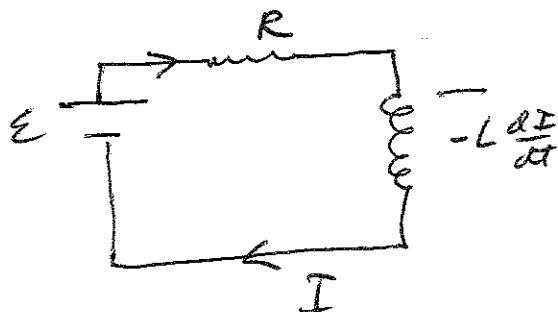

$$\mathcal{E} - IR - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} + \frac{R}{L} I = \frac{\mathcal{E}}{L} = \frac{\mathcal{E}}{R} \frac{R}{L} = I_0 \frac{R}{L}$$

$$\tau = \frac{L}{R} = \text{time constant of } L\text{-}R \text{ circuit}$$

$$= \frac{\text{Henry}}{\text{Ohm}} = \frac{\text{volt sec amp}}{\text{Amp volt}} = \text{sec}$$

$$\frac{dI}{dt} + \frac{I}{\tau} = \frac{I_0}{\tau}$$

$$\frac{dI}{dt} = \frac{I_0 - I}{\tau}$$

$$\int_0^I \frac{dI}{I_0 - I} = \int_0^t \frac{dt}{\tau} = \frac{t}{\tau}$$

$$-\ln(I_0 - I) \Big|_0^I = \frac{t}{\tau}$$

$$+\left[\ln(I_0 - I) - \ln I_0 \right] = -\frac{t}{\tau}$$

$$\ln \left(\frac{I_0 - I}{I_0} \right) = -\frac{t}{\tau}$$


$$\frac{I_0 - I}{I_0} = e^{-\frac{t}{\tau}}$$

$$I_0 - I = I_0 e^{-\frac{t}{\tau}}$$

$$I = I_0 (1 - e^{-t/\tau})$$

$t \rightarrow \infty$
 $I = I_0$

$t = 0$
 $I = 0$

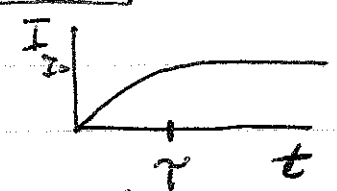


Current reaches its steady value in a time $\tau = L/R$

for $t \ll \tau$ most of potential drop is across the inductor since $IR \ll L \frac{dI}{dt}$
 for $t \gg \tau$ most of drops across resistor since $IR \gg L \frac{dI}{dt}$

LC Circuit (no resistance)

Consider a capacitor in series with an inductor. We initially charge the capacitor with a charge Q_0 .

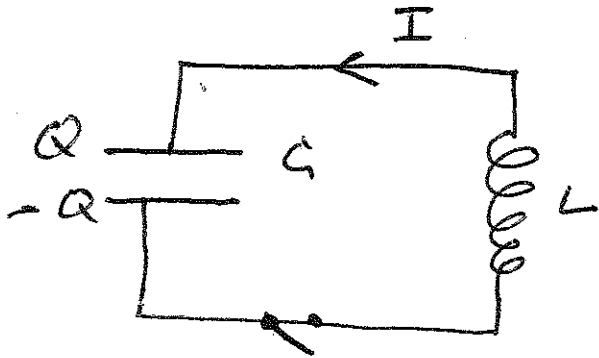Close the switch and follow the behaviour in time



$$\frac{dQ}{dt} = I$$

Using Kirchhoff's Loop rule in direction of I

$$-L \frac{dI}{dt} - \frac{Q}{C} = 0$$

$$\frac{d^2 Q}{dt^2} + \frac{1}{LC} Q = 0$$


$$\omega^2 = \frac{1}{LC}$$

$$\frac{d^2 Q}{dt^2} + \omega^2 Q = 0$$

same as equation for pendulum or spring/mass system,

$$Q = Q_0 \cos \omega t$$
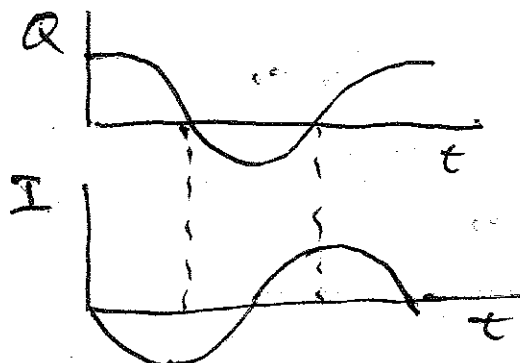
$$\text{Thus } I = \frac{dQ}{dt} = -\omega Q_0 \sin \omega t$$



Energy

$$L \frac{dI}{dt} + \frac{Q}{C} = 0$$

multiply by I

$$L I \frac{dI}{dt} + \frac{Q}{C} I = 0$$

$$\frac{d}{dt} \left(\frac{1}{2} L I^2 + \frac{d}{dt} \frac{Q^2}{2C} \right) = 0$$

$$\frac{d}{dt} \left(\frac{1}{2} L I^2 + \frac{1}{2} C V^2 \right) = 0$$


↑
energy
in
inductor

↑
energy in
capacitor

⇒ total energy conserved.

⇒ energy is exchanged between
the inductor and capacitor.

LRC Circuit

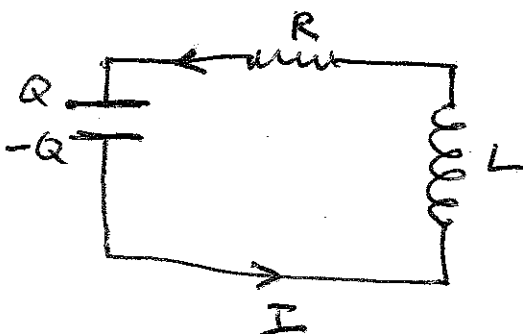

Loop rule


$$-L \frac{dI}{dt} - IR - \frac{Q}{C} = 0$$

$$\frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$$

energy

$$\frac{d}{dt} \left(\frac{1}{2} LI^2 + \frac{1}{2} CV^2 \right) = -I^2 R$$

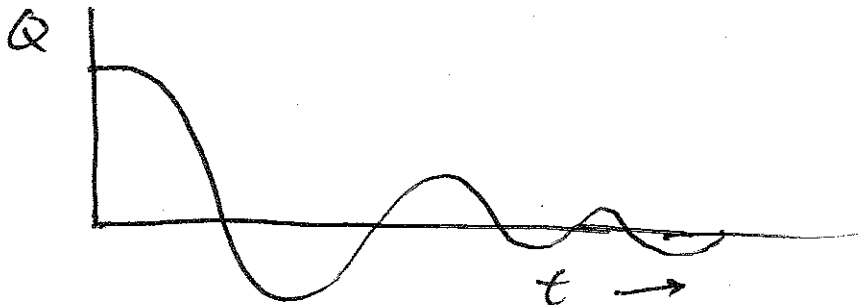The ~~any~~ energy stored in the inductor and ~~capacitor~~ capacitor is dissipated by the resistor.



Solution

$$Q = Q_0 e^{-t/\tau} \cos \omega t$$

$$\tau = \frac{2L}{R}$$

$$\omega = \left(\frac{1}{LC} - \frac{R^2}{4L^2} \right)^{\frac{1}{2}}$$

$$\text{for } \boxed{\frac{R^2}{4L^2} \leq \frac{1}{LC}}$$

⇒ R reduces the frequency of oscillation

⇒ charge damps with time.

⇒ oscillation with damping called underdamped oscillation


for $\frac{R^2}{4L^2} > \frac{1}{LC} \rightarrow$ large resistance

$$Q = Q_0 e^{-t/\tau} \left(\frac{e^{t/\tau_1} + e^{-t/\tau_1}}{2} \right)$$

$$\frac{1}{\tau_1} = \left(\frac{R^2}{4L^2} - \frac{1}{LC} \right)^{\frac{1}{2}}$$

\Rightarrow overdamped

\Rightarrow no oscillatory behavior

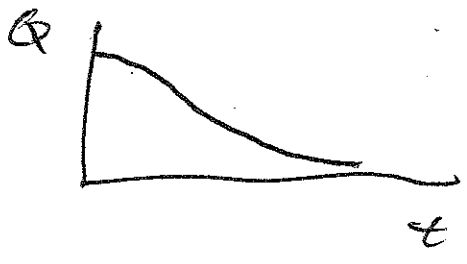


Mutual Inductance

Consider a coil of wire (coil 1) which has a current I_1 . This coil produces a magnetic field.

Suppose we have a second coil (coil 2) with N_2 turns.

The flux due to coil 1 which links through coil two is Φ_2 .

example circuit

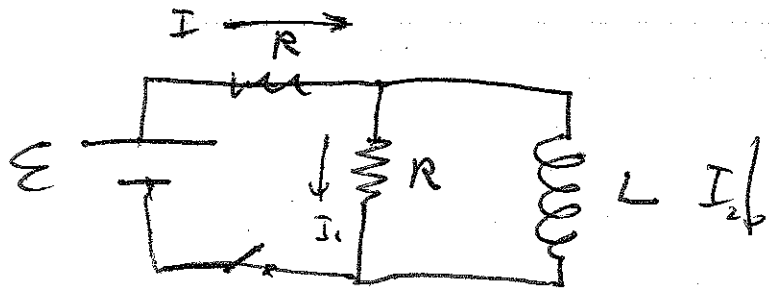

At $t=0$ close switch.

Find I_1, I_2, I just after switch is closed.

Current through I_2 is zero.

$$I = I_1$$

Loop rule

$$\epsilon - IR - I_1 R = 0$$

$$\epsilon - IR - IR = 0$$

$$\Rightarrow I = \frac{\epsilon}{2R}$$

After long time \Rightarrow steady state.

$$\frac{dI_2}{dt} = 0 \Rightarrow \text{EMF across inductor is zero}$$

loop rule


$$-I_1 R + L \frac{dI_2}{dt} = 0$$

$$\Rightarrow I_1 = 0$$

loop rule

$$\epsilon - IR = 0 \quad I = \frac{\epsilon}{R}$$

AC Circuit

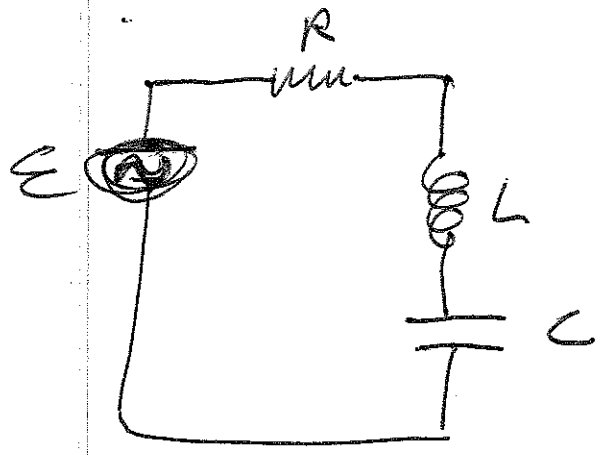

$$\Sigma = \Sigma_0 \sin \omega t$$

if $L=0, C=0$

$$\Sigma_0 \sin \omega t - IR = 0$$

$$I = \frac{\Sigma_0}{R} \sin \omega t$$

Current and emf in phase

$$\Sigma_0 \sin \omega t - IR - L \frac{dI}{dt} - \frac{Q}{C} = 0$$

⇒ note that because of L and C, I not in phase with Σ_0 .

Let $Q = Q_s \sin \omega t + Q_c \cos \omega t$

$$I = \omega Q_s \cos \omega t - \omega Q_c \sin \omega t$$

$$\frac{dI}{dt} = -\omega^2 Q_s \sin \omega t - \omega^2 Q_c \cos \omega t$$

Gather $\sin \omega t$ and $\cos \omega t$ together separately.

$$[]_1 \sin \omega t + []_2 \cos \omega t = 0$$

$$\cancel{\Sigma_0 \sin \omega t} + \omega Q_c R + L \omega^2 Q_s - \frac{Q_s}{C} = 0$$

$$\Rightarrow Q_c = Q_s \left(\frac{1}{C} - L \omega^2 \right) \frac{1}{\omega R} - \frac{\Sigma_0}{\omega R}$$

~~...~~

$$-\omega Q_s R + L \omega^2 Q_c - \frac{Q_c}{C} = 0$$

$$\Rightarrow Q_s = \left(\omega^2 L - \frac{1}{C} \right) \frac{Q_c}{\omega R}$$

$$Q_c = - \left(\frac{1}{L} + \omega^2 R \right) \left(\omega^2 L - \frac{1}{C} \right) \frac{Q_c L^2}{\omega R^2} - \frac{\epsilon_0}{\omega R}$$

$$\omega^2 Q_c \neq \left(\omega^2 - \frac{1}{LC} \right)^2 \frac{L^2}{\omega R^2} Q_c = - \frac{\epsilon_0 \omega}{R}$$

$$\gamma = \frac{L}{R}$$

$$Q_c \left[\omega^2 + \left(\omega^2 - \frac{1}{LC} \right)^2 \gamma^2 \right] = - \omega \frac{\epsilon_0}{R}$$

$$Q_c = \frac{- \omega \frac{\epsilon_0}{R}}{\left[\omega^2 + \left(\omega^2 - \frac{1}{LC} \right)^2 \gamma^2 \right]}$$

also can find Q_s

\Rightarrow suppose R is very small $\Rightarrow \gamma$ large.

Q_c small if $\omega^2 \neq \frac{1}{LC}$

At $\omega^2 = \frac{1}{LC}$ $Q_s = 0$

$$Q_c = - \omega \frac{\epsilon_0}{R \omega^2} = - \left(\frac{\epsilon_0}{R} \right) \frac{1}{\omega}$$

\uparrow as $R \rightarrow 0$ Q_c

$$I = \cancel{\omega Q_c \cos \omega t} + \frac{\epsilon_0}{R} \sin \omega t$$

\Rightarrow large current \Rightarrow resonance.

Maxwells Eqs

Have found that if have a magnetic field which varies in time, we generate an inductive electric field.

What if we have an electric field which varies in time

⇒ produces a magnetic field

Maxwells Eqs

closed surface {

$$\oint \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0}$$


$$\oint \vec{B} \cdot d\vec{A} = 0$$

~~the~~ magnetic field lines don't start or stop. Displacement current

surface with bounding curve. {

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I + \mu_0 \epsilon_0 \frac{d}{dt} \oint \vec{E} \cdot d\vec{A}$$

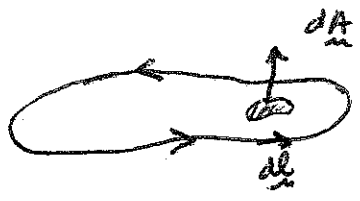
$$\oint \vec{E} \cdot d\vec{l} = - \frac{d}{dt} \oint \vec{B} \cdot d\vec{A}$$



~~Addition~~


Induced magnetic fields

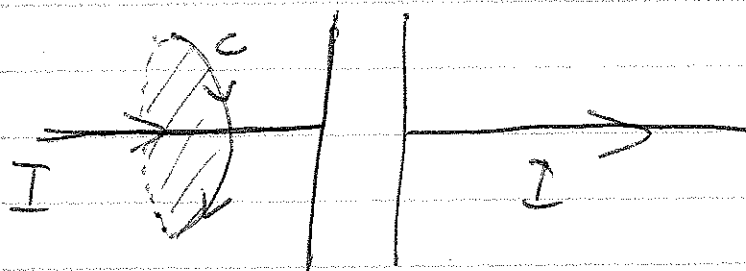Consider a current carrying wire entering a parallel plate capacitor



$$\oint_C \underline{B} \cdot d\underline{l} = \mu_0 I$$

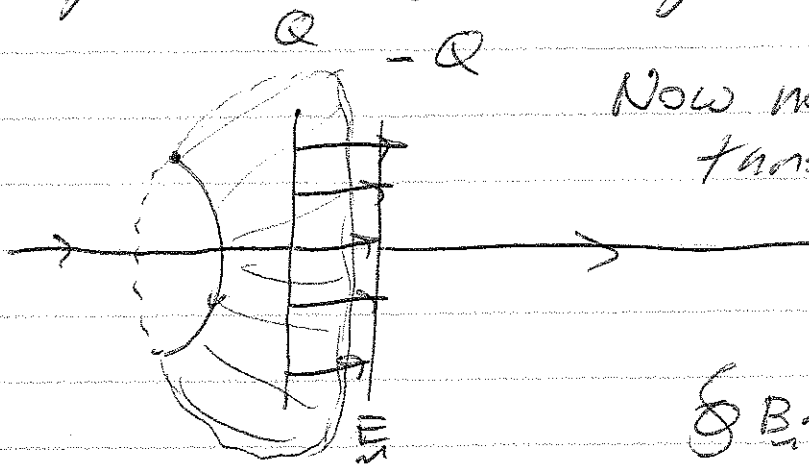Now distort the surface enclosing C to pass through the capacitor



Now no current cuts through the surface so Ampere's law says

$$\oint_C \underline{B} \cdot d\underline{l} = 0$$

\Rightarrow this is not possible since know that \underline{B} has not changed.

$$\oint \underline{B} \cdot d\underline{l} = \mu_0 \epsilon_0 \frac{d}{dt} \oint \underline{E} \cdot d\underline{A}$$

In the capacitor

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0}$$

$$\begin{aligned} \oint \underline{E} \cdot d\underline{A} &= \int E dA \quad (dA \text{ points to right}) \\ &= EA \\ &= \frac{Q}{\epsilon_0} \end{aligned}$$

$$\oint \underline{B} \cdot d\underline{l} = \mu_0 \epsilon_0 \frac{d}{dt} \left(\frac{Q}{\epsilon_0} \right) = \mu_0 I$$

\Rightarrow same as before.

\Rightarrow this completes Maxwell's Eqs

changing \underline{B} \Rightarrow \underline{E}

changing \underline{E} \Rightarrow \underline{B}

\Rightarrow electromagnetic waves (light).