

example

resistivity of copper  $\rho = 1.72 \times 10^{-8} \Omega \text{m}$   
 steel  $20 \times 10^{-8}$

How long is a copper wire with  $A = 1 \text{ mm}^2$   
 which has  $R = 1 \Omega$ .

$$R = 1 \Omega = \frac{1.72 \times 10^{-8} \Omega \text{m} L}{10^{-6} \text{m}^2}$$



$$L_c = \frac{1}{.0172} \text{m} \approx 58 \text{m}$$

$$L_s = \frac{1}{.2} \text{m} = 5 \text{m}$$


Electromotive Force and Circuits

An electric current always flows down a potential hill. To complete a circuit the

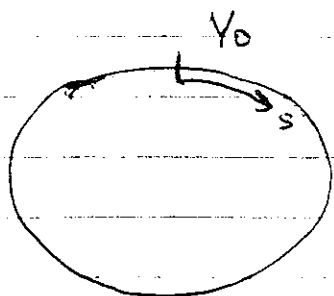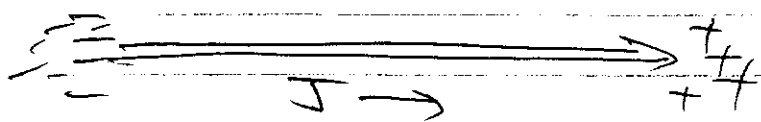current must close on itself or charge will accumulate



$V$  can decrease around a closed loop

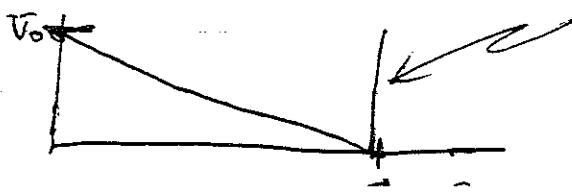


need some mechanism to reset the voltage buildup.

source of voltage

An electromotive force ~~is~~ forces charge  
up hill to a higher potential (EMF)

⇒ acts against the electric field,

⇒ measured in volts

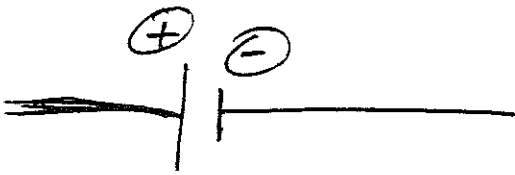

represents a source of  
emf,

⇒ example a roller coaster

⇒ the chain pulls the car up along hill. (emf)

⇒ gravity the ~~is~~ accelerates the car  
until reaches the start

⇒ cycle repeats

} current  
driven by  
potential  
drop.

examples

A battery ⇒ chemical reaction forces  
charge up the potential

Electric Generator

etc

Van de Graaf Machine.

# Kirchoff's Loop Rule

~~The sum of the~~


As you ~~to~~ move completely around a current loop you must arrive back at the potential where you started.

⇒ the sum of the potential drops around the loop must equal the sum of the EMFs.
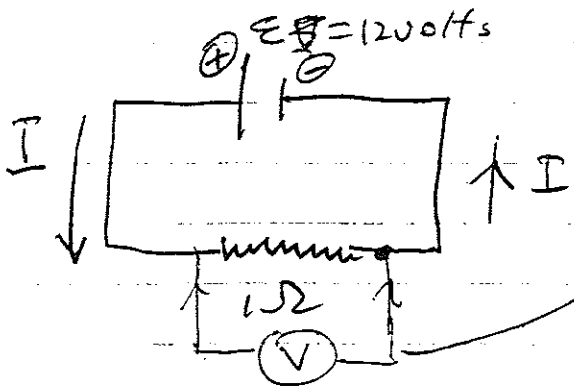
## example

Consider a circuit with an EMF of 12 volts and a resistor with a resistance of  $1 \Omega$ .

Neglect resistance of the ~~wire~~ wire. (How make a resistor?) counter clockwise




$$-IR + \mathcal{E} = 0$$

$$I = \frac{12 \text{ volts}}{1 \Omega}$$

$$= 12 \text{ amps}$$

$$\dots - IR = 0$$

example

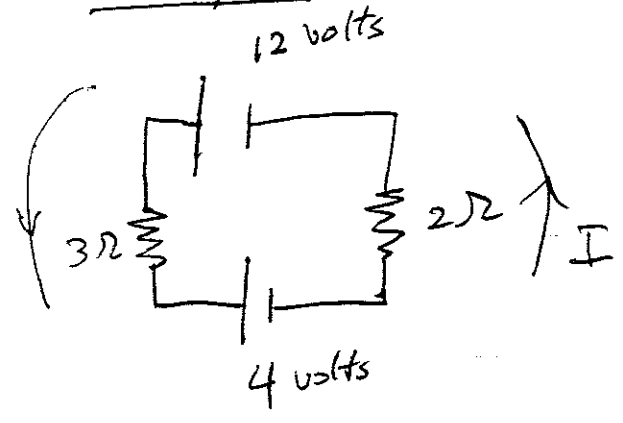


$$-I 3\Omega - 4 \text{ volts} - 2\Omega I + 12 \text{ volts} = 0$$


$$I = \frac{8}{5} \text{ amps}$$

Energy Dissipation in a Resistor

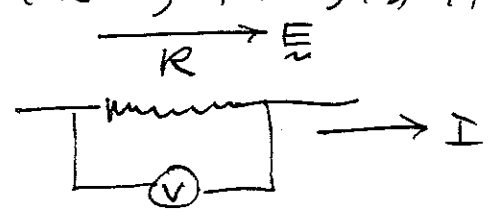Consider a resistor  $R$  with current  $I$  flowing through it.



$$V = IR$$

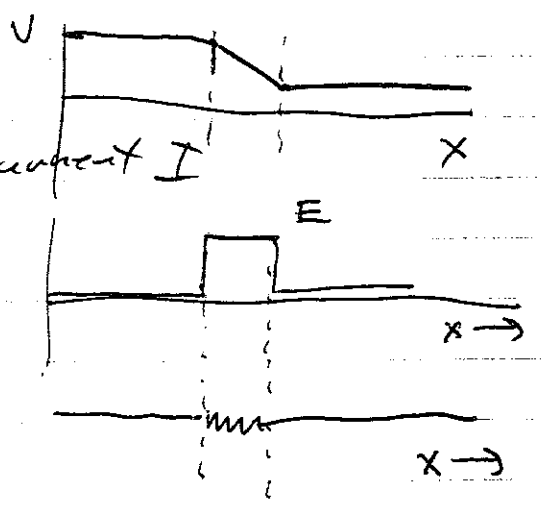

Consider a charge  $dQ$  which moves down the potential hill

⇒ receives energy,

$$dW = dQ V$$

from the electric field ⇒ ~~lost~~ lost as heat during collisions in resistor

Rate of energy transfer to heat in resistor

$$\frac{dW}{dt} = P = \text{power} = \frac{dQ}{dt} V$$

$$= IV$$

$$P = IV = I^2 R$$

units 1 watt =  $\frac{\text{coul}}{\text{sec}} \frac{\text{Joule}}{\text{coul}}$

$$= \frac{\text{Joule}}{\text{sec}}$$

$$V = 120 \text{ volts}$$

$$R = 10 \Omega$$

$$I = 12 \text{ amps}$$

$$P = \underline{1440 \text{ watt}}$$

Source of Energy from EMF



The emf raises the charge  $dQ$  up the potential  $\mathcal{E}$

$\Rightarrow$  gives charge  $dW = dQ\mathcal{E}$

$$\frac{dW}{dt} = I\mathcal{E}$$

$\mathcal{E}I =$  rate at which emf supplies energy to the charges moving through the emf.

Resistors in Series

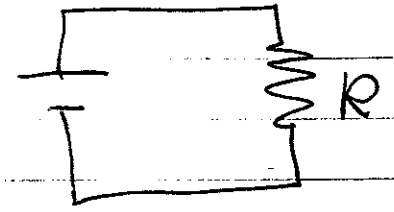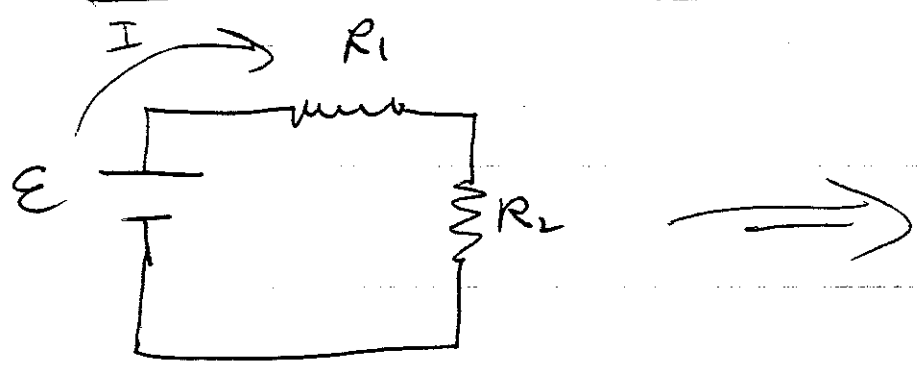


$$\mathcal{E} - IR_1 - IR_2 = 0$$

$$\mathcal{E} - I(R_1 + R_2) = 0$$

$$R = R_1 + R_2$$

⇒ currents through all resistors are the same

Resistors in Parallel

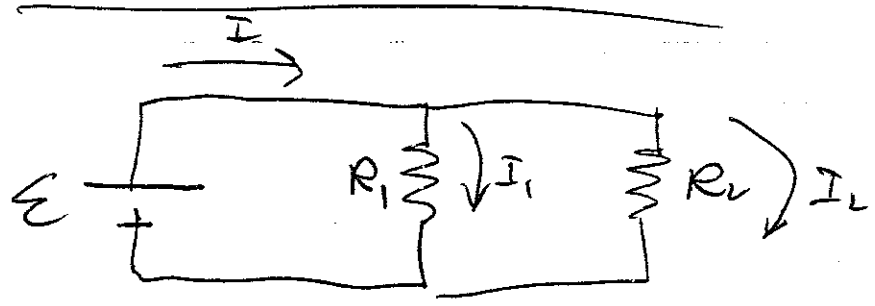

→ voltage drop across  $R_1$  and  $R_2$  is equal

$$I_1 R_1 = I_2 R_2 \quad I_1 = I_2 \frac{R_2}{R_1}$$

~~$$\mathcal{E} = IR = (I_1 + I_2)R$$~~

$$I = I_1 + I_2 = I_2 \frac{R_2}{R_1} + I$$

~~$$I_2$$~~

$$I = \frac{\mathcal{E}}{R}$$

$$I = I_2 \left( 1 + \frac{R_2}{R_1} \right)$$

$$\mathcal{E} = I_2 R_2$$

$$I_2 = \frac{\mathcal{E}}{R_2}$$

$$I = \frac{\mathcal{E}}{R_2} \left( 1 + \frac{R_2}{R_1} \right)$$


$$= \mathcal{E} \left( \frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{\mathcal{E}}{R}$$

$$\Rightarrow \boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}}$$

## Kirchoff's Rules


For circuits more

## Mixed Circuits

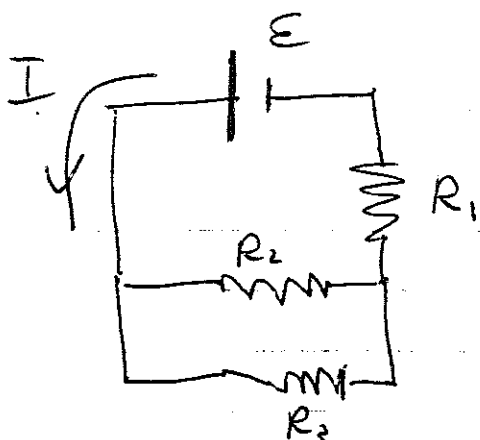


Consider the circuit shown.

First consider

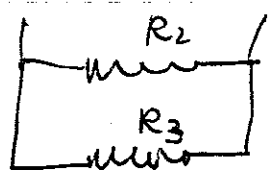


$\Rightarrow$

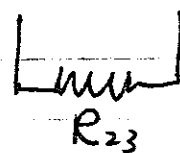

$$\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_3}$$

We are left with

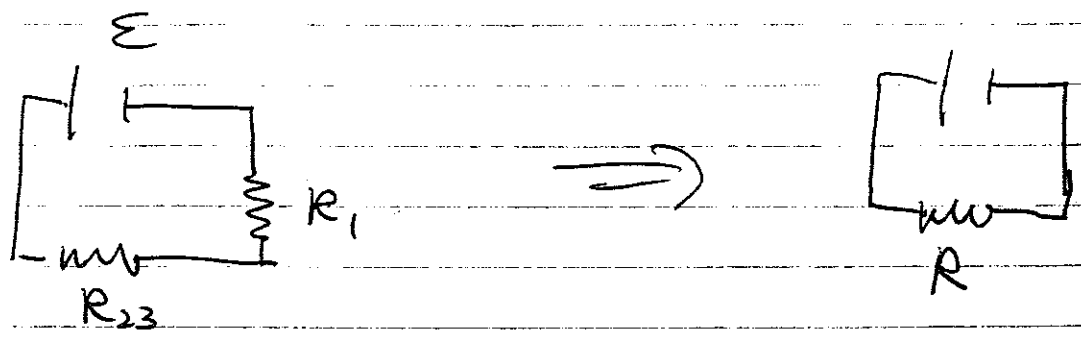

$$R = R_1 + R_{23}$$


$$R = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

~~More complex~~

### Kirchoffs Rules

Some circuits can not be collapsed to parallel resistors or series resistors

Eg.

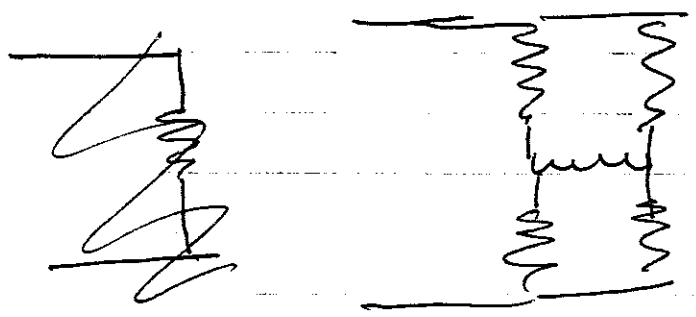

Have two rules to deal with such circuits.




A branch point is a point where three or more conductors join together,

A loop is any closed path in the circuit.

Have two rules to deal with these complex circuits.

① point rule - the sum of the currents towards any branch point is zero

$$\sum_i I_i = 0$$

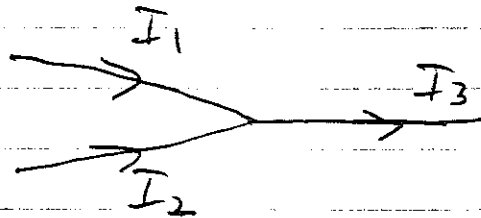

$$I_1 + I_2 - I_3 = 0$$

note that current toward

B.P. are

$I_1$


$I_2$

$-I_3$

② The sum of the potential differences around any loop must equal zero.

⇒ includes EMFs

example

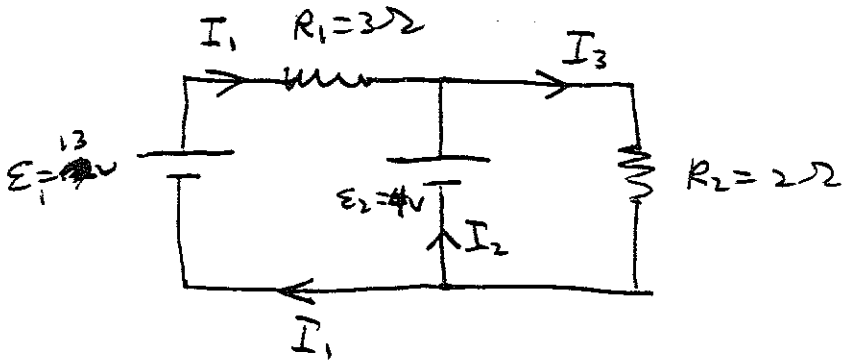

pt rule

$$I_1 + I_2 - I_3 = 0$$

loop rule

$$E_1 - I_1 R_1 - E_2 = 0 \Rightarrow I_1 = \frac{E_1 - E_2}{R_1}$$

$$I_1 = \frac{9V}{3\Omega} = 3A$$

$$E_2 - I_3 R_2 = 0$$

$$I_3 = \frac{E_2}{R_2}$$

$$I_3 = \frac{4V}{2\Omega} = 2A$$

$$I_2 = I_3 - I_1 = -1A$$



what does this mean?


voltage drop across  $R_1$ ?

$$I_1 R_1 = 9 \text{ volts}$$

voltage across  $R_2$

$$I_3 R_2 = 4 \text{ volts}$$

Add switch on  $I_2$  wire

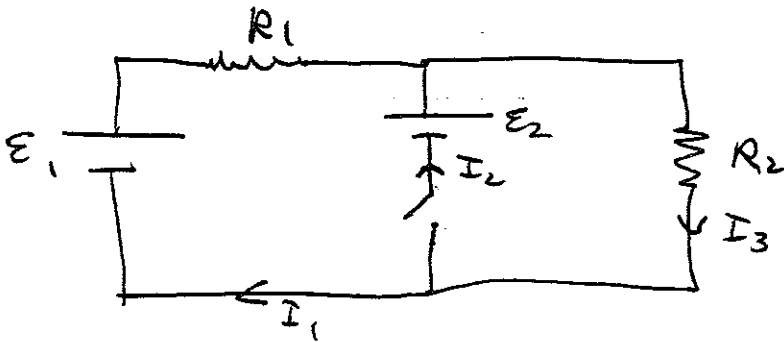

$$\Rightarrow \underline{I_2 = 0}$$

$$\Rightarrow I_1 = I_3$$

~~$$\mathcal{E}_1 - I_1 R_1 - I_3 R_2 = 0$$~~

~~$$\mathcal{E}_1 - I_1 R_1 - I_1 R_2 = 0$$~~

$$I_1 = \frac{\mathcal{E}_1}{R_1 + R_2} = \frac{13}{5} \text{ A.}$$

what is pot drop across  $R_1$ ?  $R_2$ ?

$$I_1 R_1 = \frac{39}{5} \text{ V}$$

$$\frac{26}{5} \text{ V}$$

across switch?

~~$$\Delta V + \mathcal{E}_2 + I_1 R_1 - \mathcal{E}_1 = 0$$~~


$$\Delta V + 4\text{V} + \frac{39}{5}\text{V} - 13\text{V} = 0$$

$$\Delta V + 4\text{V} + \frac{4}{5}\text{V} = 0$$

$$\Delta V = -\frac{4}{5}\text{V}$$
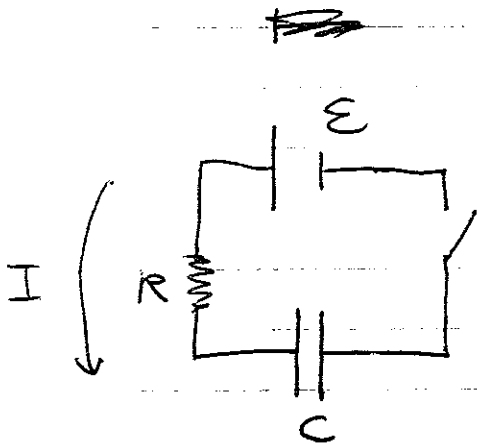
## RC Circuit

Consider a circuit with an emf  $\mathcal{E}$ , a resistor  $R$  and a capacitor  $C$ .



At  $t=0$  we throw the switch. A current will flow.

Charge will build up on the capacitor until the

potential drop across the capacitor is equal to  $\mathcal{E}$ . To show this, add

~~up~~ up the potential ~~changes~~ jumps around the loop.

$$V_C = \frac{Q}{C}$$

$$\mathcal{E} - IR - \frac{Q}{C} = 0$$

$$\mathcal{E} - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

$$\frac{dQ}{dt} + \frac{1}{RC} Q = \frac{\mathcal{E}}{R}$$

$$\text{Let } \tau = RC$$

$$\frac{dQ}{dt} + \frac{1}{\tau} Q = \frac{\epsilon A}{R A} = \frac{\epsilon A}{\tau}$$

$\tau =$  time constant for RC circuit

$\Rightarrow$  characteristic time required to build up charge on the capacitor.

$\Rightarrow$  larger resistance to current flow  $\Rightarrow$  longer time

$\Rightarrow$  larger capacitance longer time.  
(over)

Solution

$$Q = \frac{\epsilon \tau A}{R} \left( 1 - e^{-t/\tau} \right)$$

~~As  $t \rightarrow \infty$~~

For  $t \gg \tau \Rightarrow e^{-t/\tau} \ll 1$

$$Q \approx \frac{\epsilon \tau}{R} = \frac{\epsilon A}{R} \epsilon$$

$\Rightarrow$  potential across capacitor  $= \epsilon$

$$I = \frac{dQ}{dt} = \frac{\epsilon \tau}{R} \left( \frac{d}{dt} 1 - \frac{d}{dt} e^{-t/\tau} \right)$$

$$= \frac{\epsilon \tau}{R} \left( \frac{1}{\tau} e^{-t/\tau} \right) = \frac{\epsilon}{R} e^{-t/\tau}$$

$$t \ll \tau \quad I = \frac{\epsilon}{R} \quad t \gg \tau \quad I \rightarrow 0.$$


$$\frac{dQ}{dt} = \frac{\varepsilon A - Q}{\tau}$$

$$\int_0^Q \frac{dQ}{\varepsilon A - Q} = \int_0^t \frac{dt}{\tau}$$


$$+ \ln(\varepsilon A - Q) \Big|_0^Q = -\frac{t}{\tau}$$

$$\frac{\varepsilon A - Q}{\varepsilon A} = e^{-\frac{t}{\tau}} (\varepsilon A)$$
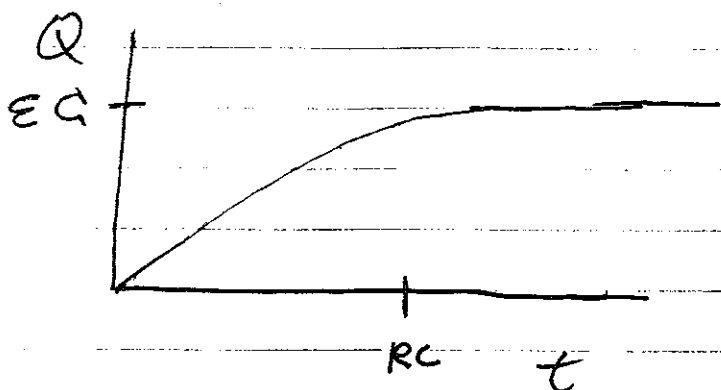
$$Q = \varepsilon A (1 - e^{-\frac{t}{\tau}})$$




$$I = \frac{dQ}{dt}$$

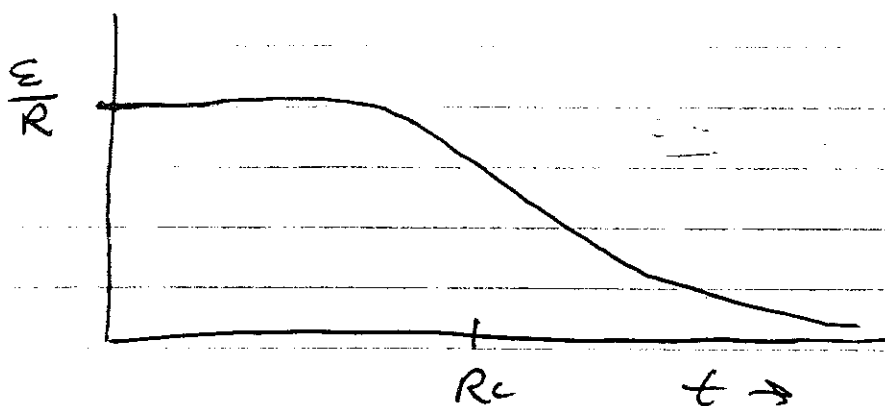
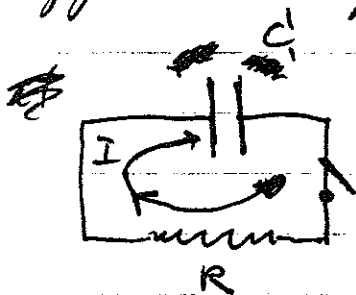
### Discharging a Capacitor

Suppose a capacitor has a charge  $Q_0$ .



The capacitor is connected in series with a resistor. At  $t=0$  the switch is closed.

$$-IR + \frac{Q}{C} = 0$$

~~$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$~~

$$\frac{dQ}{dt} + \frac{Q}{\tau} = 0$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = - \int_0^t \frac{dt}{\tau} = - \frac{t}{\tau}$$

$$\ln \frac{Q}{Q_0} = - \frac{t}{\tau}$$

$$\frac{Q}{Q_0} = e^{-t/\tau}$$