

# SOLUTIONS CHAPTER 16


8. There are eight different combinations that use all three capacitors in the circuit. These combinations and their equivalent capacitances are:

All three capacitors in series -  $C_{eq} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$

All three capacitors in parallel -  $C_{eq} = C_1 + C_2 + C_3$


One capacitor in series with a parallel combination of the other two:
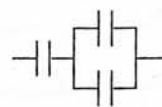
$$C_{eq} = \left( \frac{1}{C_1 + C_2} + \frac{1}{C_3} \right)^{-1}, C_{eq} = \left( \frac{1}{C_3 + C_1} + \frac{1}{C_2} \right)^{-1}, C_{eq} = \left( \frac{1}{C_2 + C_3} + \frac{1}{C_1} \right)^{-1}$$



One capacitor in parallel with a series combination of the other two:
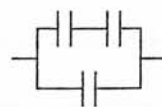
$$C_{eq} = \left( \frac{1}{C_1 + C_2} \right)^{-1} + C_3, C_{eq} = \left( \frac{1}{C_3 + C_1} \right)^{-1} + C_2, C_{eq} = \left( \frac{1}{C_2 + C_3} \right)^{-1} + C_1$$



12. The energy stored in a capacitor is  $W = \frac{1}{2}C(\Delta V)^2$ .

- (a) If the potential difference is doubled while all other factors remain constant, the stored energy is quadrupled.
- (b) Assuming a parallel plate capacitor, the capacitance is  $C = \kappa\epsilon_0 A/d$  and the energy stored becomes  $W = \frac{\kappa\epsilon_0 A(\Delta V)^2}{2d}$ . Thus, if the plate separation is doubled while the potential difference is held constant, the stored energy will be cut in half.

16.5  $E = \frac{|\Delta V|}{d} = \frac{25\,000 \text{ J/C}}{1.5 \times 10^{-2} \text{ m}} = \boxed{1.7 \times 10^6 \text{ N/C}}$

16.8 (a)  $|\Delta V| = Ed = (5.90 \times 10^3 \text{ V/m})(1.00 \times 10^{-2} \text{ m}) = \boxed{59.0 \text{ V}}$

(b)  $\frac{1}{2}m_e v^2 - 0 = \Delta KE = W = -\Delta PE_e = |q(\Delta V)|,$

$$\text{so } v = \sqrt{\frac{2|q(\Delta V)|}{m_e}} = \sqrt{\frac{2(1.60 \times 10^{-19} \text{ C})(59.0 \text{ J/C})}{9.11 \times 10^{-31} \text{ kg}}} = \boxed{4.55 \times 10^6 \text{ m/s}}$$

16.12 Calling  $q_3$  the charge at the corner opposite  $P$ ,

$$\begin{aligned}
V &= V_1 + V_2 + V_3 = k_e \left( \frac{q_1}{r_1} + \frac{q_2}{r_2} + \frac{q_3}{\sqrt{r_1^2 + r_2^2}} \right) \\
&= \left( 8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \right) \left( \frac{8.00 \times 10^{-6} \text{ C}}{0.200 \text{ m}} - \frac{8.00 \times 10^{-6} \text{ C}}{0.350 \text{ m}} + \frac{12.0 \times 10^{-6} \text{ C}}{\sqrt{(0.200)^2 + (0.350)^2} \text{ m}} \right) \\
&= \boxed{4.22 \times 10^5 \text{ V}}
\end{aligned}$$

16.19 From conservation of energy,  $(KE + PE_e)_f = (KE + PE_e)_i$ , which gives


$$\begin{aligned}
0 + \frac{k_e Qq}{r_f} &= \frac{1}{2} m_\alpha v_i^2 + 0 \text{ or } r_f = \frac{2k_e Qq}{m_\alpha v_i^2} = \frac{2k_e (79e)(2e)}{m_\alpha v_i^2} \\
r_f &= \frac{2 \left( 8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \right) (158)(1.60 \times 10^{-19} \text{ C})^2}{(6.64 \times 10^{-27} \text{ kg})(2.00 \times 10^7 \text{ m/s})^2} = \boxed{2.74 \times 10^{-14} \text{ m}}
\end{aligned}$$

16.25 (a)  $E = \frac{\Delta V}{d} = \frac{20.0 \text{ V}}{1.80 \times 10^{-3} \text{ m}} = 1.11 \times 10^4 \text{ V/m} = \boxed{11.1 \text{ kV/m}}$  directed toward the negative plate

(b)  $C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(7.60 \times 10^{-4} \text{ m}^2)}{1.80 \times 10^{-3} \text{ m}}$   
 $= 3.74 \times 10^{-12} \text{ F} = \boxed{3.74 \text{ pF}}$

(c)  $Q = C(\Delta V) = (3.74 \times 10^{-12} \text{ F})(20.0 \text{ V}) = 7.47 \times 10^{-11} \text{ C} = \boxed{74.7 \text{ pC}}$  on one plate and  $\boxed{-74.7 \text{ pC}}$  on the other plate.

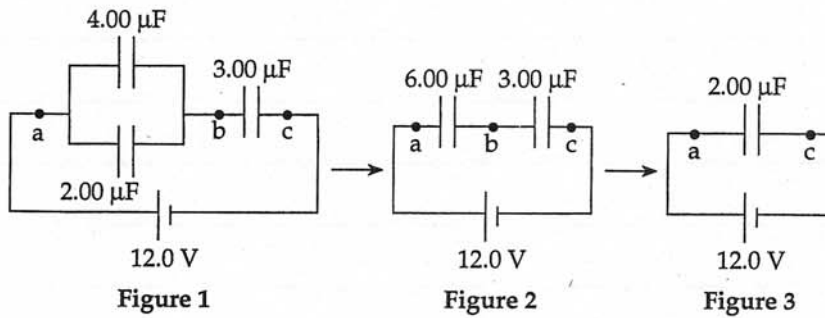- 16.31 (a) Using the rules for combining capacitors in series and in parallel, the circuit is reduced in steps as shown below. The equivalent capacitor is shown to be a  $2.00 \mu\text{F}$  capacitor.



(b) From Figure 3:  $Q_{ac} = C_{ac} (\Delta V)_{ac} = (2.00 \mu\text{F})(12.0 \text{ V}) = 24.0 \mu\text{C}$

From Figure 2:  $Q_{ab} = Q_{bc} = Q_{ac} = 24.0 \mu\text{C}$

Thus, the charge on the  $3.00 \mu\text{F}$  capacitor is  $Q_3 = 24.0 \mu\text{C}$

Continuing to use Figure 2,  $(\Delta V)_{ab} = \frac{Q_{ab}}{C_{ab}} = \frac{24.0 \mu\text{C}}{6.00 \mu\text{F}} = 4.00 \text{ V}$ ,

and  $(\Delta V)_3 = (\Delta V)_{bc} = \frac{Q_{bc}}{C_{bc}} = \frac{24.0 \mu\text{C}}{3.00 \mu\text{F}} = 8.00 \text{ V}$

From Figure 1,  $(\Delta V)_4 = (\Delta V)_2 = (\Delta V)_{ab} = 4.00 \text{ V}$

and  $Q_4 = C_4 (\Delta V)_4 = (4.00 \mu\text{F})(4.00 \text{ V}) = 16.0 \mu\text{C}$

$Q_2 = C_2 (\Delta V)_2 = (2.00 \mu\text{F})(4.00 \text{ V}) = 8.00 \mu\text{C}$

16.35

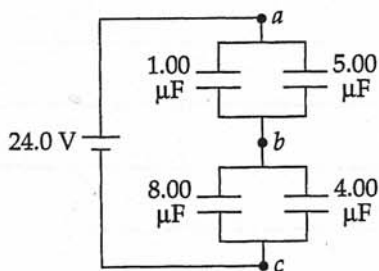


Figure 1

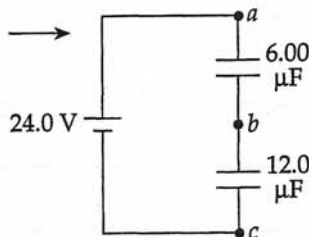


Figure 2

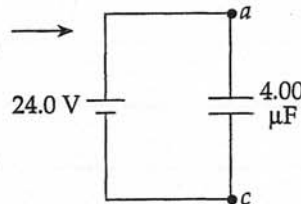


Figure 3

The circuit may be reduced in steps as shown above.

Using the Figure 3,  $Q_{ac} = (4.00 \mu\text{F})(24.0 \text{ V}) = 96.0 \mu\text{C}.$

Then, in Figure 2,  $(\Delta V)_{ab} = \frac{Q_{ac}}{C_{ab}} = \frac{96.0 \mu\text{C}}{6.00 \mu\text{F}} = 16.0 \text{ V},$

and  $(\Delta V)_{bc} = (\Delta V)_{ac} - (\Delta V)_{ab} = 24.0 \text{ V} - 16.0 \text{ V} = 8.00 \text{ V}.$

Finally, using Figure 1,  $Q_1 = C_1(\Delta V)_{ab} = (1.00 \mu\text{F})(16.0 \text{ V}) = \boxed{16.0 \mu\text{C}},$

$Q_5 = (5.00 \mu\text{F})(\Delta V)_{ab} = \boxed{80.0 \mu\text{C}},$       $Q_8 = (8.00 \mu\text{F})(\Delta V)_{bc} = \boxed{64.0 \mu\text{C}},$

and  $Q_4 = (4.00 \mu\text{F})(\Delta V)_{bc} = \boxed{32.0 \mu\text{C}}$

16.44 (a) When connected in parallel, the energy stored is

$$W = \frac{1}{2}C_1(\Delta V)^2 + \frac{1}{2}C_2(\Delta V)^2 = \frac{1}{2}(C_1 + C_2)(\Delta V)^2$$

$$= \frac{1}{2}[(25.0 + 5.00) \times 10^{-6} \text{ F}](100 \text{ V})^2 = \boxed{0.150 \text{ J}}$$

(b) When connected in series, the equivalent capacitance is

$$C_{eq} = \left( \frac{1}{25.0} + \frac{1}{5.00} \right)^{-1} \mu\text{F} = 4.17 \mu\text{F}$$

From  $W = \frac{1}{2}C_{eq}(\Delta V)^2$ , the potential difference required to store the same energy as in part (a) above is

$$\Delta V = \sqrt{\frac{2W}{C_{eq}}} = \sqrt{\frac{2(0.150 \text{ J})}{4.17 \times 10^{-6} \text{ F}}} = \boxed{268 \text{ V}}$$